
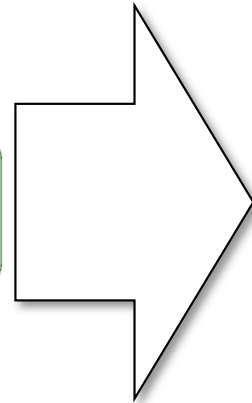


# HexBot 2

## Circuits & Wiring

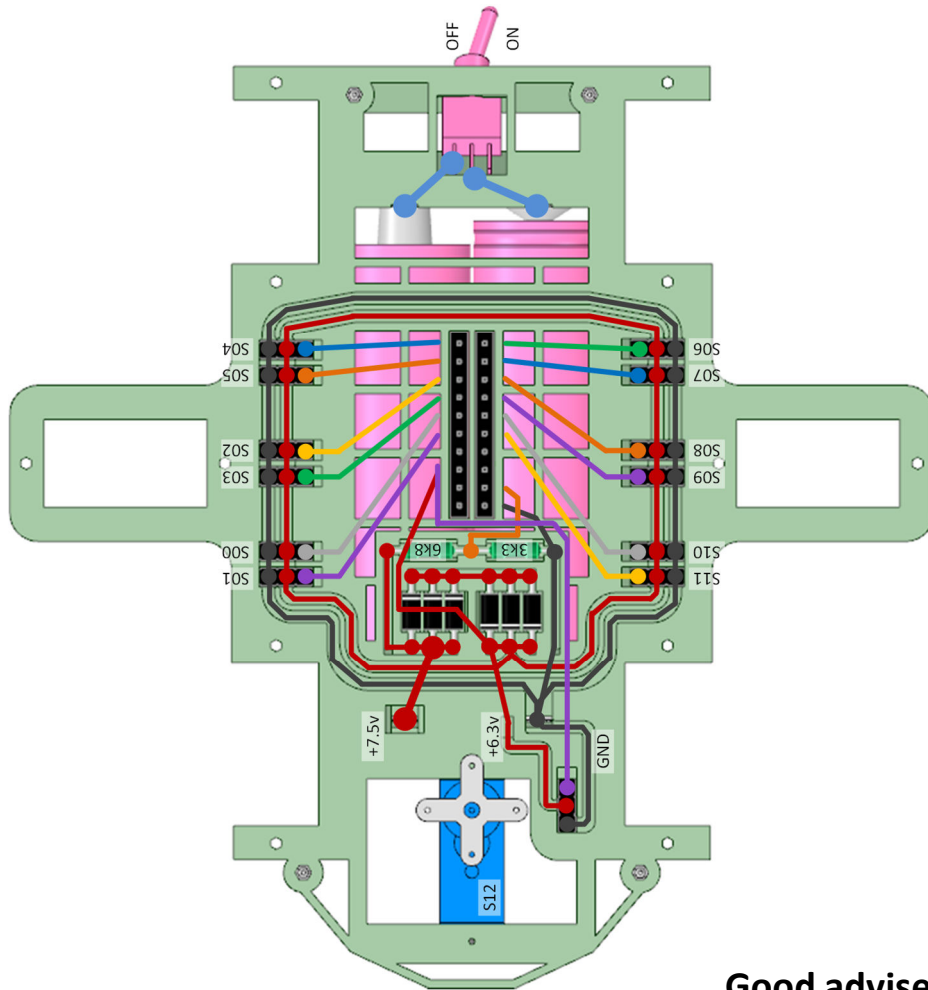

**Good advise:** read through the whole of this document before attempting this project.

# Hand Tools:

## Recommended:

- Fine Nosed Pliers
- Side Cutters
- 1.5 mm Drill
- 2.0 mm Drill
- 4.0 mm Drill
- Needle Files
- Screwdrivers
- Craft Knife



Note: Not all items are shown here.

# Tools & Materials:

- Temperature controlled iron
- Solder flux
- Resin cored solder
- Hot melt glue gun
- 2-part epoxy resin glue
- Screw drivers
- Wire wrapping tool
- Wire wrapping wire 30 AWG
- 24 AWG stranded wire (red & black)





# Special Tools

Hot air gun for heat shrink sleeving


Ratchet crimping tool + 2.54mm female connectors



Watch videos on the internet to learn how to best use this tool, before attempting to shorten the servo leads.




# HexBot 2 Total Wiring

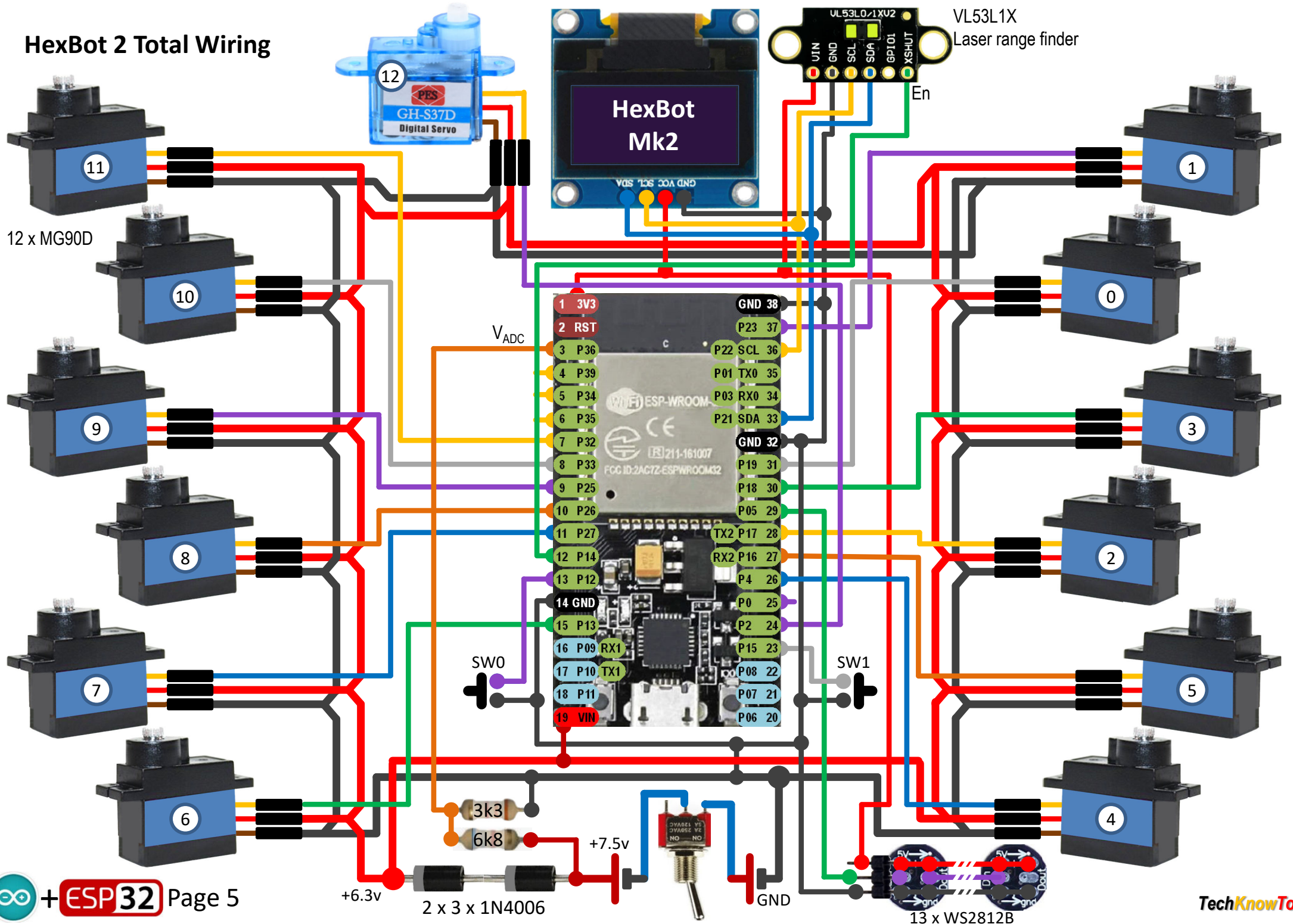

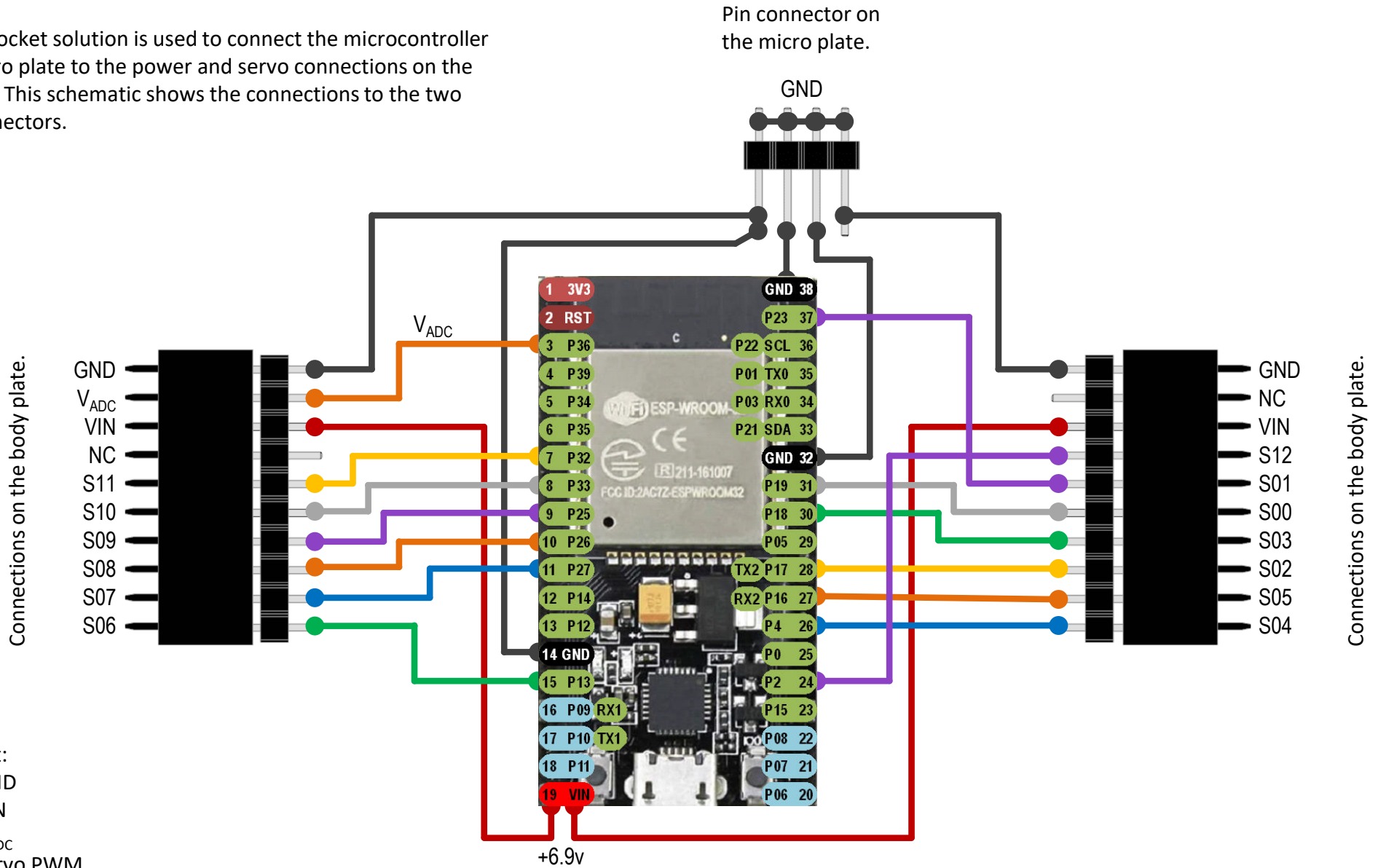
# HexdBot 2 Control Wiring

A pin and socket solution is used to connect the microcontroller on the micro plate to the power and servo connections on the body plate. This schematic shows the connections to the two 10 pin connectors.


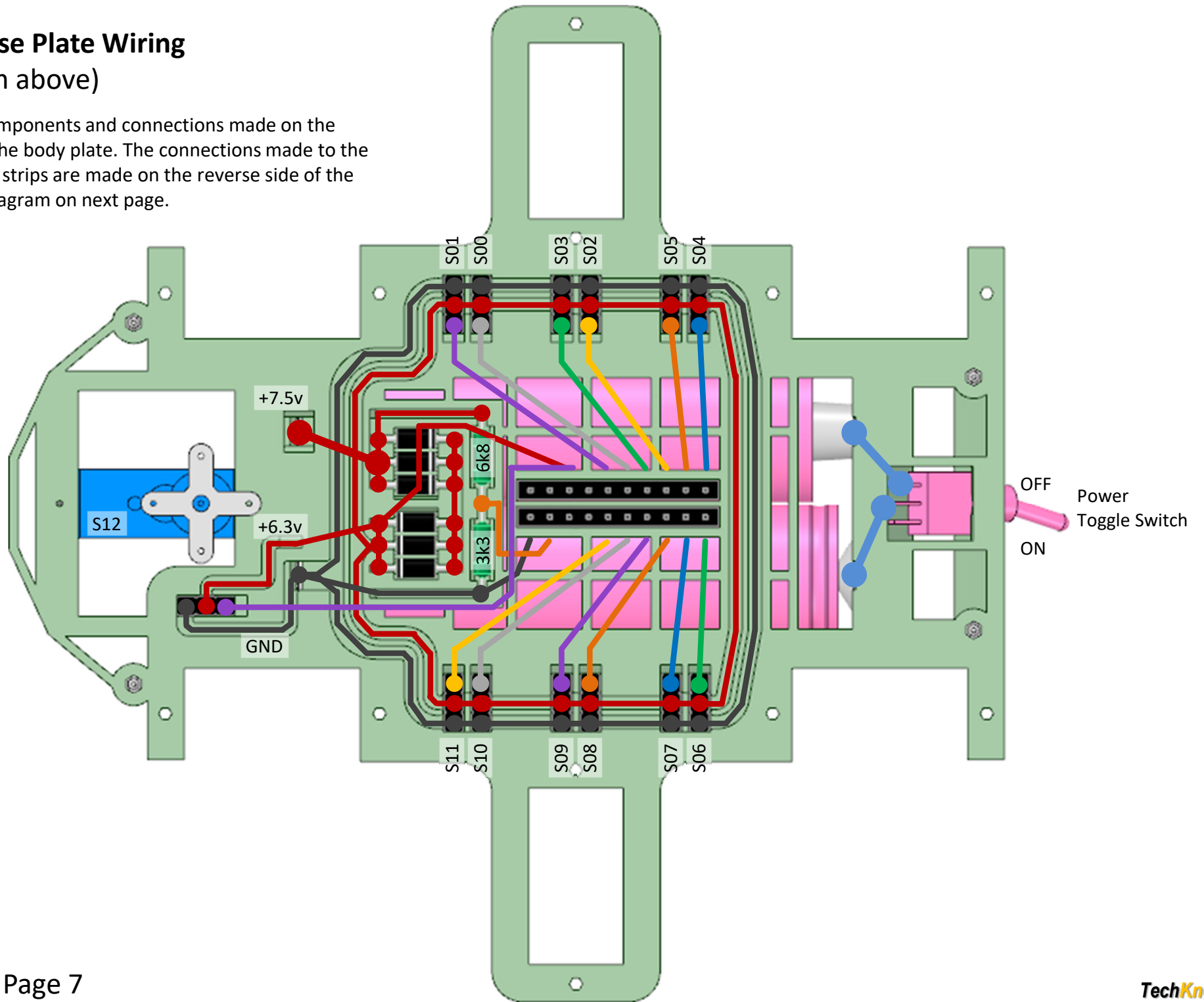
## HexBot 2 Base Plate Wiring (viewed from above)


This shows the components and connections made on the upper surface of the body plate. The connections made to the two 10-pin socket strips are made on the reverse side of the body plate. See diagram on next page.





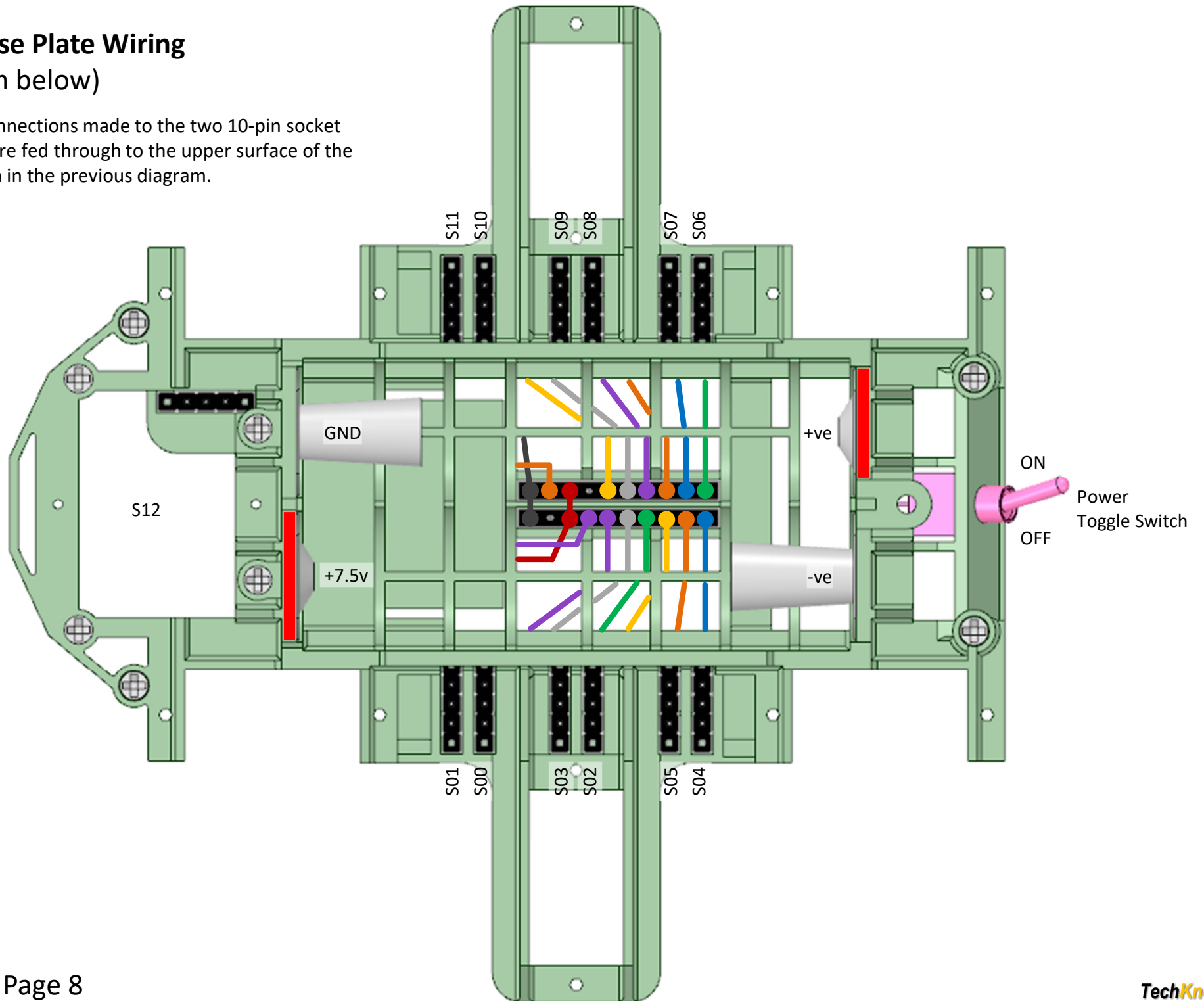
## HexBot 2 Base Plate Wiring (viewed from below)

This shows the connections made to the two 10-pin socket strips. The wires are fed through to the upper surface of the body plate, shown in the previous diagram.



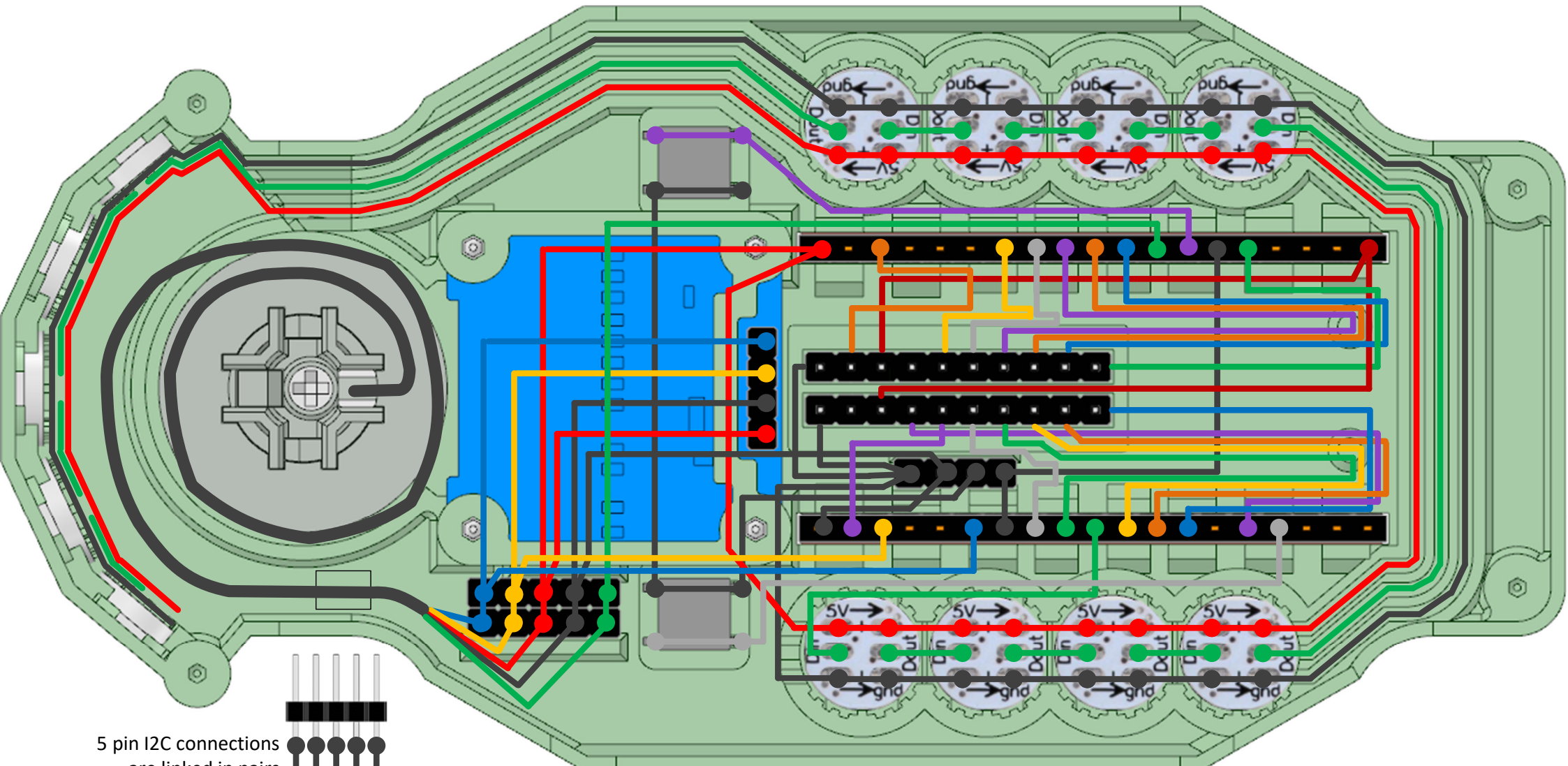
# HexBot 2 Micro Plate Wiring (viewed from below)


**Note** that the wiring for the centre floating 20 pin connector are longer than shown in some cases, and all are looped back towards the rear of the robot. This gives the floating connector scope for movement, and makes it much easier to insert this pin connector into the base plate sockets during final assembly. See photos to follow.



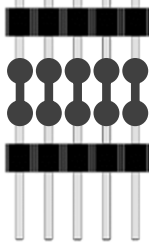5 pin I2C connections are linked in pairs before gluing in



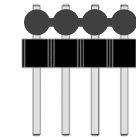20 pin floating pin strip viewed from above




GND pins are linked together before gluing in




## Wiring Sequence


01 Start with the body plate

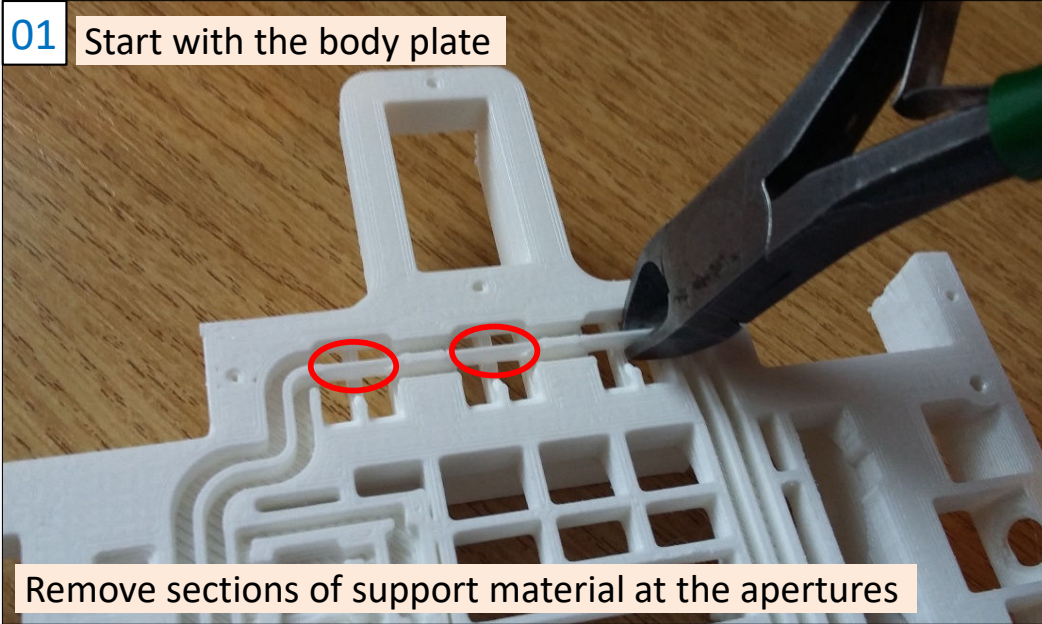

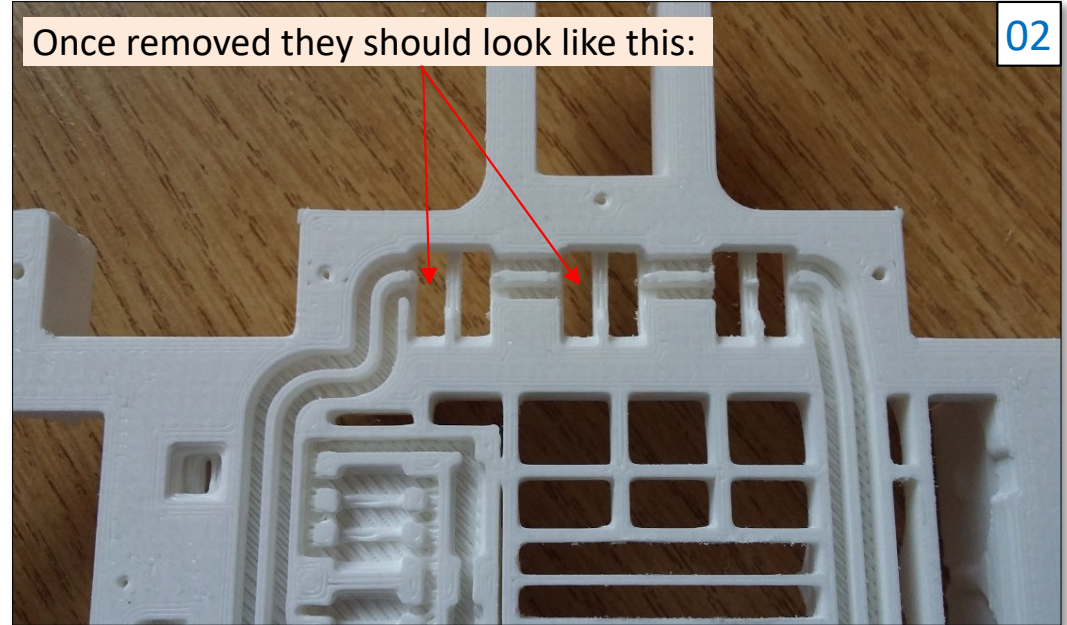
02 Once removed they should look like this:



03 Refer to the 3D Parts document




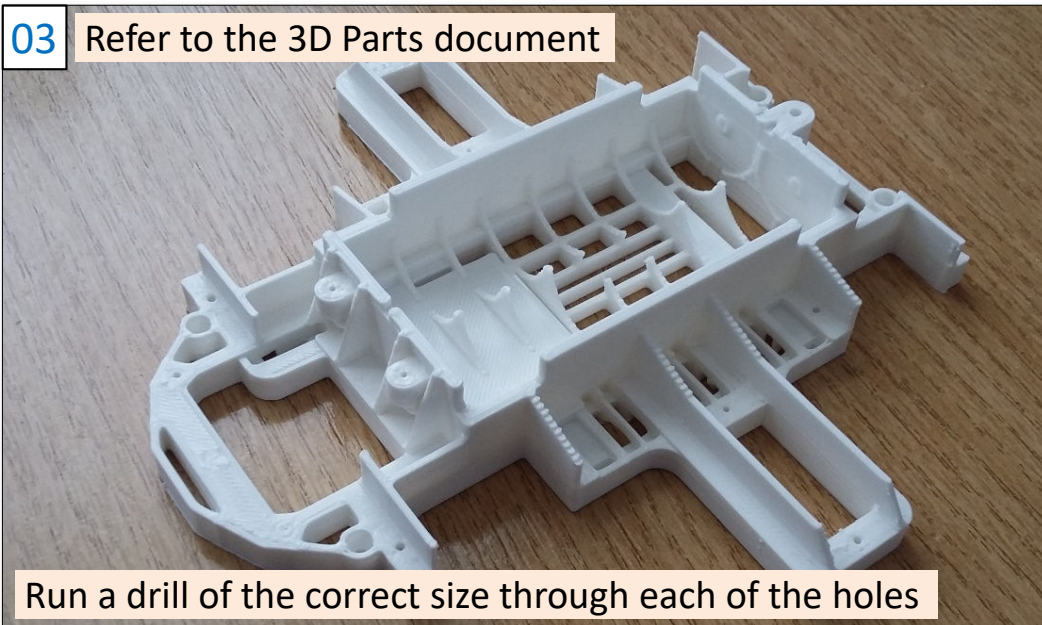


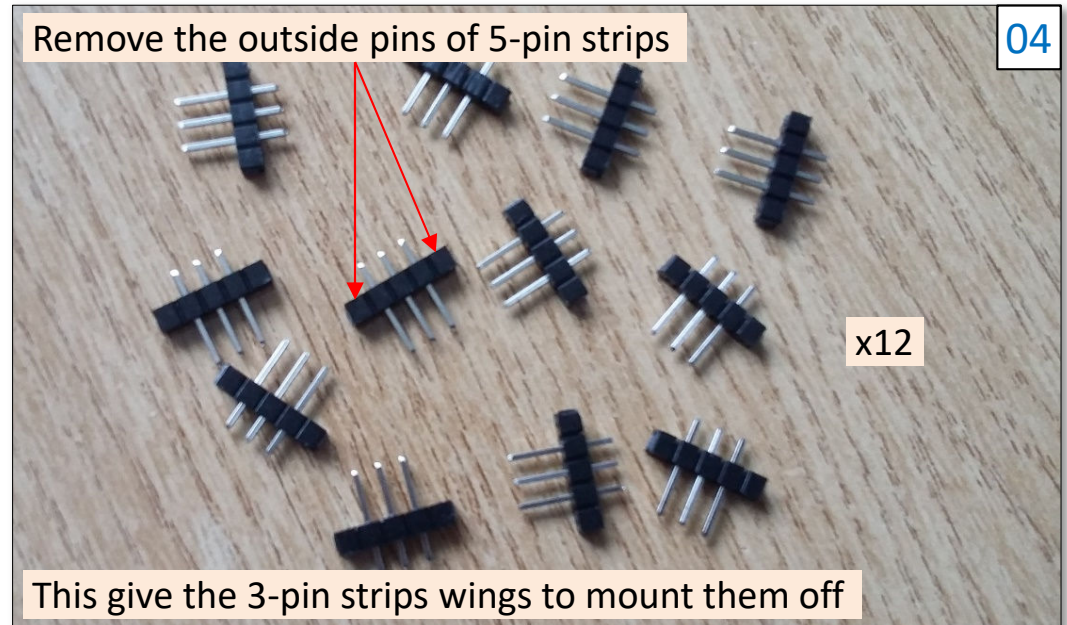04 Remove the outside pins of 5-pin strips





# Wiring Sequence

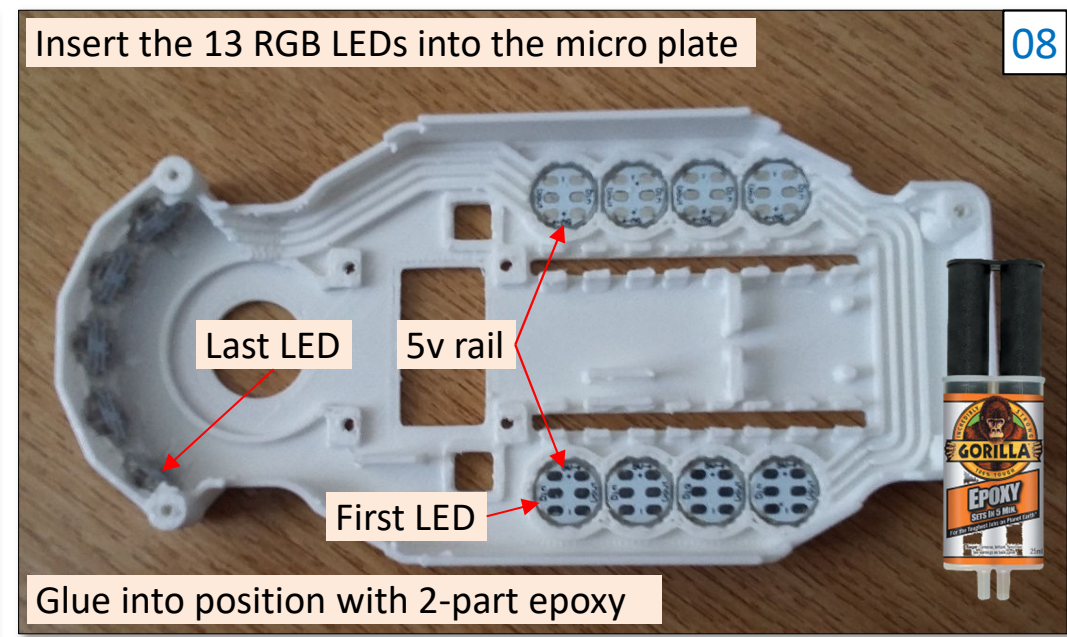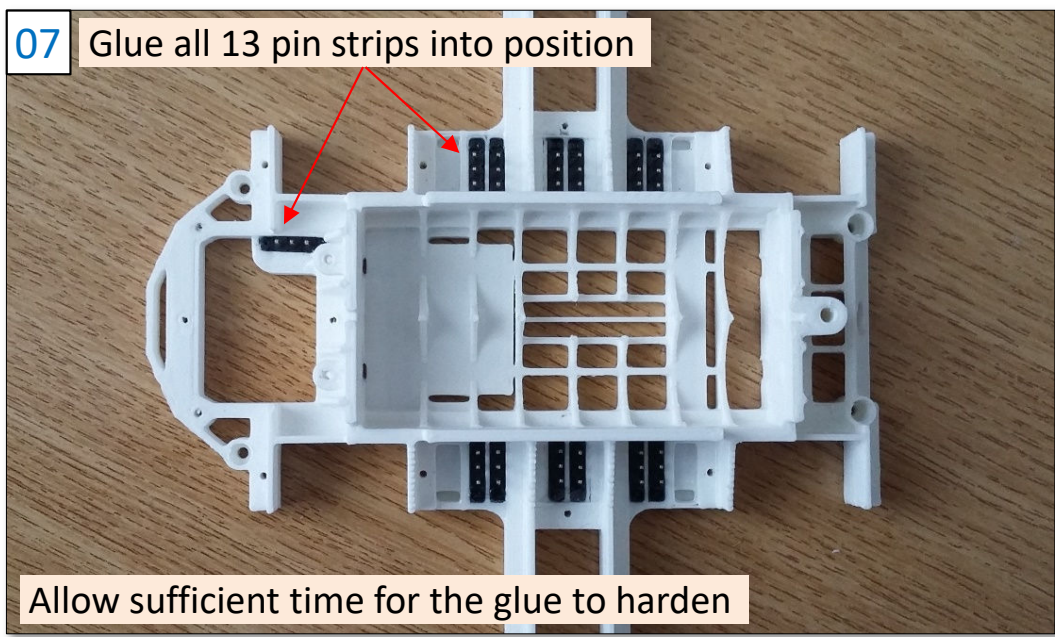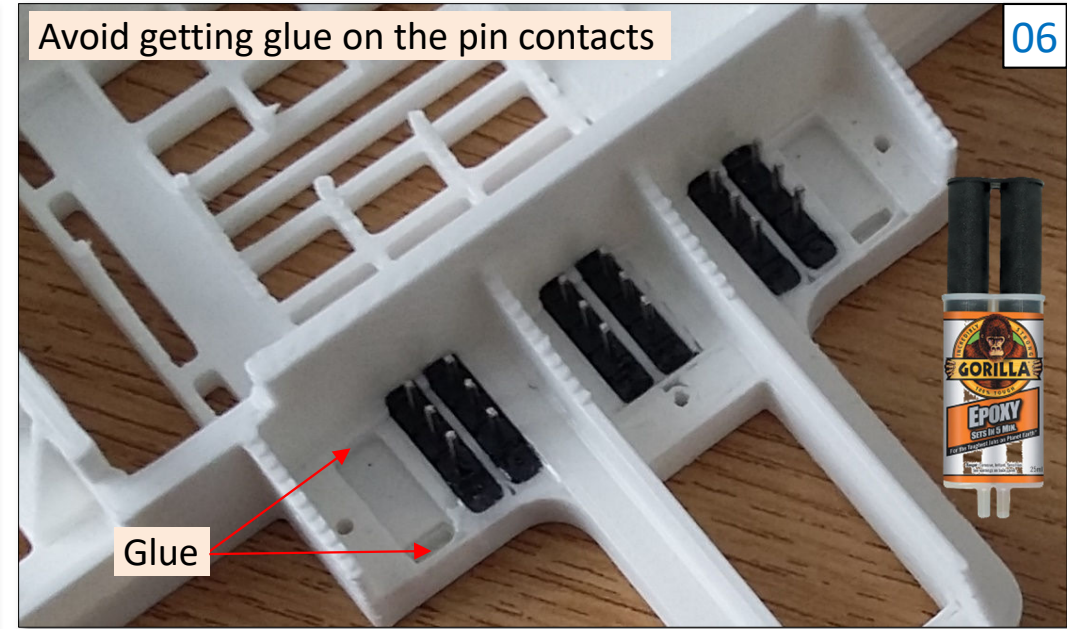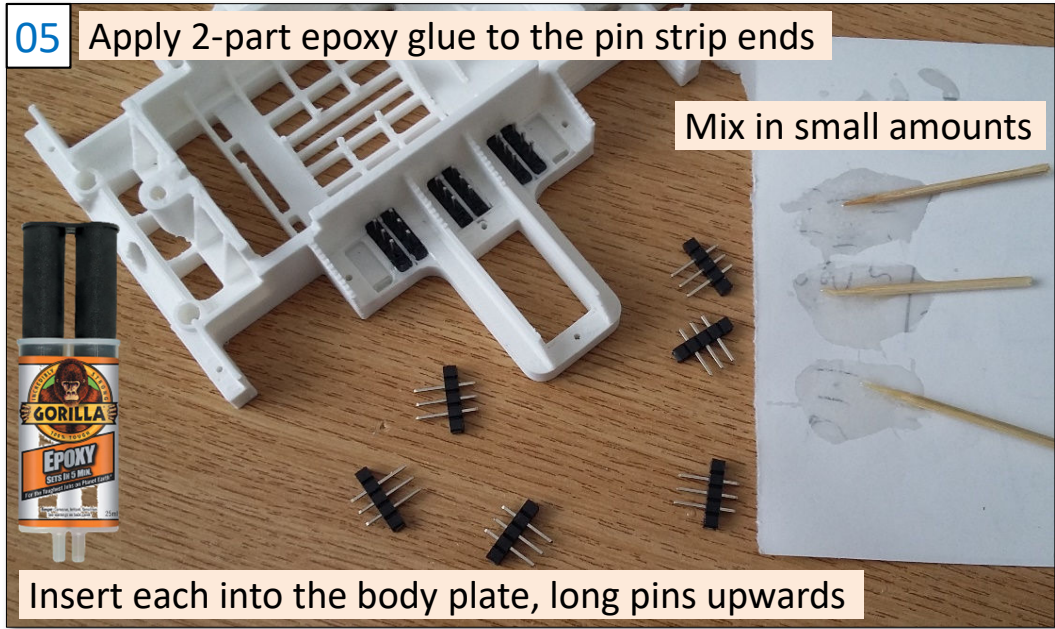




# Wiring Sequence


09 Apply two drops of glue to each LED




10 Do the same with the front LEDs

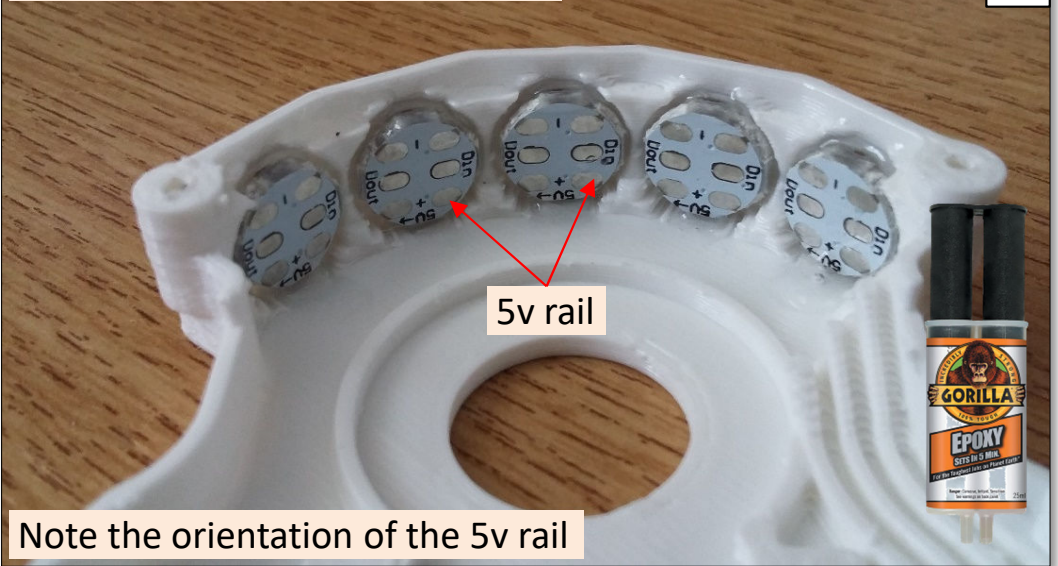

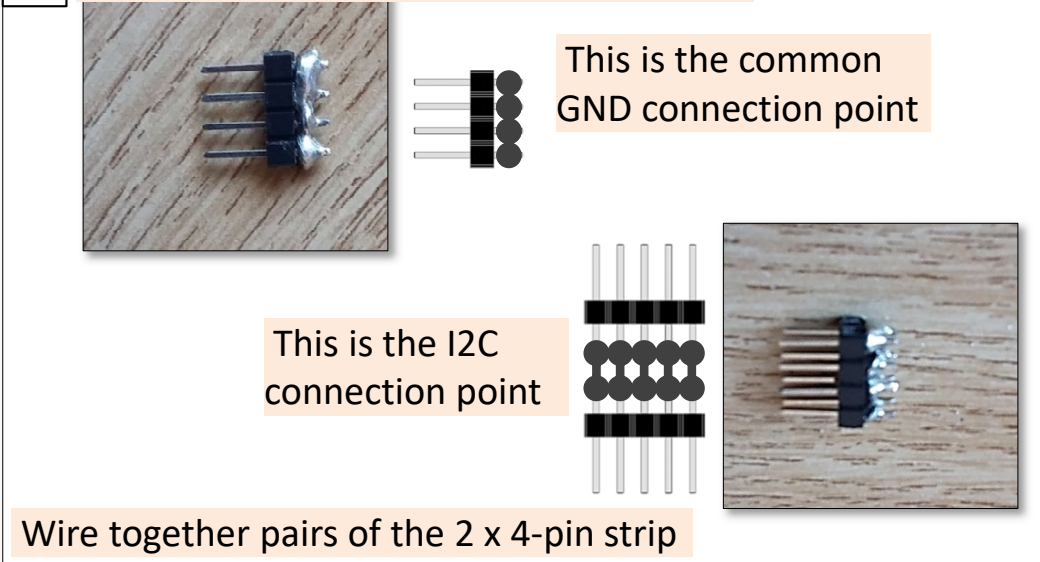11 Wire together the pins of the 4-pin strip



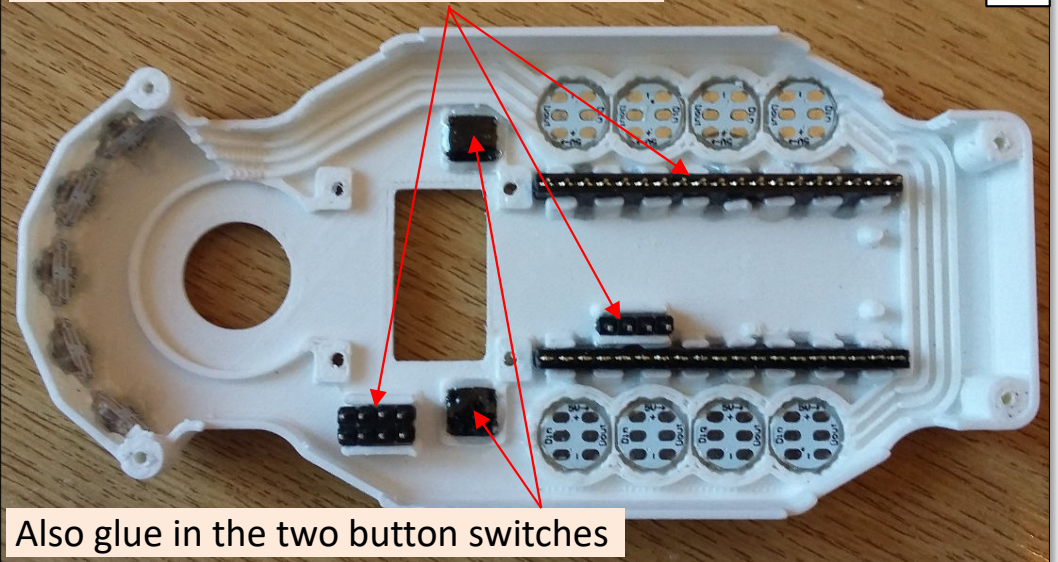
12 Glue the pin strips into the micro plate






# Wiring Sequence

13 Trial fit the battery connections

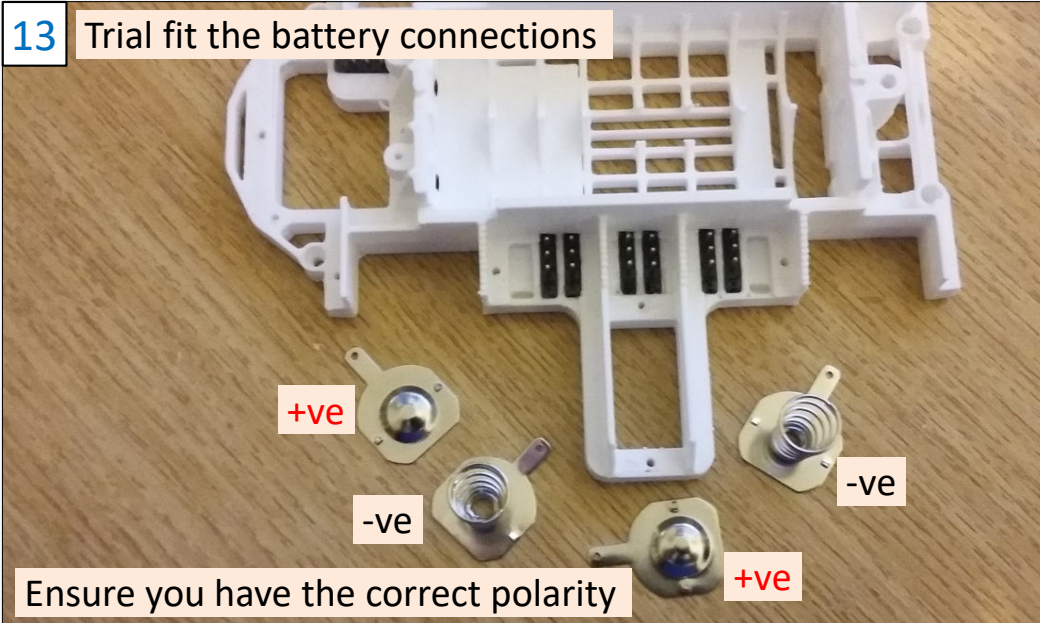


Ensure you have the correct polarity

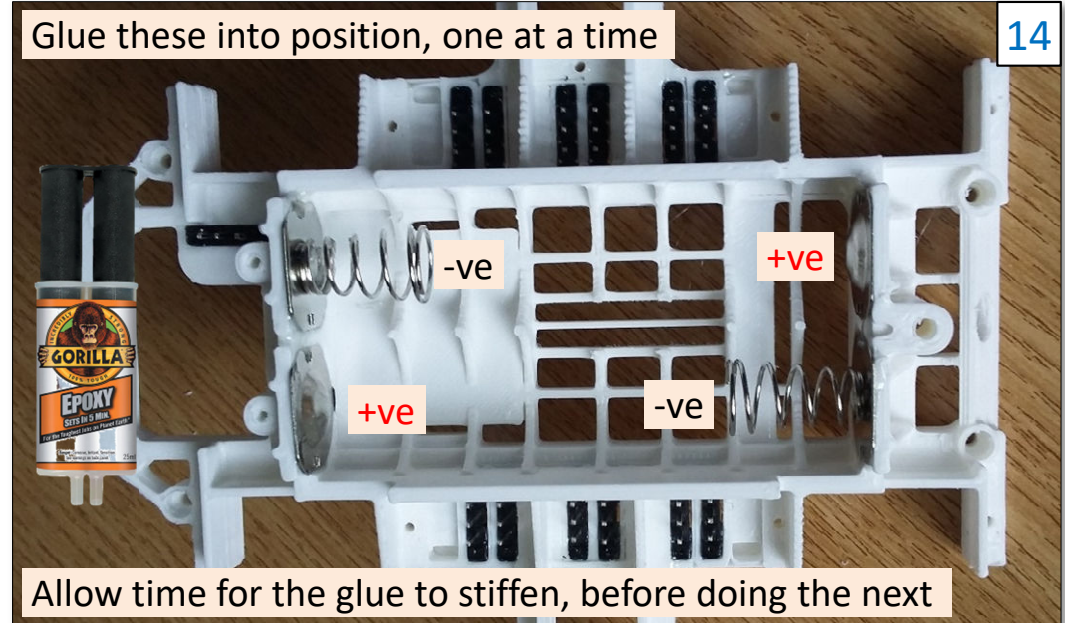14 Glue these into position, one at a time




Allow time for the glue to stiffen, before doing the next

15 Now glue in the 6 x 1N4006 diodes

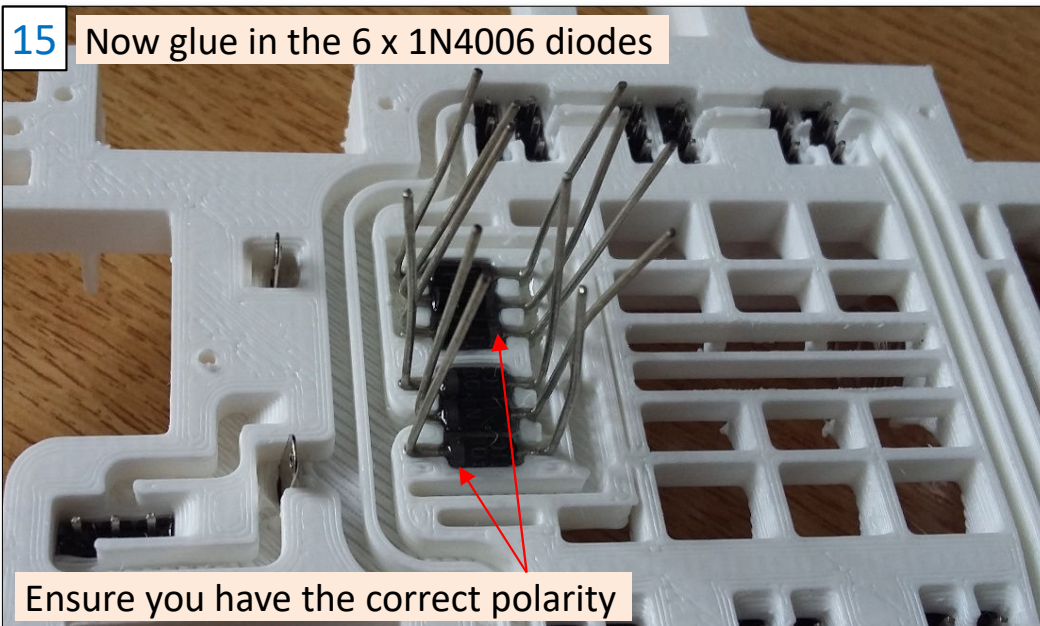

Ensure you have the correct polarity

16 Mount the display in the micro plate

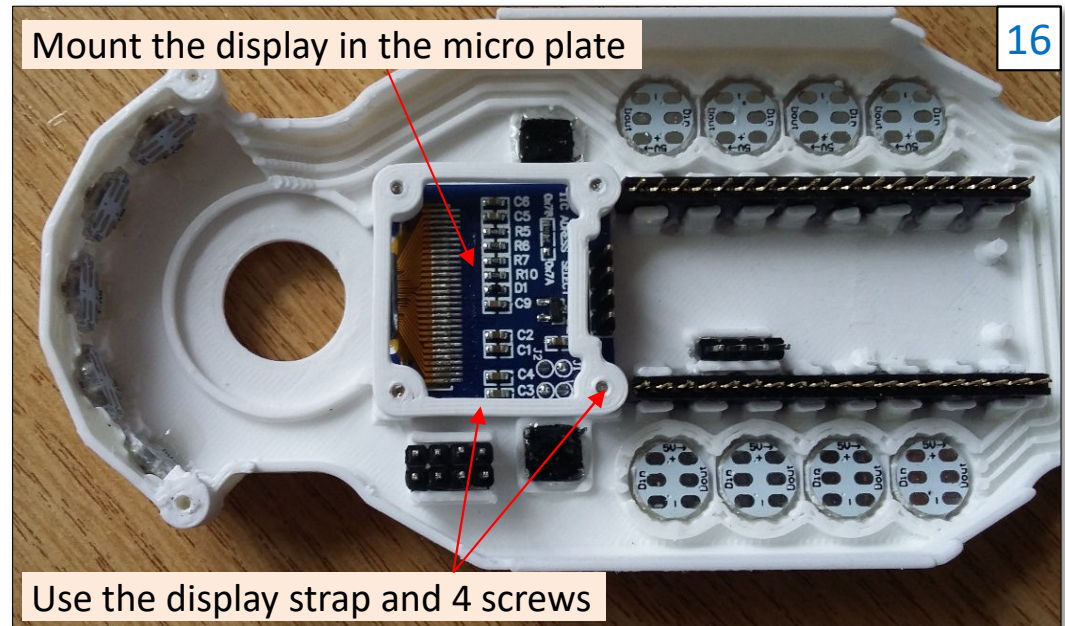


Use the display strap and 4 screws




## Wiring Sequence


17 Glue in the two resistors

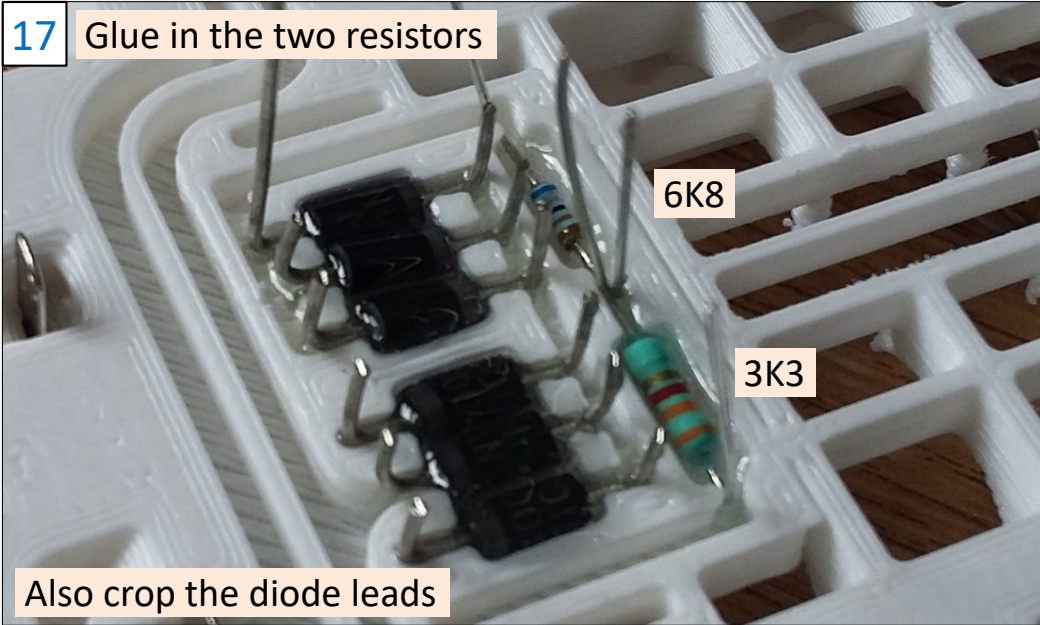

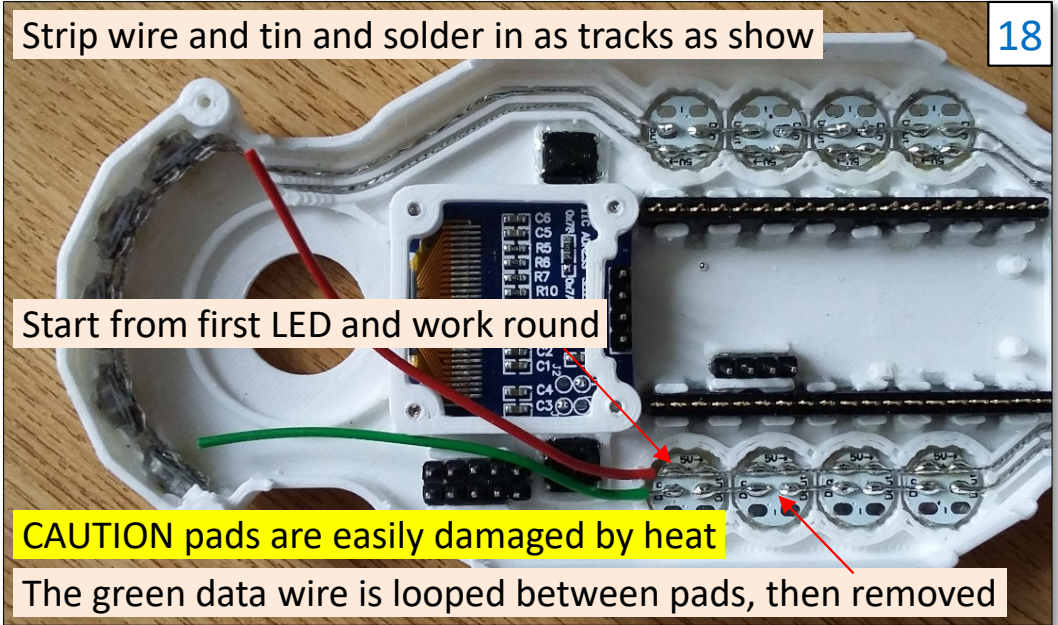
18 Strip wire and tin and solder in as tracks as show



19 Now solder in power wires

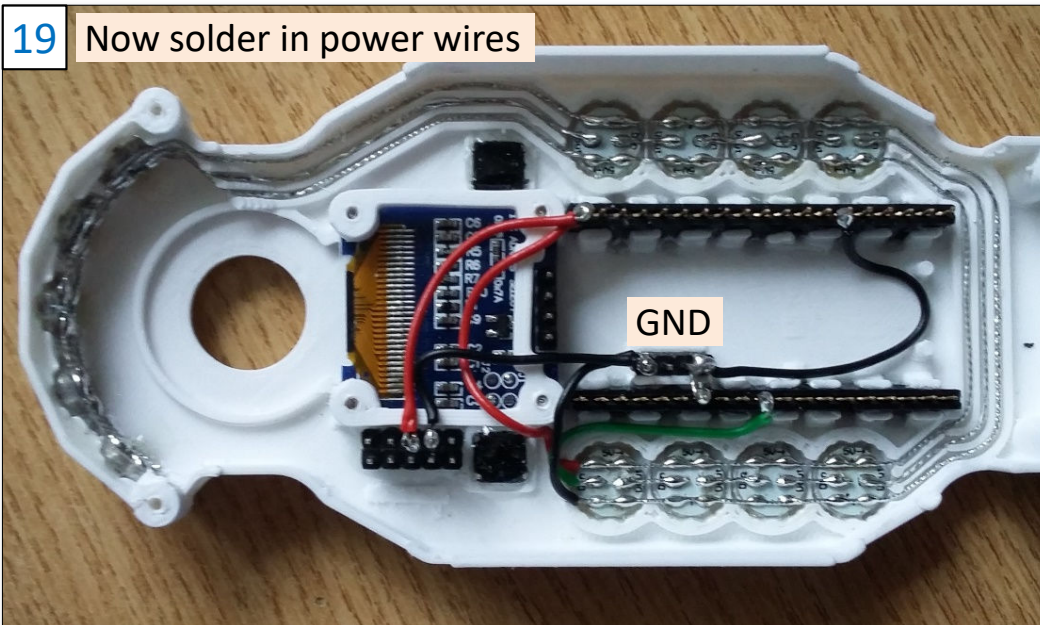

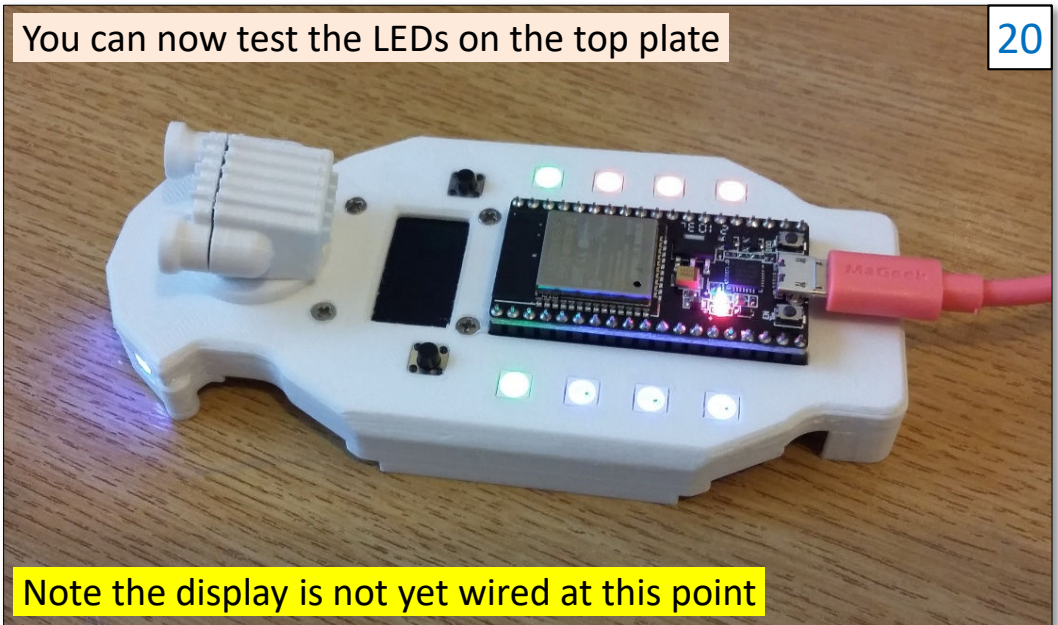
20 You can now test the LEDs on the top plate





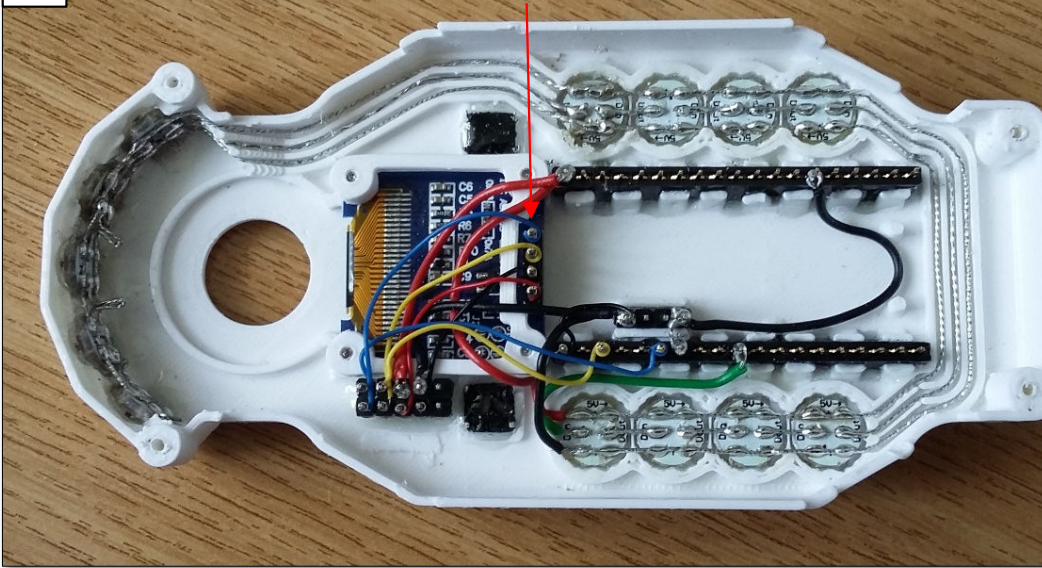
## Wiring Sequence


21 Now wire wrap the display I2C interface



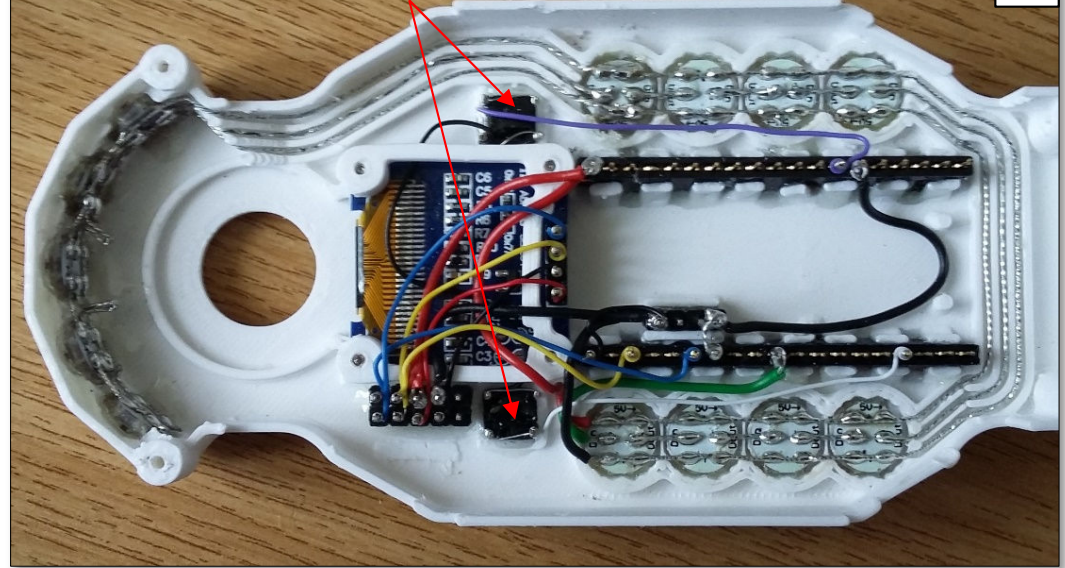
22 Next wire wrap the push two button switches



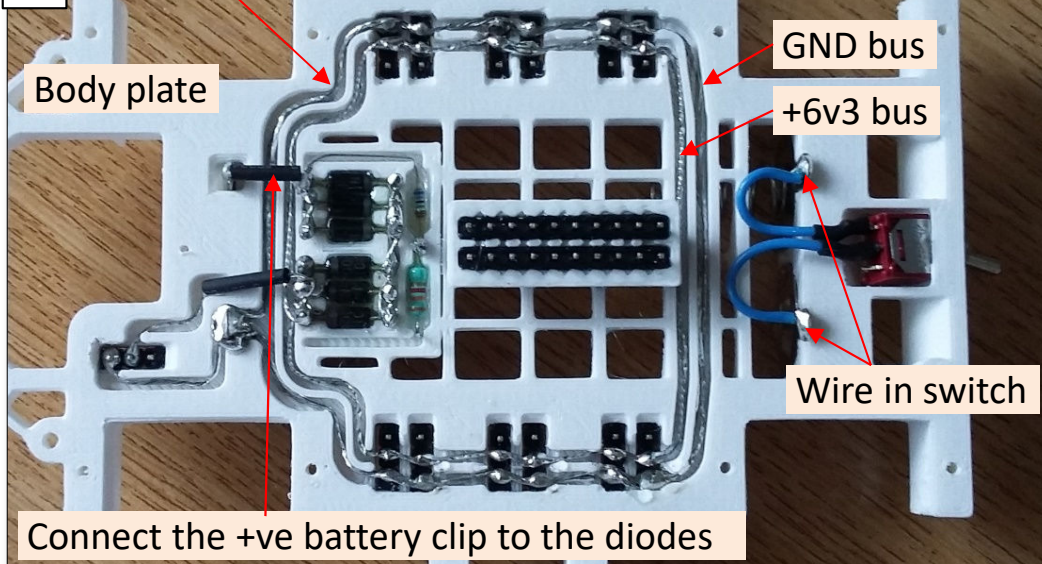23 Use tinned wire to form a servo power bus loop




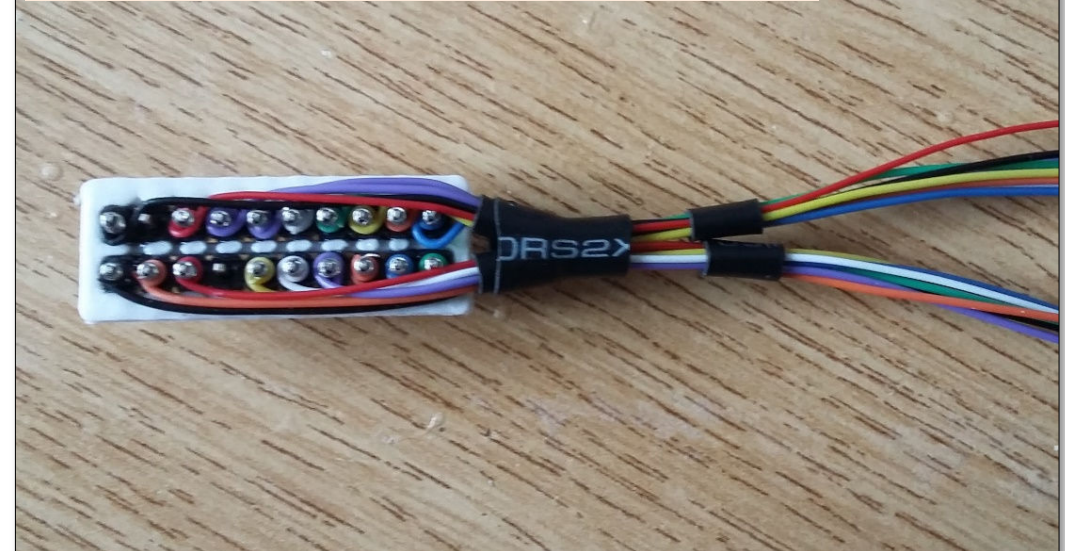24 Wire up the control harness described overleaf






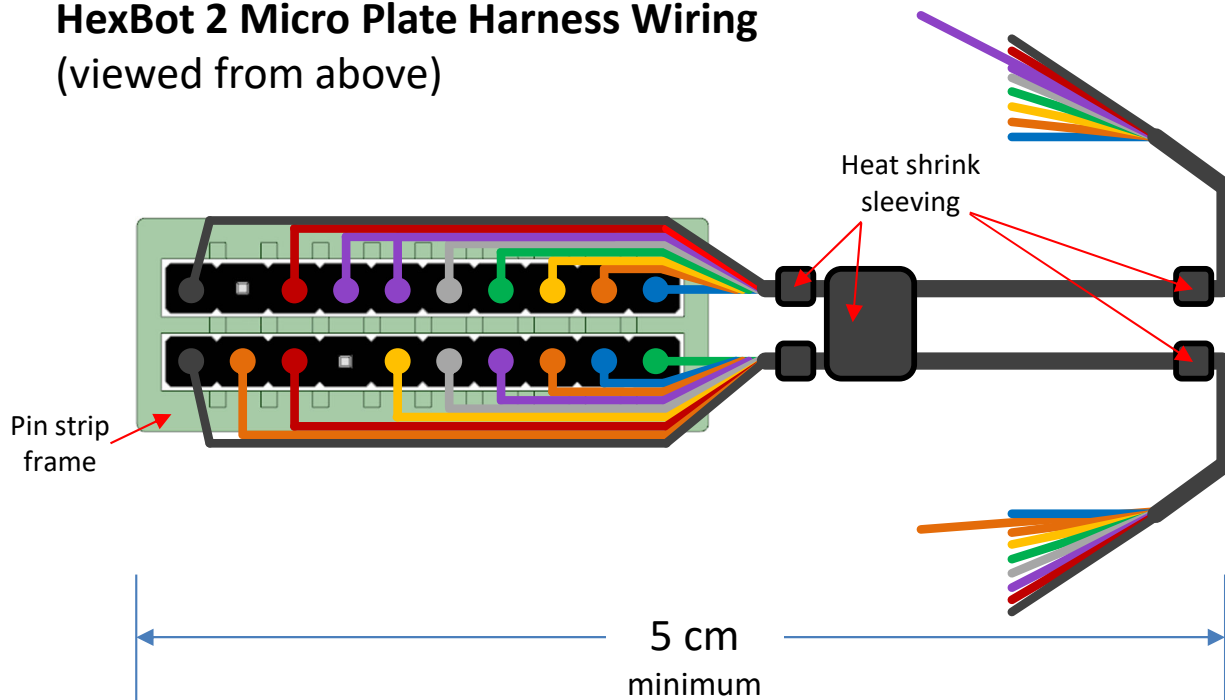
## HexBot 2 Micro Plate Harness Wiring (viewed from above)



**Note:** start with 14cm lengths of wire minimum. Make the connections to the two pin strips first; then apply heat shrink sleeving to group the wires together as shown; first as two harnesses then grouped together as one near the pin strip end. Finally wire the free ends to the ESP32 socket strip connectors, as shown in the previous image.

**Note:** The top pin strip has two purple wires and the lower strip has two orange wires. Make one of the wires longer in each case, or tie a small knot at the end, so that you can identify them when they are bundled together.

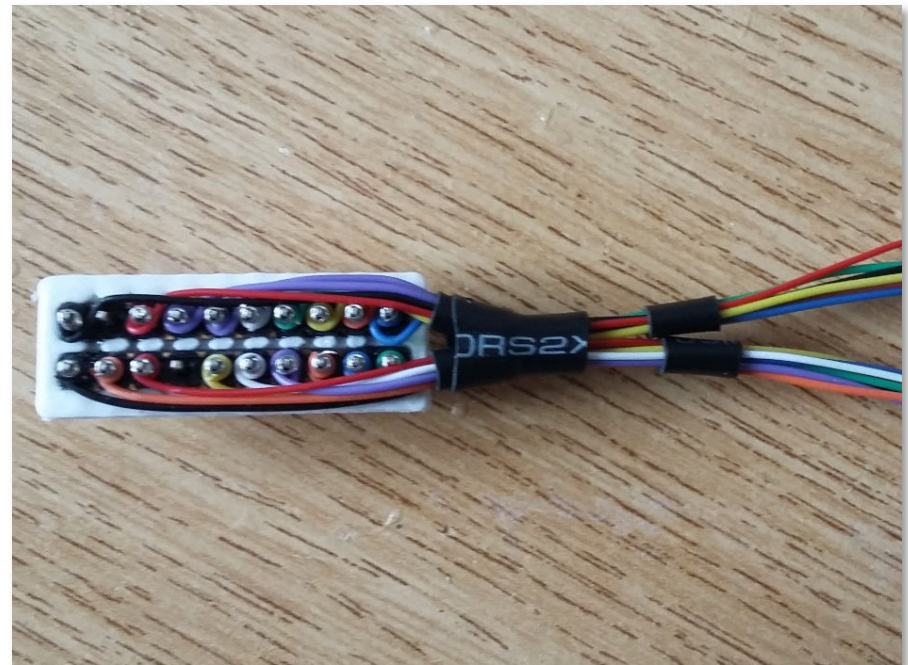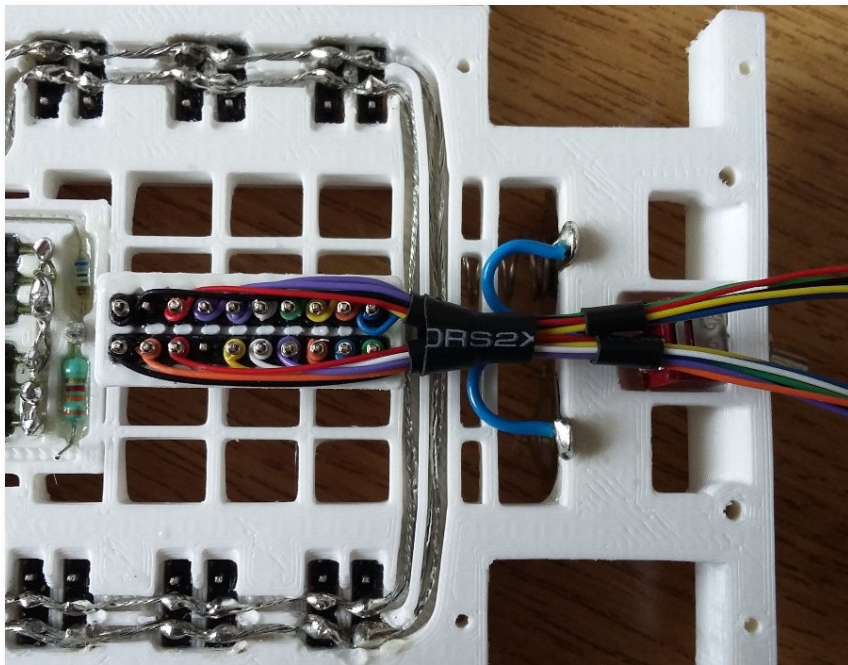
**Note:** Plugging the 20 pin floating pin strips into the sockets on the body plate will help to hold the job whilst you apply the wire wrap wire, and the heat shrink sleeving





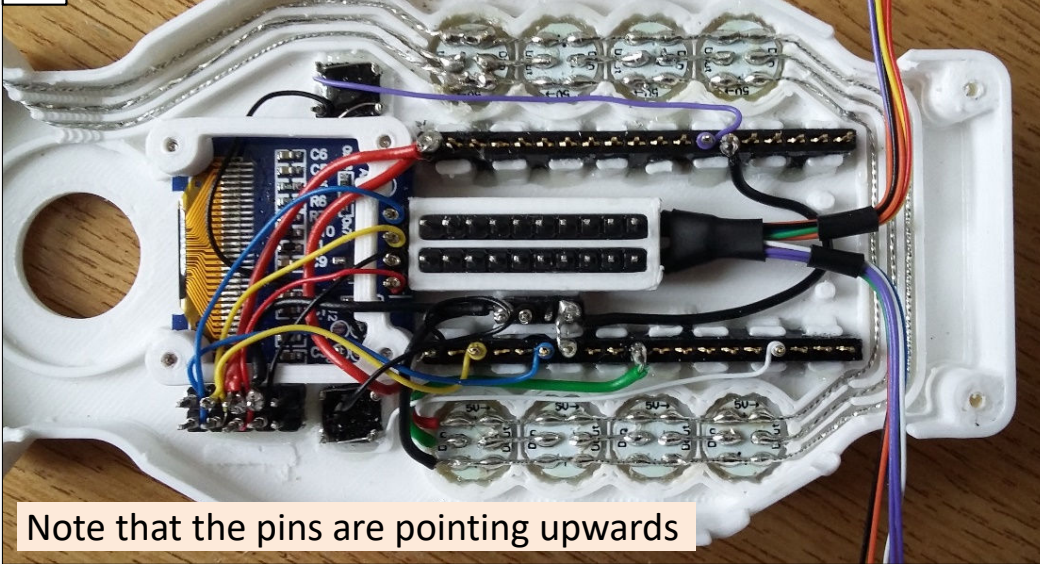
## Wiring Sequence

25 Position the harness as show within the top plate




Note that the pins are pointing upwards

26 Wire wrap one side of the harness

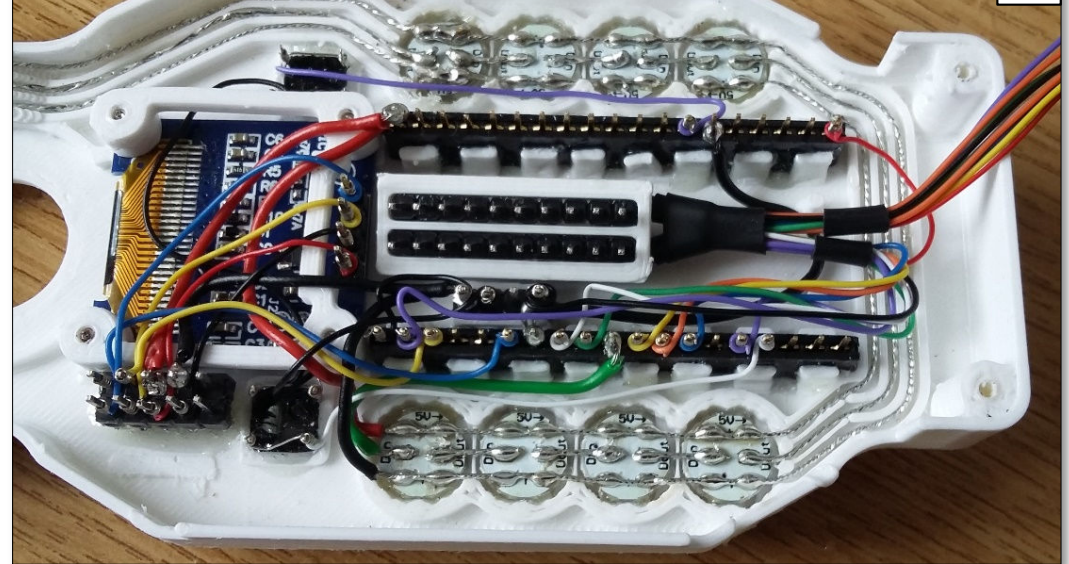


27

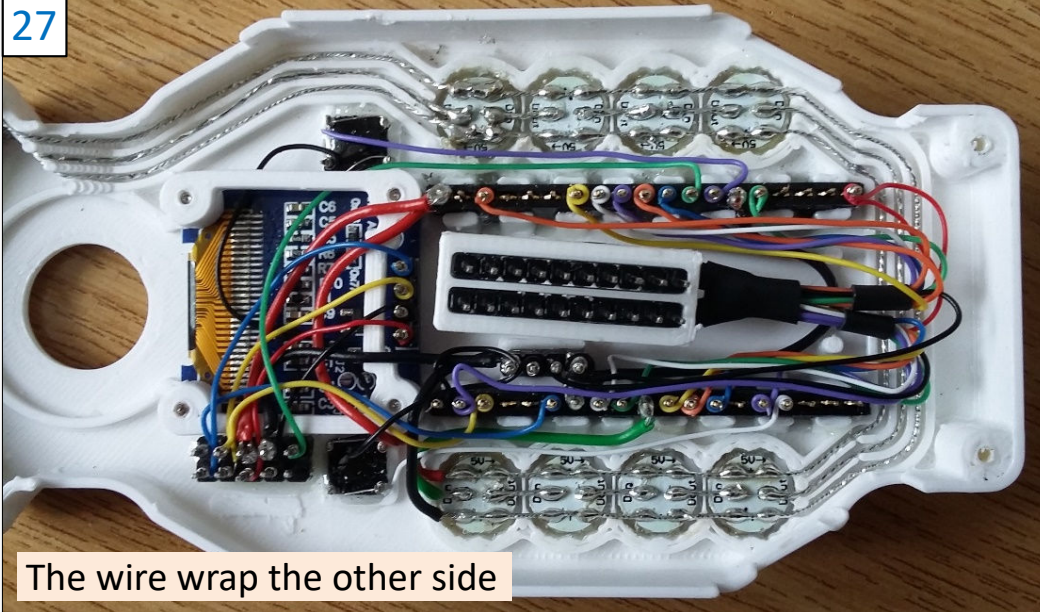

The wire wrap the other side

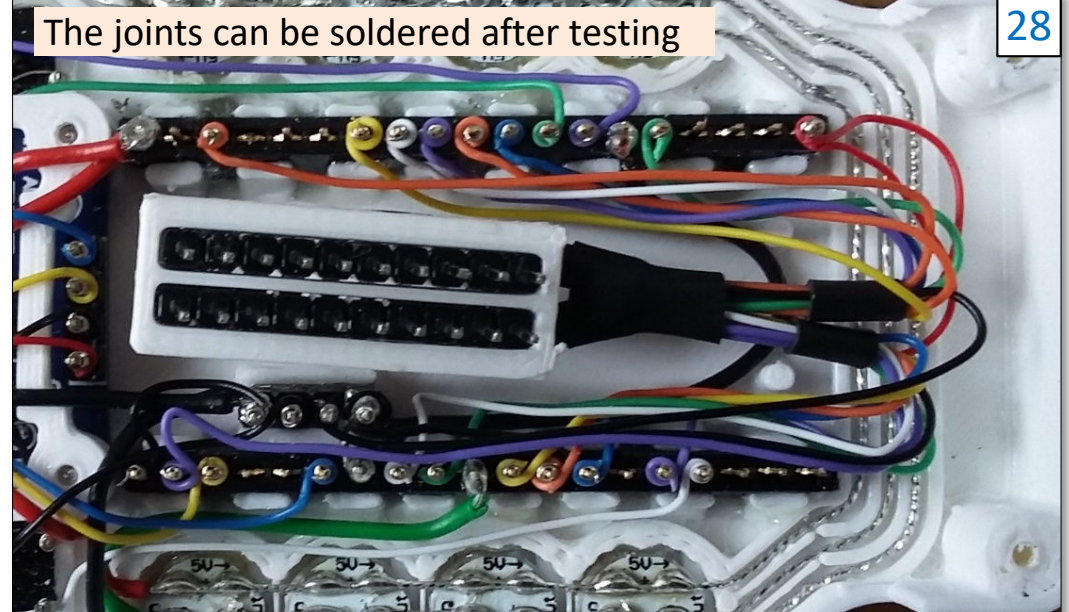28 The joints can be soldered after testing





28





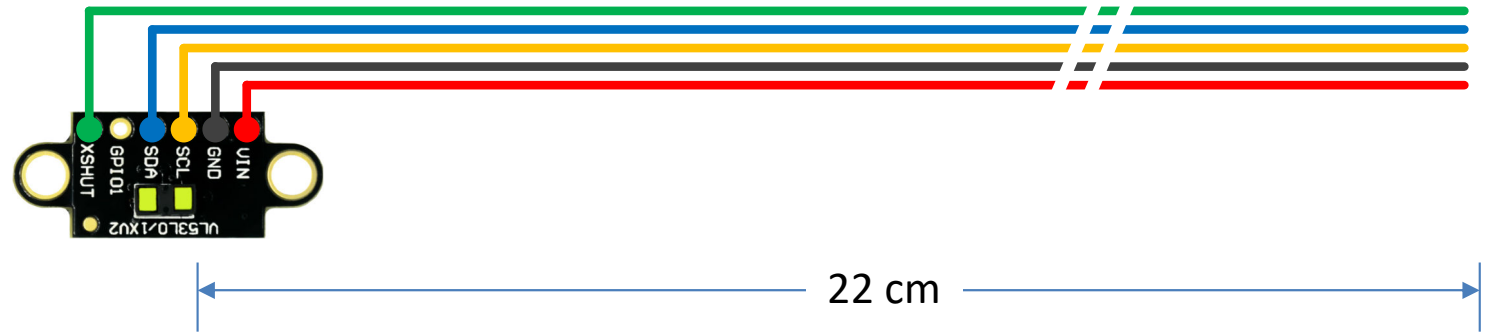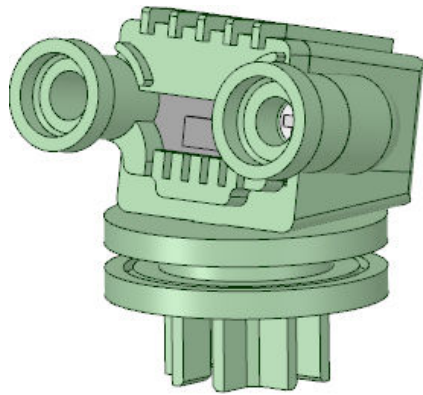
## HexBot 2 Head Wiring

**Note:** start with 22cm lengths of wire minimum. Make the connections to the pins on the VL53L1X sensor first. Then feed the five wires through the neck aperture before screwing on the eye plate. Then mount the head onto the top face of the micro plate and glue the retaining disc into position from the other side, with the wiring protruding through the neck aperture.



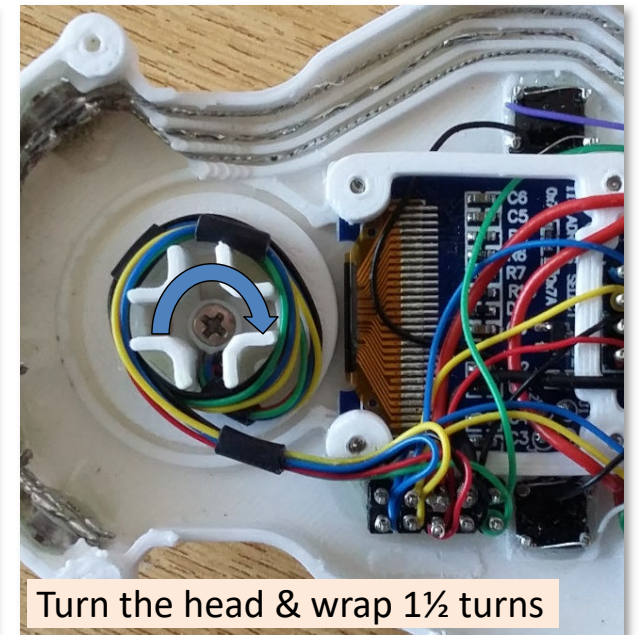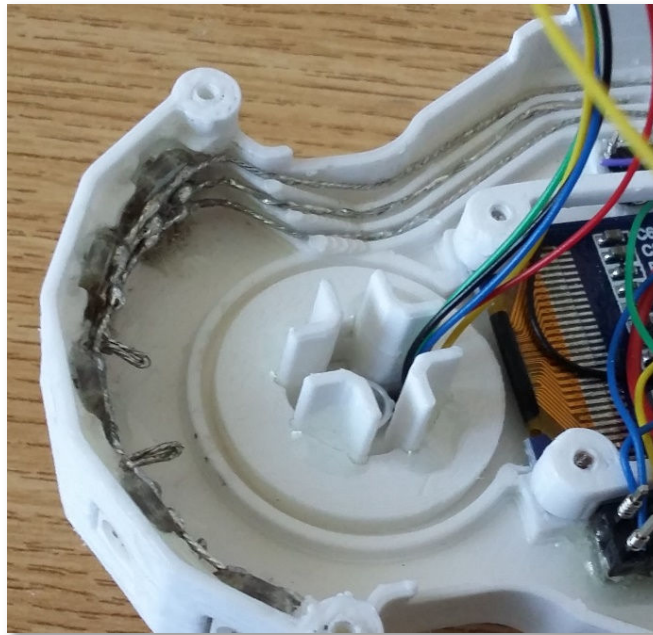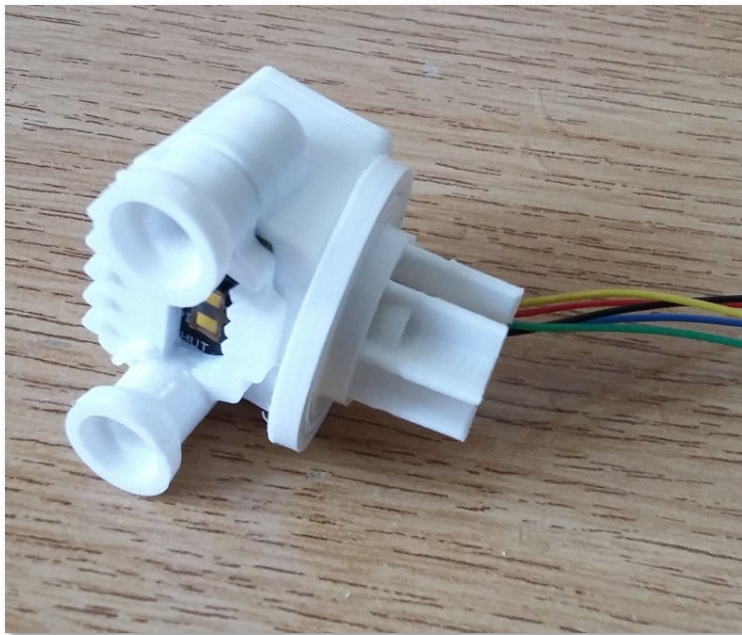
Turn the head 90° to the left, then coil the wires around the neck in an anti-clockwise direction for 1½ turns, as shown below. Then make off the wire wraps to the 4 pin I2C strip. Check that the head can be rotated from left to right without the wire coiling too tightly on the neck. The glue the wire to the vertical supporting post as a tether point.





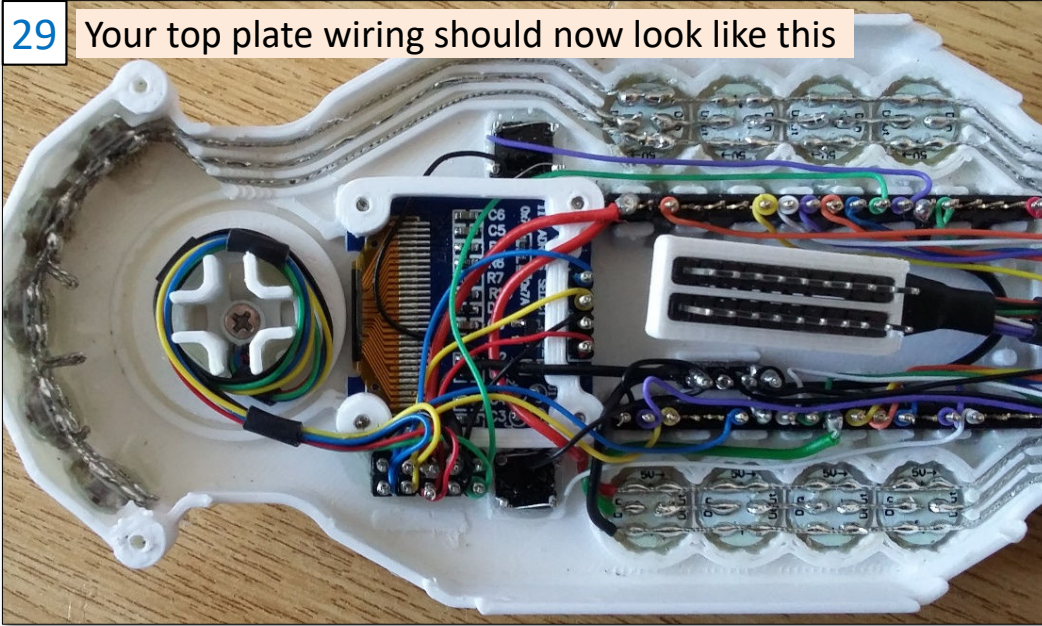
## Wiring Sequence

29 Your top plate wiring should now look like this




30

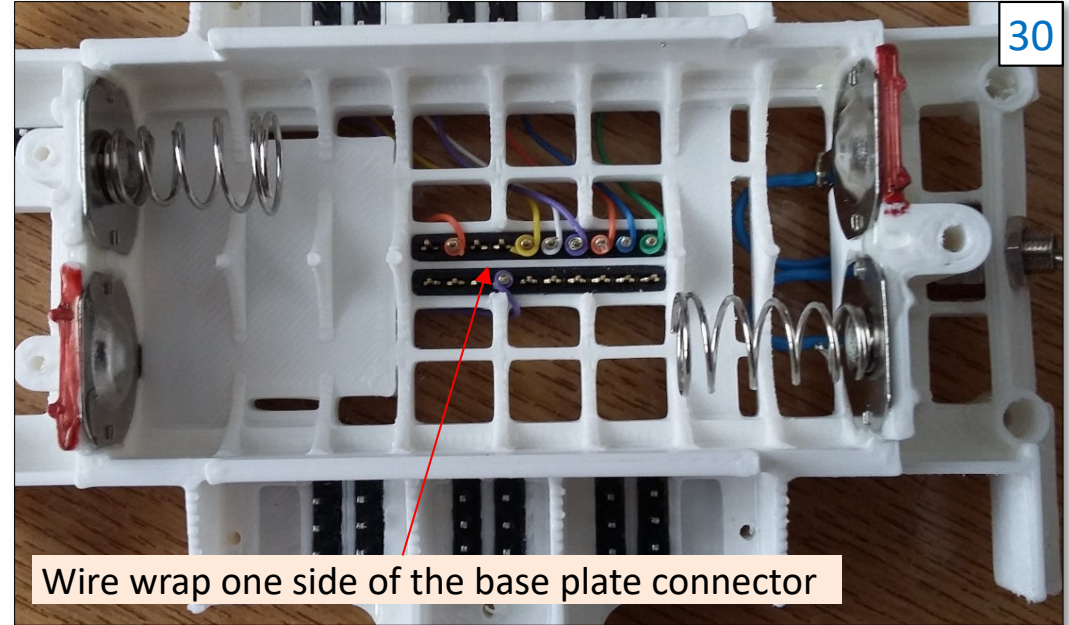

Wire wrap one side of the base plate connector


31

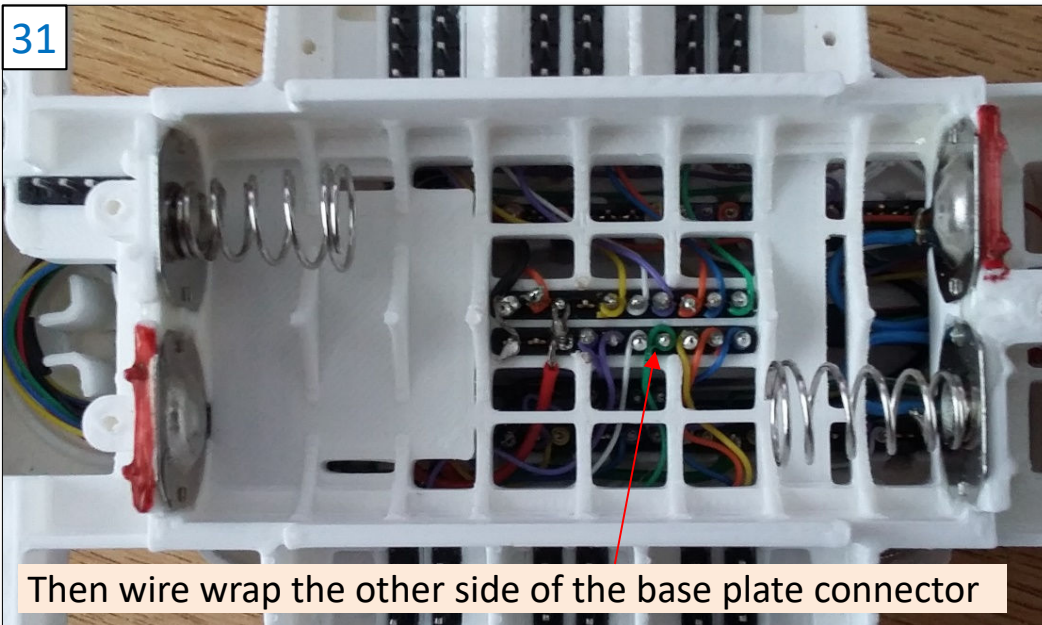

Then wire wrap the other side of the base plate connector

32

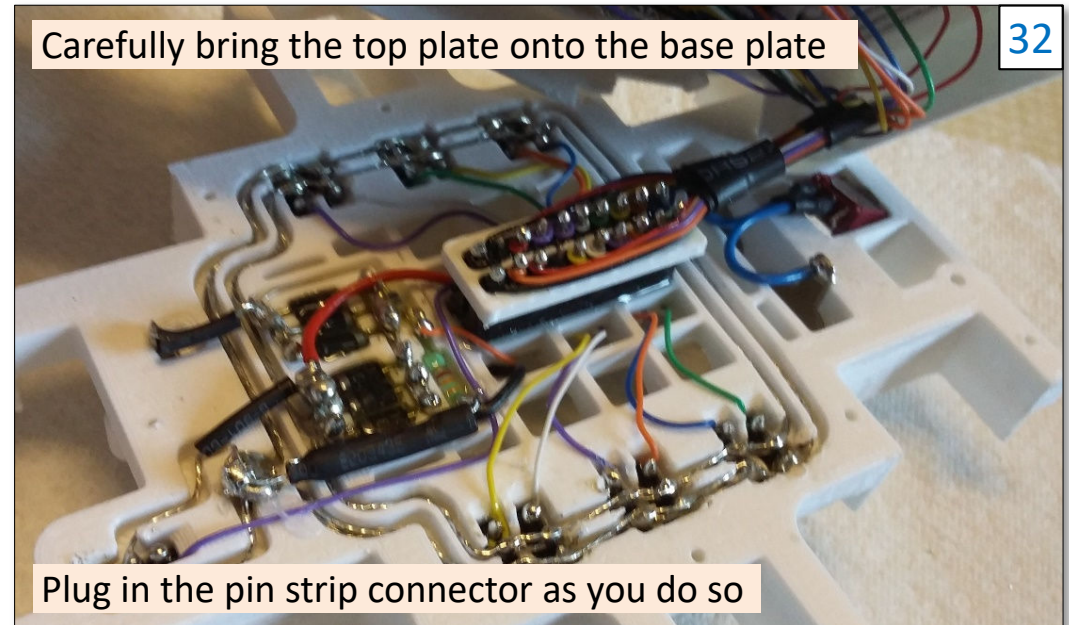Carefully bring the top plate onto the base plate




Plug in the pin strip connector as you do so



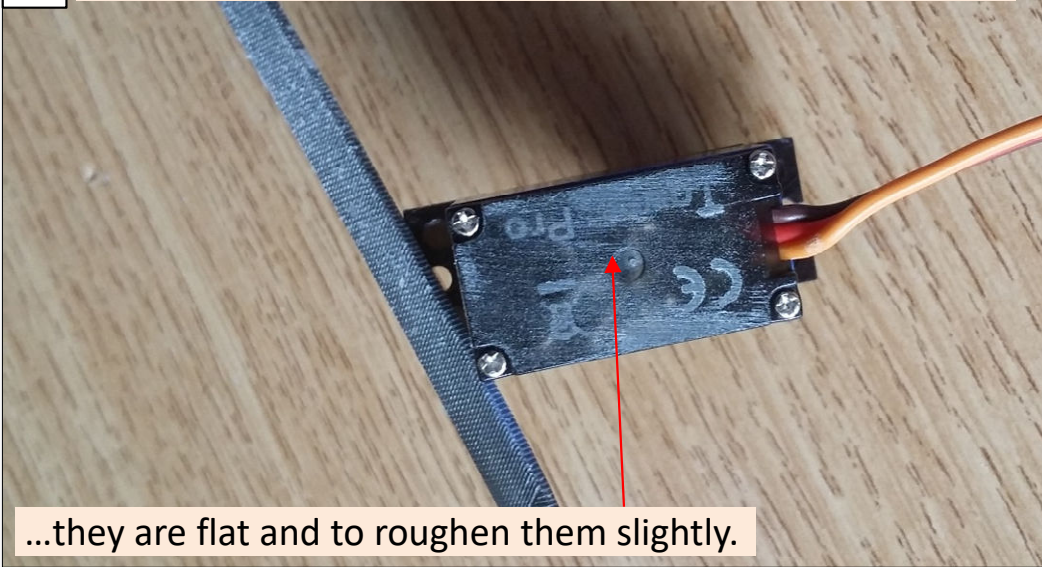
## Wiring Sequence


33 Dress the base face of the servos with a file, to ensure...



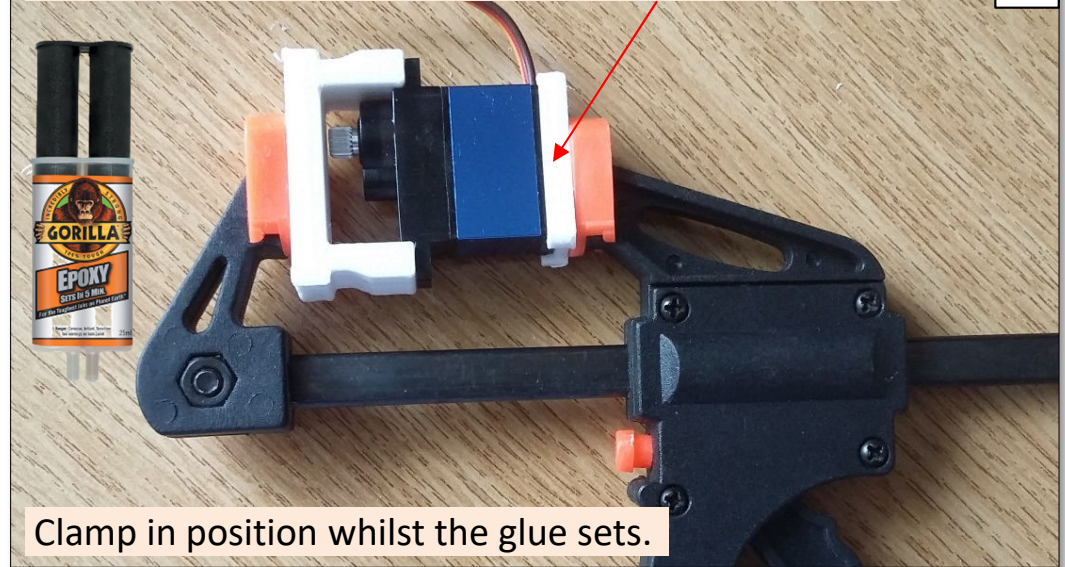
34 Glue a bearing plate onto the bottom of each servo.



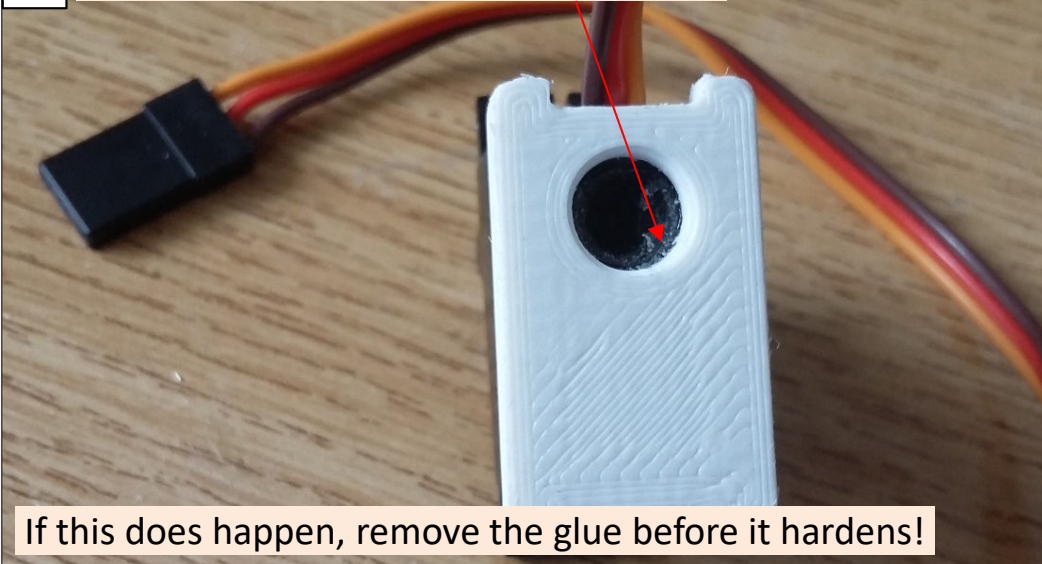35 Avoid getting glue in the bearing hole



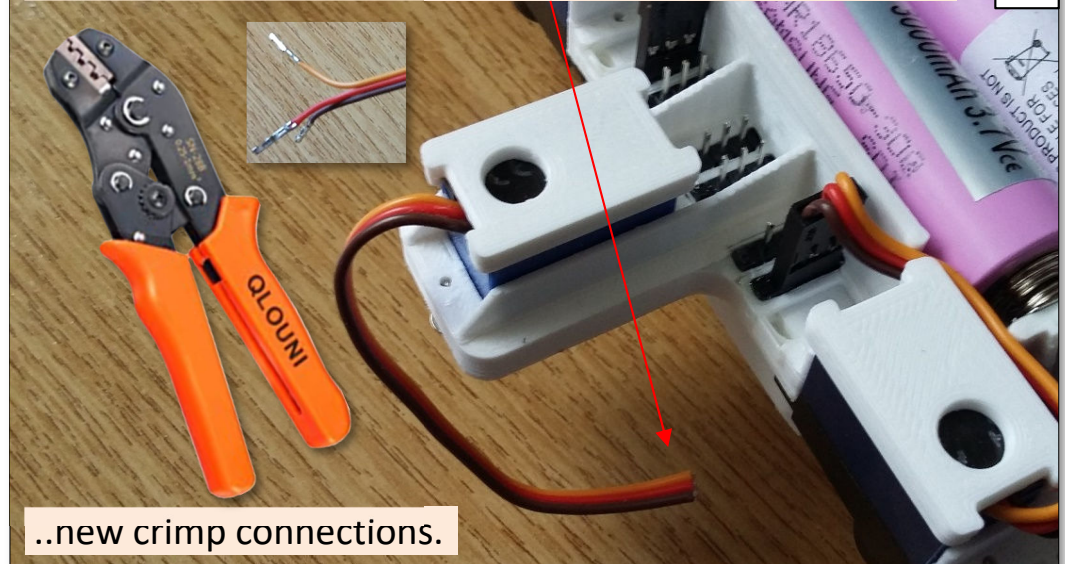
36 Cut the servo leads with sufficient length to make-off..





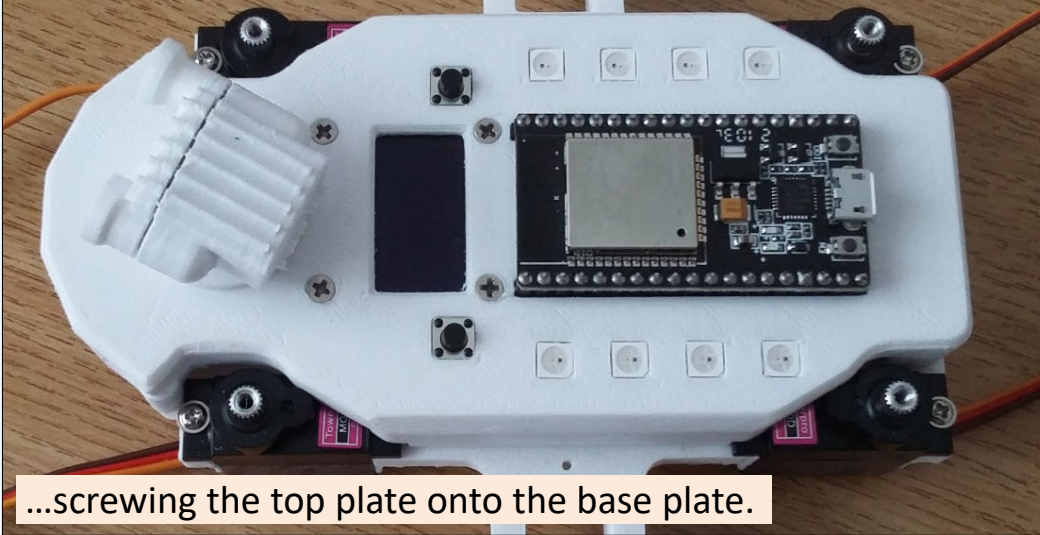
## Wiring Sequence


37 Mount the front and rear servo motors before...




38 Then mount the side servo motors.

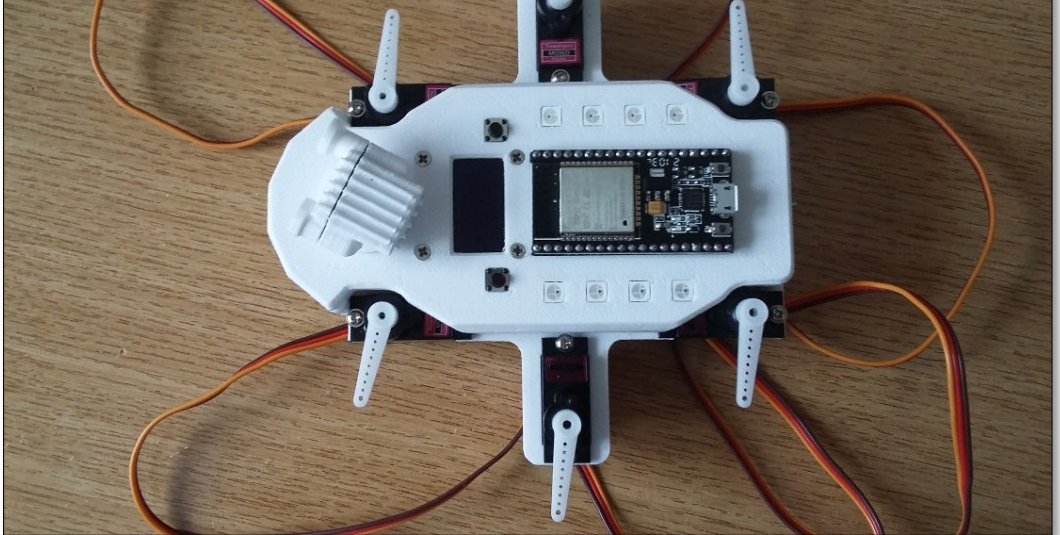

39 Next mount the head servo motor.

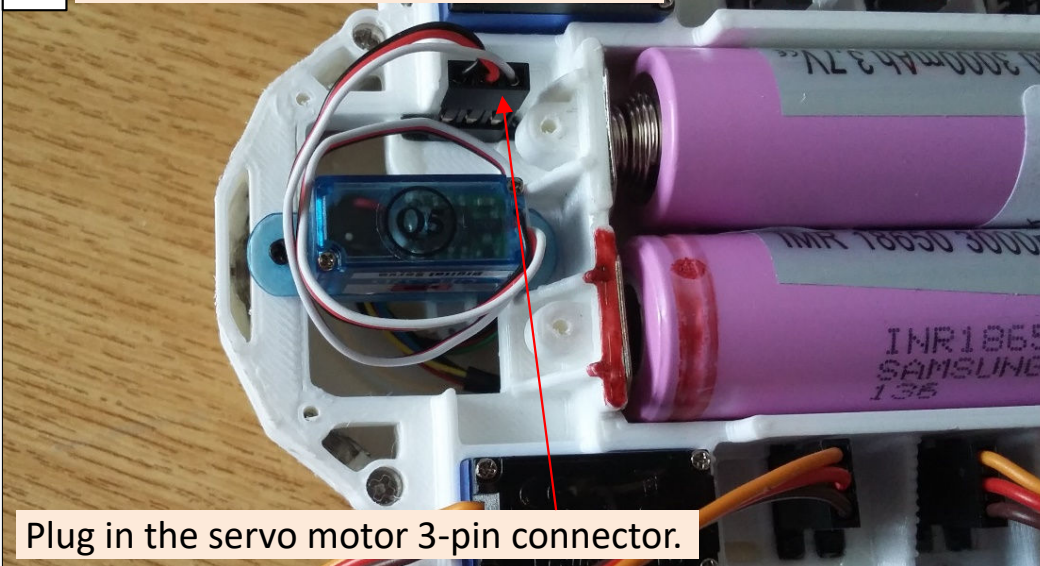


40 Then fit the chin cover.

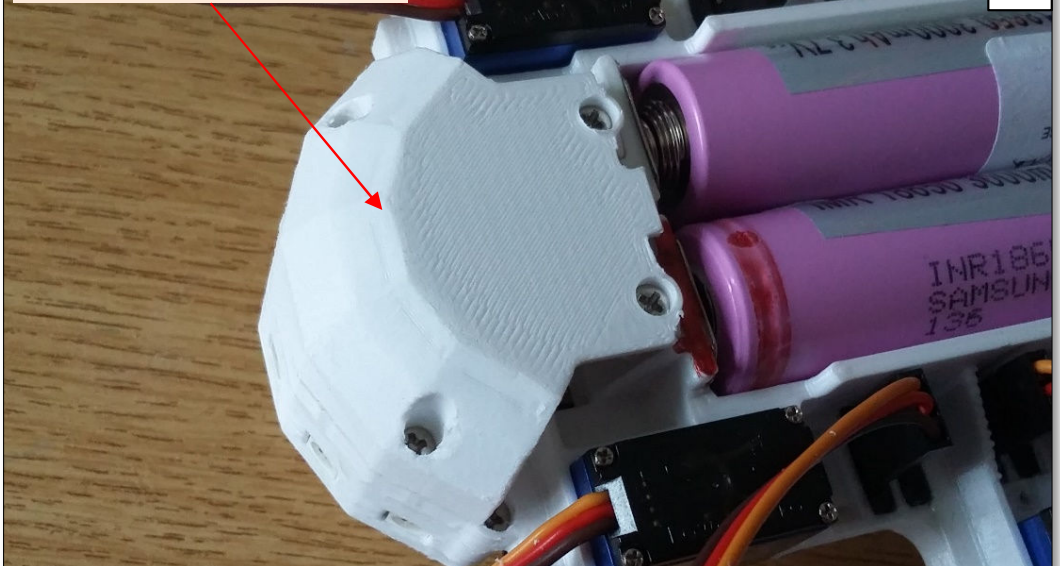


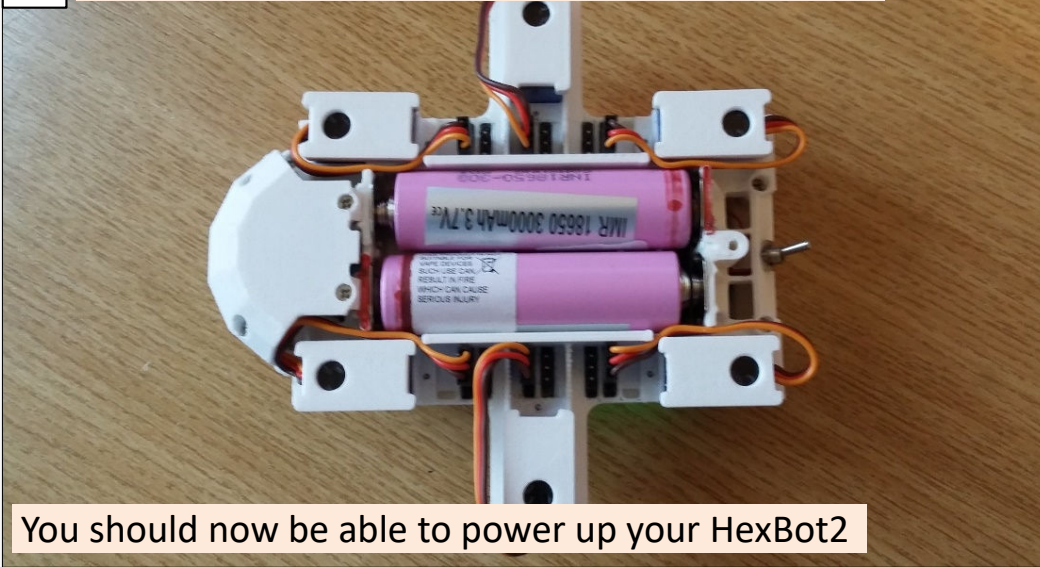
## Wiring Sequence

41 Mount the front and rear servo motors before...




You should now be able to power up your HexBot2

42 Glue the servo arms into the lever plates




Avoid getting glue on the servo splines

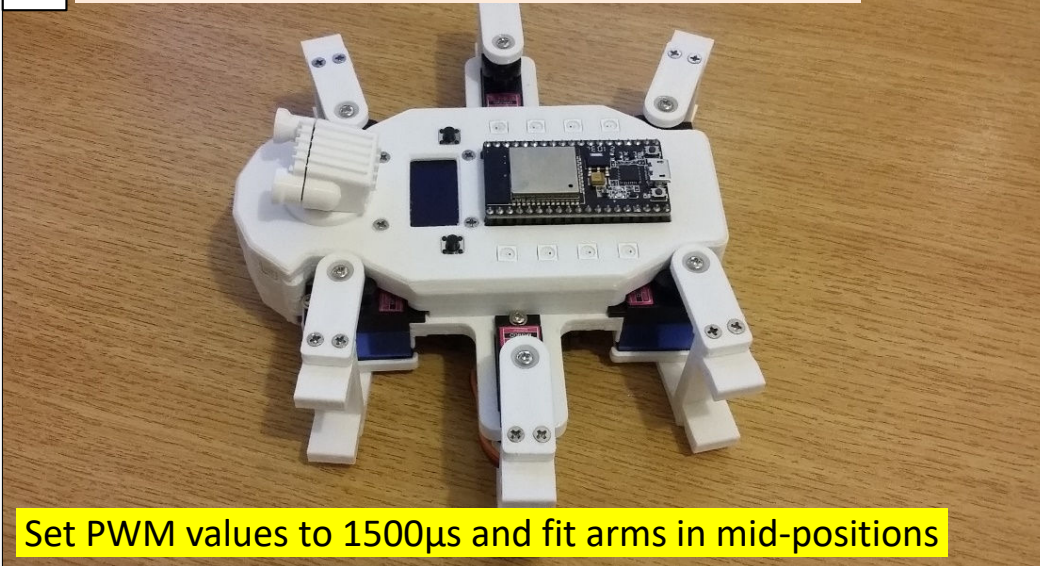43 Attach the lever and link plates to the servos



Set PWM values to 1500 $\mu$ s and fit arms in mid-positions


44 Viewed from below

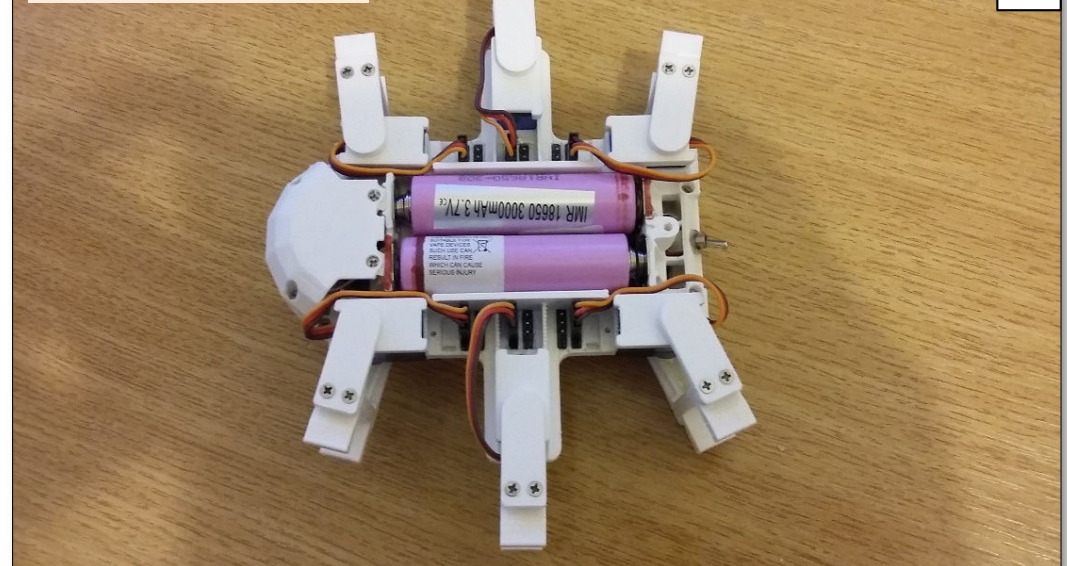



## Wiring Sequence


45

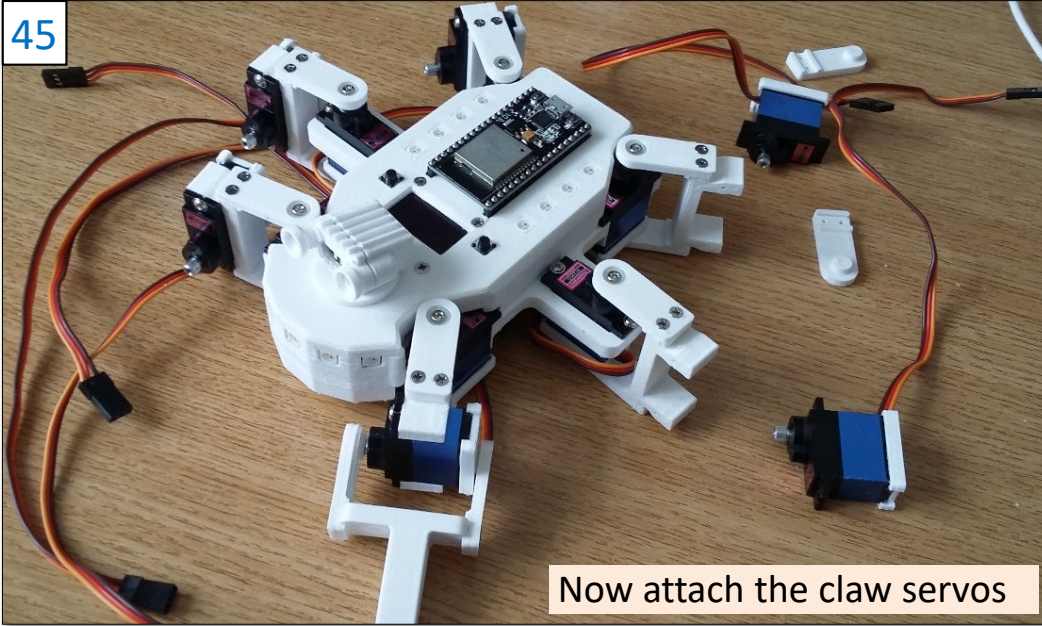


Now attach the claw servos

Loop the servo wires so they can move freely

46

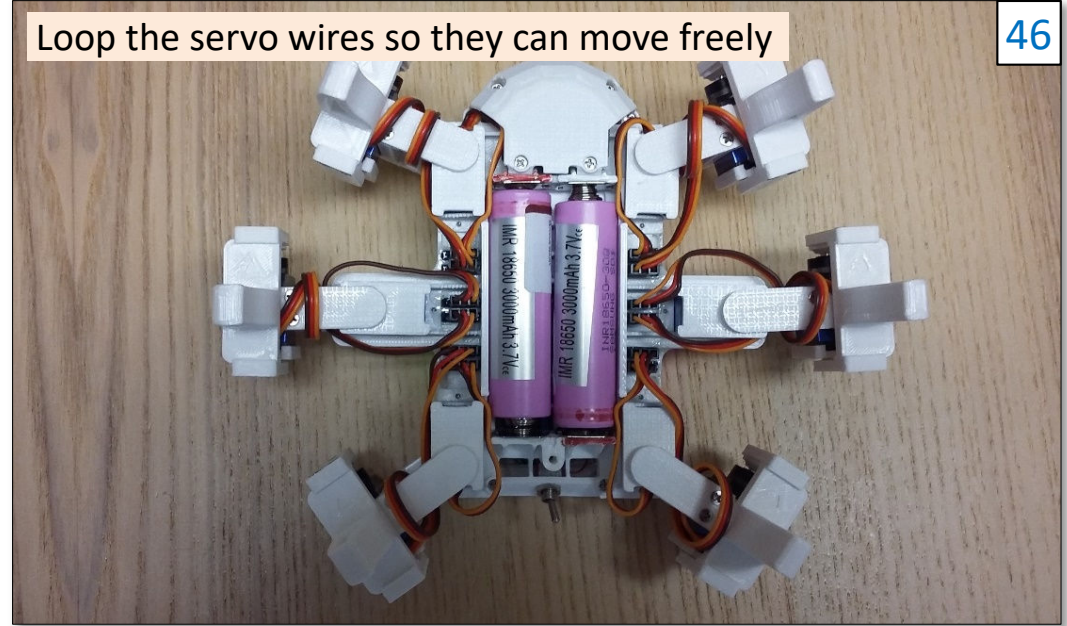


47

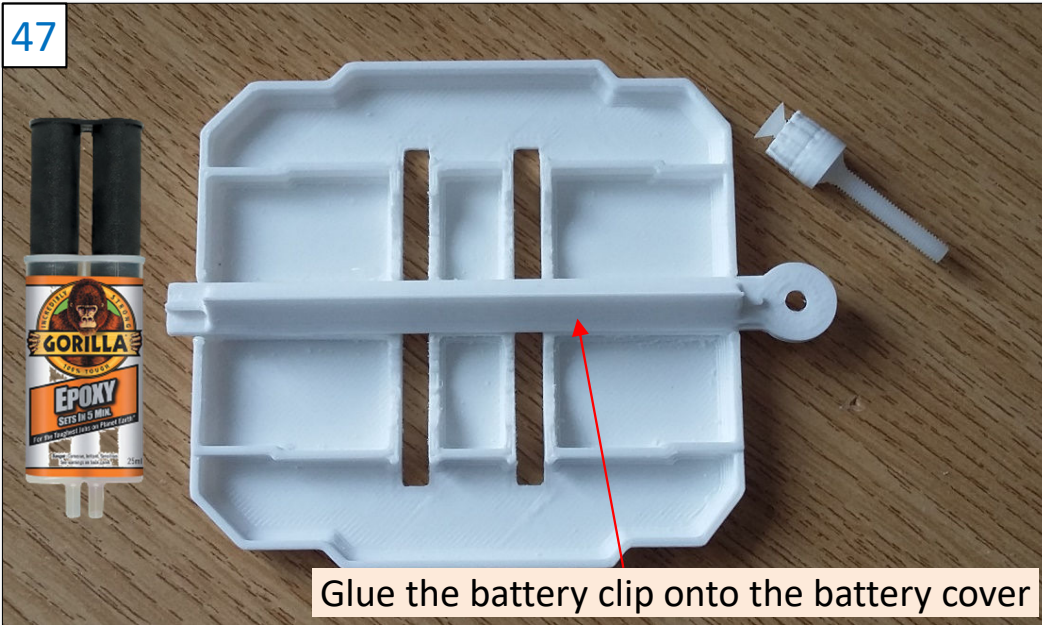

Glue the battery clip onto the battery cover

48

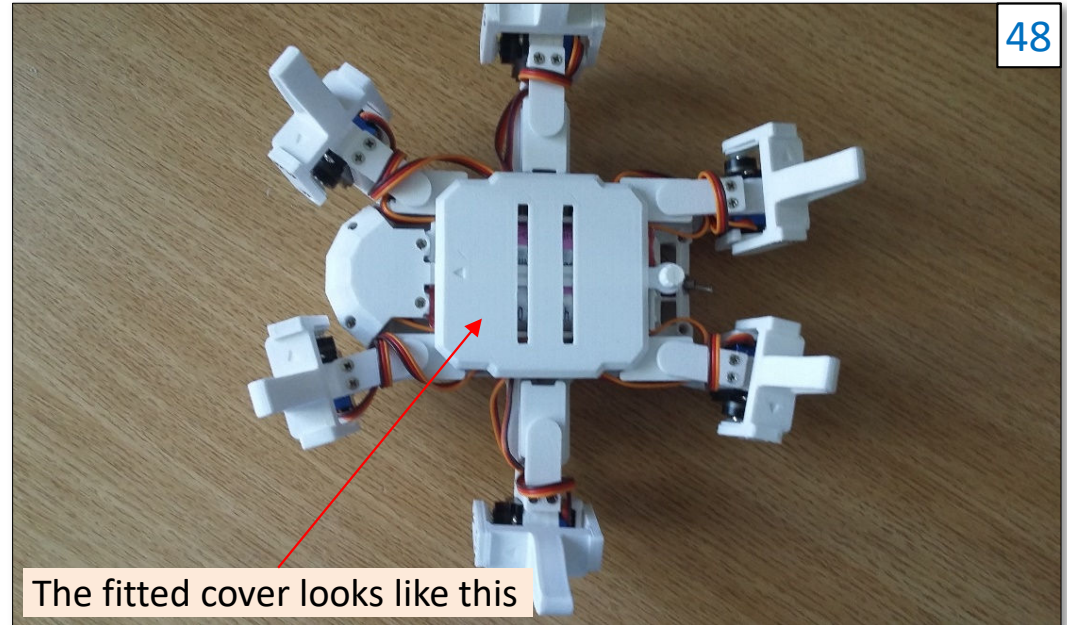

The fitted cover looks like this



## Wiring Sequence

49




50





# RGB LED assignments

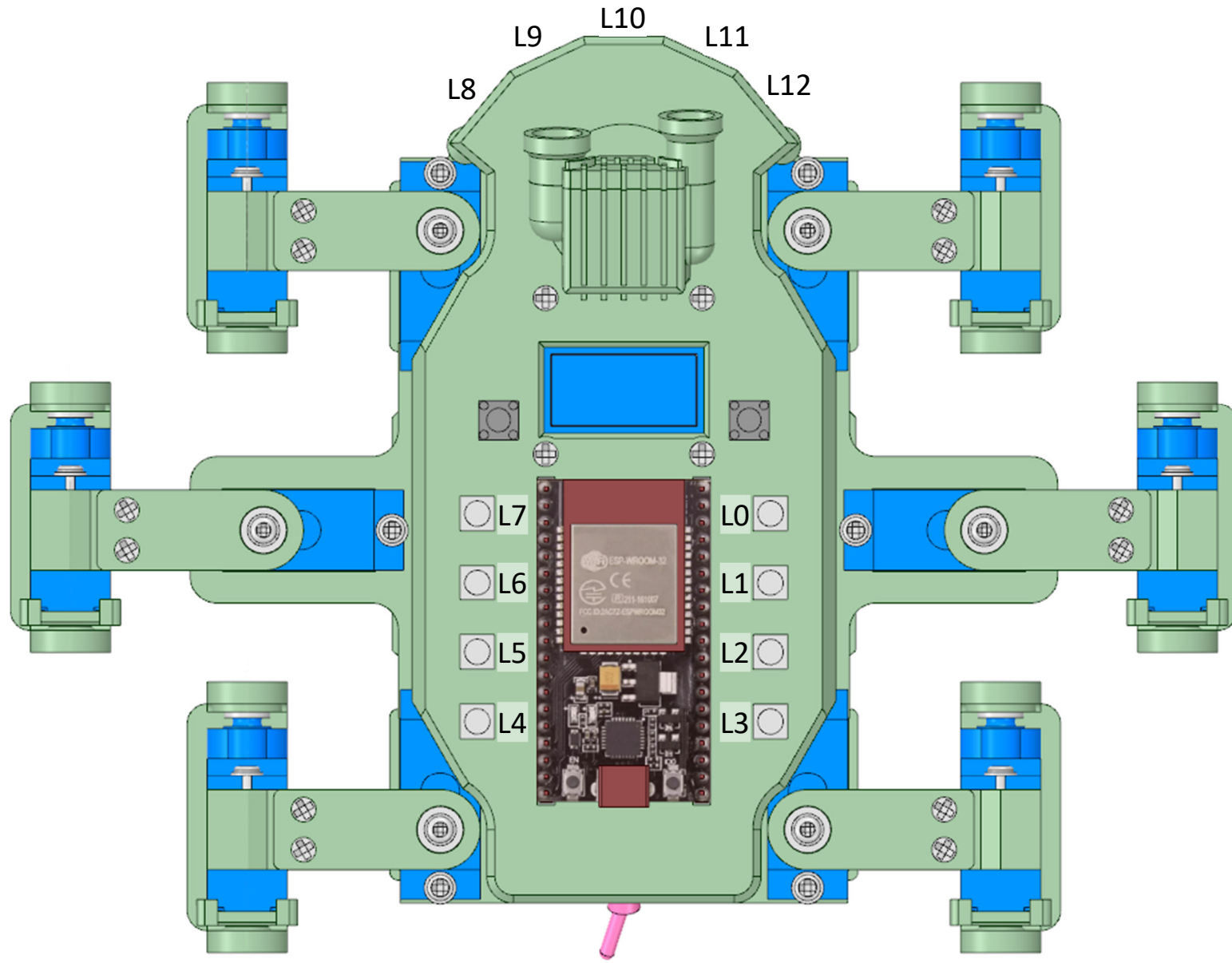



## Battery Voltage Health Monitoring

See 18650 discharge curve obtained from the internet. In this analysis both batteries are identical and connected in series,

Assume fully charged batteries max voltage is  $V_{BM} \geq 8.2v$  max

I measured my rechargeable PP3 at 8.65v when connected and ON.

Set battery warning point at  $V_B = 7.00v$

Set battery critical point at  $V_{BC} = 6.60v$

ESP32 is powered from batteries connected to  $V_{in}$ .

3.3v at  $V_{ADC} == 4095$  on 12-bit converter (4095 max).

If we use a 6k8 resistor feeding A0 and a 3k3 resistor to GND, we get a

conversion factor of  $10.1v == 4095$  or  $2.47mV/bit$  or  $404.85$

Using a Multimeter I determined the conversion factor needed to be reduced to 383.9 to display voltage correctly.

MAX:  $V_M = 8.2v$ , gives  $A0 = 3148$  on ADC ( $V_M * 383.9$ )


WARNING:  $V_B = 7.0v$ , gives  $A0 = 2687$  on ADC ( $V_B * 383.9$ )

CRITICAL:  $V_{BC} = 6.6v$ , gives  $A0 = 2534$  on ADC ( $V_{BC} * 383.9$ )


The code will sample the battery voltage on power-up to ensure it is sufficient, then at every 40ms interval, calculating an average (1/20) to remove noise.

Given the relatively light current drawn I have assumed a linear discharge curve ranging from 8.2v (100%) to 6.6v (0%) capacity. The rate of discharge is monitored and used to actively predict the life of the battery in use.

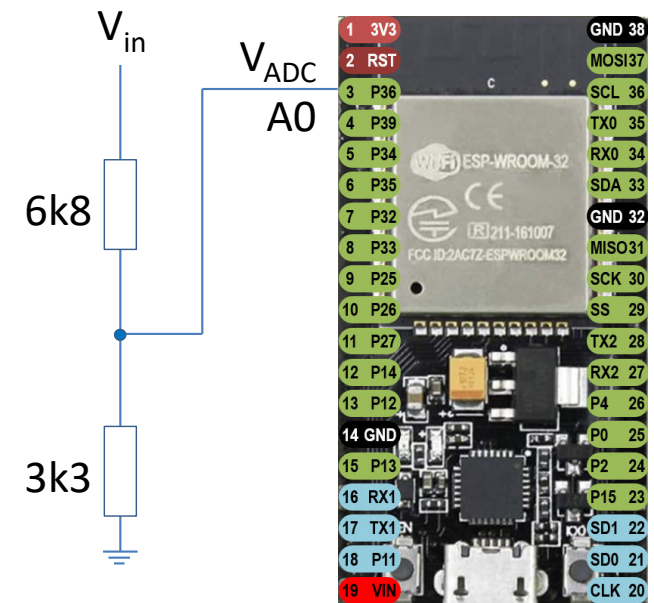Note: If connected to USB port with internal battery switched OFF the ADC will read a value 5 volts ( $A0 = 1919$ ) or less. So if the micro starts with such a low reading it knows that it is on USB power.



18650 Lithium Battery Discharge Profile

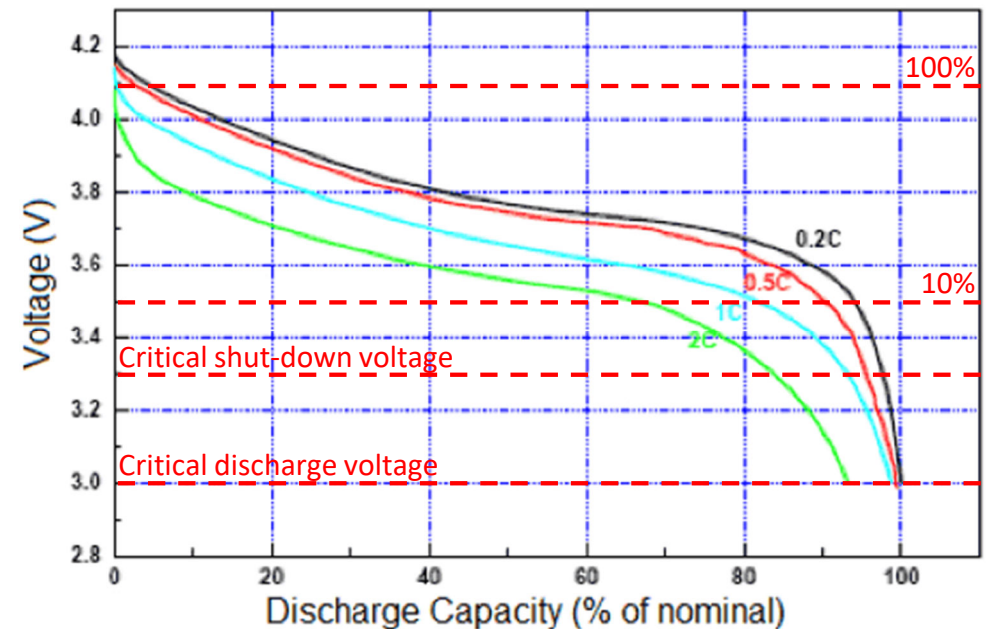

Discharge: 3.0V cutoff at room temperature.