
Cube 8x8x5 HD

Circuits & Wiring

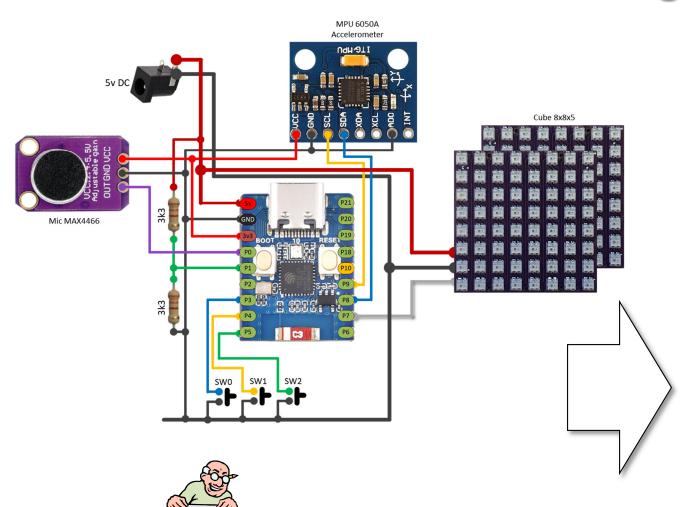



Read through this documentation completely <u>before</u> attempting this project. The construction in parts is quite tricky, to say the least.



Hand Tools:

Recommended:

Fine nosed pliers

Side cutters

1.5 mm Drill

2.0 mm Drill

4.0 mm Drill

Needle files

Screwdrivers

Craft knife



Note: Not all items needed are shown here.

Some printed components act as aids and gauges. Use them.



Tools & Materials:

60W Temperature controlled iron
Solder flux resin
Resin cored solder
Hot melt glue gun {optional}
2-part epoxy resin glue
Screw drivers
Wire wrapping tool
Wire wrapping wire 30 AWG
24 AWG stranded wire (red & black)
Multimeter





Issue: 1.2

Released: 29/01/2025


TechKnowTone





After upload, press RESET to run your code

Design Prototyping

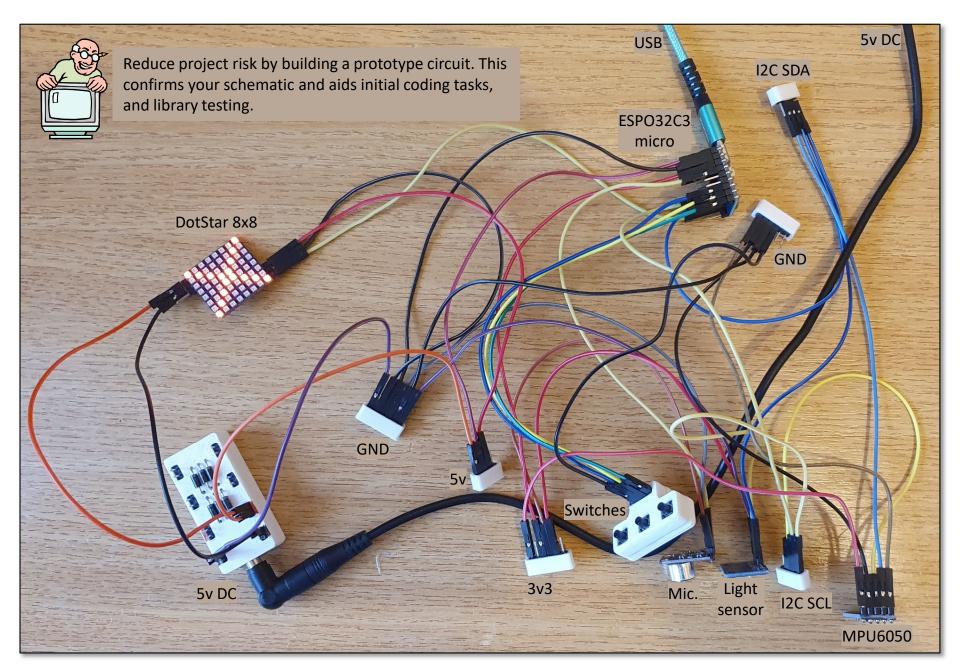





Front Plate Column Wiring


This diagram shows the front plate wiring, as viewed from the rear, upside down. All major components are shown in plan view, for reference, but may be flipped over in practise.

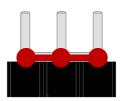The three common connection points, 5v, GND and 3v3 are made from pin strips. The pins are pushed through the base, so that they are flush with the plastic body, then soldered together with wire, and cropped to size, once mounted.



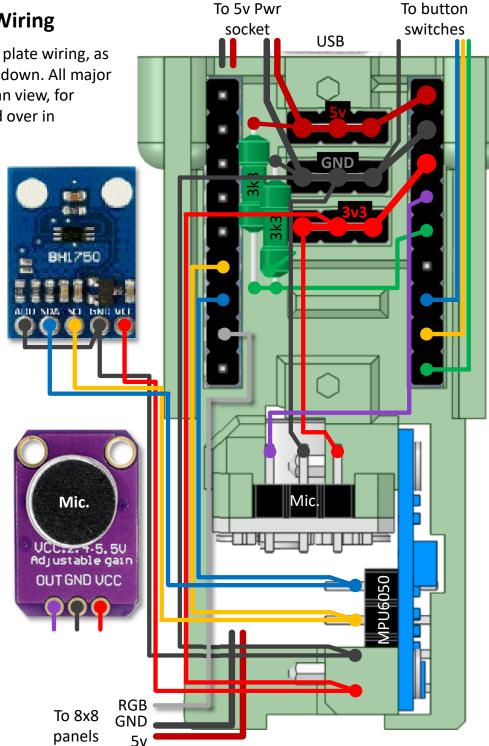Note: keep pins as short as possible. There is very limited space in this design. Always crop them back once wiring and soldering are complete.



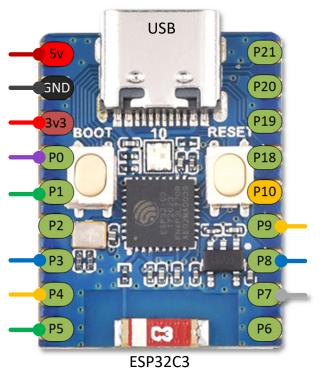


Issue: 1.2 Released: 29/01/2025


Front Plate Wiring - Step 1


With the ESP32C3 Zero micro glued into position, along with the mount for the microphone sensor, and the two 3k3 resistors, wire up the three common supply lines and the resistors as shown.

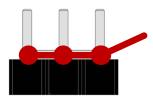The three common connection points, 5v, GND and 3v3 are made from pin strips. The pins a re pushed through the plastic bases, so that they are flush with them. Then the pins are soldered together with wire, from the micro, and cropped to size.



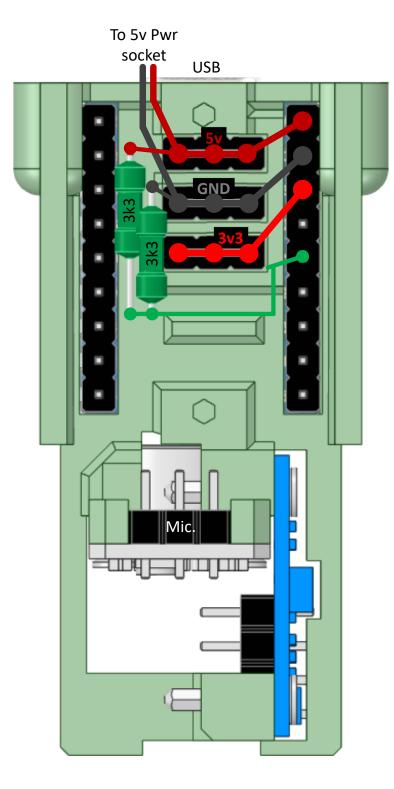Wires are attached to the 5v and GND points, with sufficient length to feed through into the base, and connect to the power socket.



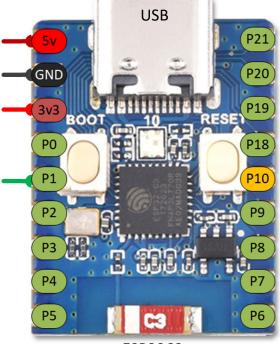

ESP32C3


Front Plate Wiring – Step 2


Next attach wires to the GND and the three switch input connection points, with sufficient length to reach the switches in the base; to be connected later.

Then wire up three the microphone connections, using wire-wrap wire. Then solder the joints, before attaching it to its mount with two screws. And then complete the wiring to the micro and common power points, GND and 3v3.

Ensure the wires are long enough before soldering onto the mic pcb.

Mic.

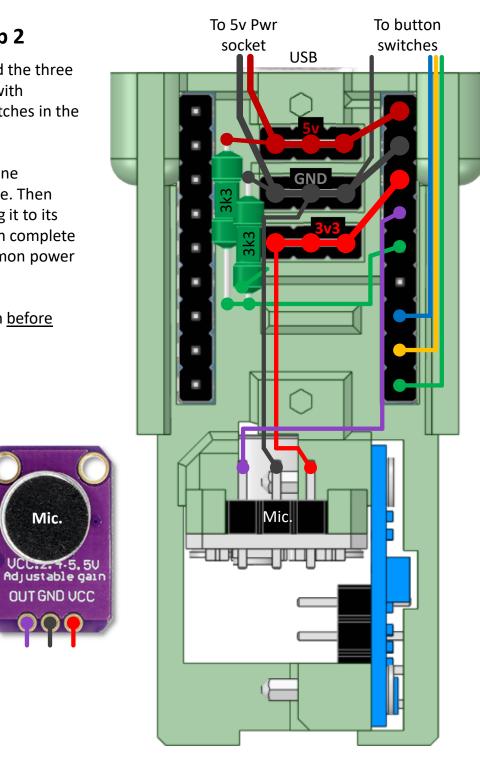

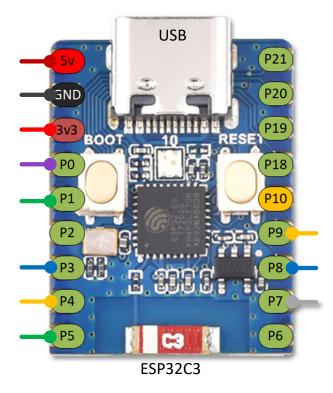



Front Plate Wiring – Step 3


Next, with the BH1750 light sensor glued to the back plate. Wire the micro to the MPU6050 motions sensor first.


Then attach wires to the BH1750 light sensor, including the address line.

Note: you will need to crop the pins on the light sensor and the common connection points, as they are too long, and will prevent the back cover from being in place.


Ensure that there is clearance between the common connection pins and the light sensor pcb. So that they do not touch the pcb when the case is closed.

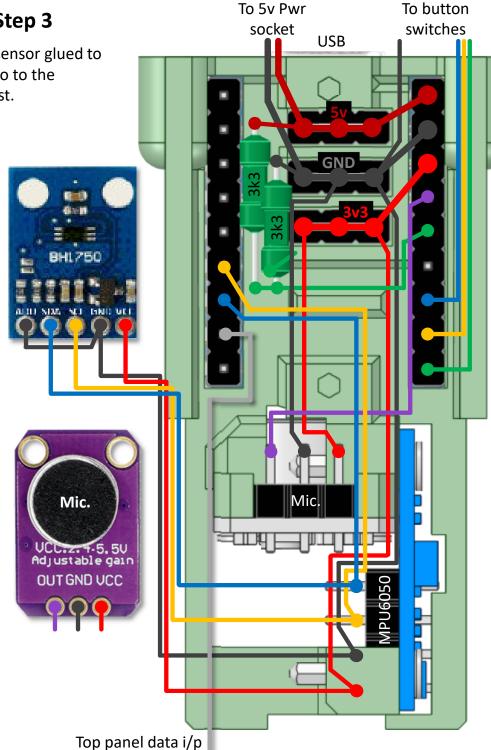This completes the column wiring. The wiring of the base switches is next.



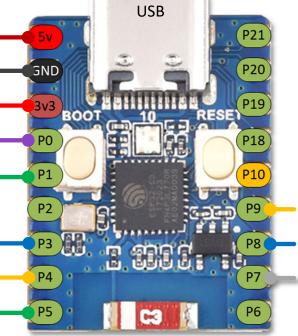

ESP32C3

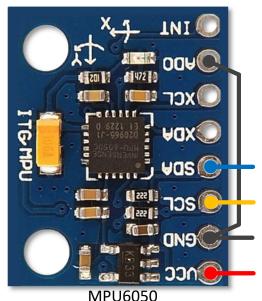

Issue: 1.2 Released: 29/01/2025

TechKnowTone




Base Wiring - Part 1


The base button switches are wired as shown. Note that there are two pins for each of the switch contacts. They are like staples inside the swich body, and pushing the switch shorts them together.

For clarity the wiring here obscures the USB entry point, but in practise the wires are held out of the way, above the switches.

The 5v positive and GND connections are wired from the internal pin strips to the external socket, once the base is fastened to the body column.

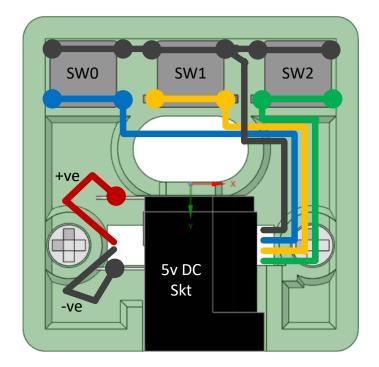Then once the cube panels are attached to the body column, the GND and 5v feed from the cube are also wired to the external sockets once the assembly is complete.



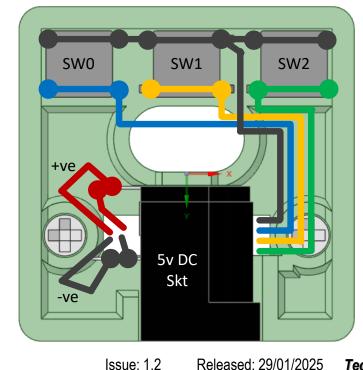




Released: 29/01/2025 TechKnowTone

8x8 Panel Wiring

RGB strip code tests, run on a panel, show that the LEDs will work at 3v3 to 5v, driven via an ESP32C3, running FastLED. Whilst the ESP32C3 works at 3v3, there does not appear to be any need for a level-shifting LED, as with the previous WS2812B panels, so one is not used in this project. This affects the LED mapping for the LED matrix, resulting in a code change.

When viewed from the front, with data input fed from the bottom right, the bottom right LED '0' is the first in the chain of LEDs. The next LED '1' is above that, and so on, making the top right LED '7'. The LED chain then restarts at the bottom '8', and follows the same sequence up the panel. Such that finally, the top left LED is number '63' in the daisy chain.

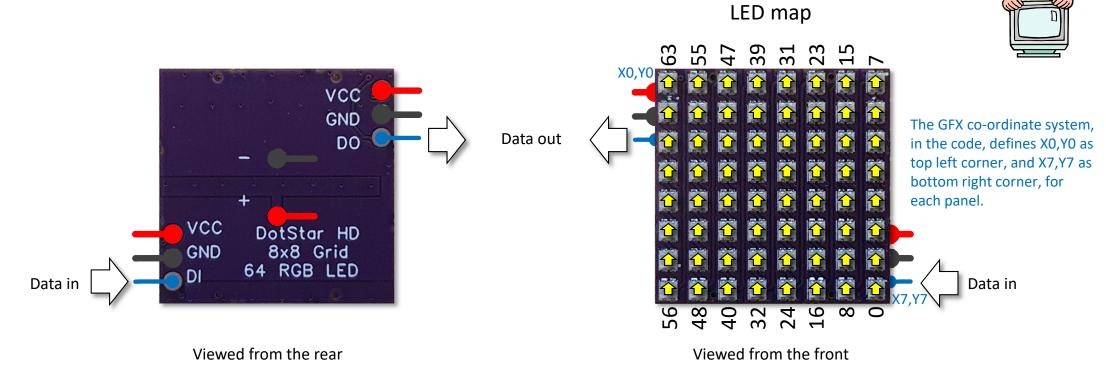This is different to the previous projects WS2812B 8x8 panels, which also started bottom right, but ran horizontally left across the panel, rather than up it. Thankfully, the revised GFX code functions, I've written, takes all of this LED mapping into account; which means that the animations used in the previous project will work with this one too.



8x8 LED Matrix Mapping

Data connections are shown from the outside, but actual wiring will need to be mirrored on the inside. There are 320 (64 x 5) LEDs in total.


On the Top Plate, the first LED in the sequence is at the bottom right-hand corner. The top LED matrix then drives LED 64 on the rear facing plate, bottom right, and so on as indicated in this diagram, which shows how LEDs in the overall strip are addressed on each panel.

Rear face Top face

Ensure that you understand the detail in this diagram, as it will help you with coding cube patterns in the future.

> Face 0: 000 - 063 Face 1: 064 - 127 Face 2: 128 - 191 Face 3: 192 - 255 Face 4: 256 - 319

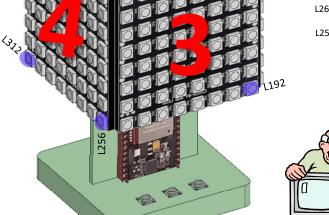Arrows indicate the flow of RGB data within each panels LED strip.






The code GFX functions expect the LED panels to be connected in this way. If you fail to follow this convention, you will get unexpected results, which will be difficult to correct in code. Right face


8x8x5 LED Matrix Wiring


Data and power connections are shown here, from the inside of the cube.

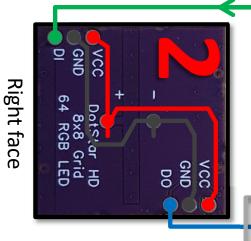The data in DI connection, on panel 0, is fed directly from the ESP32C3 micros, GPIO7 output pin. The data out DO connection, on panel 4, is not used in this design. But could be used to extend the LED array further, if needed.



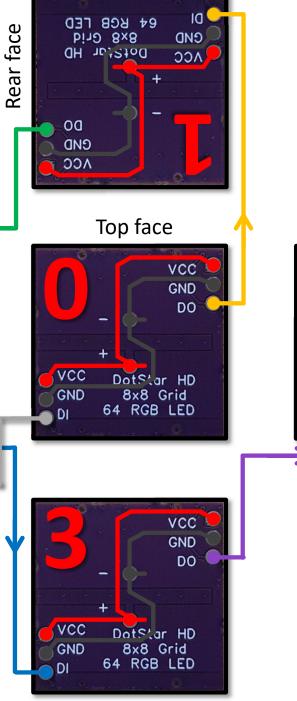The panel VCC (+5v) and GND connections, for each panel, are wired together. Then one pair of wires brings power up from the cubes base socket.



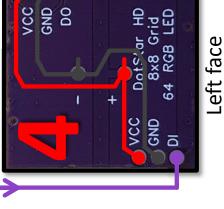

Front face

Issue: 1.2

8x8x5 LED Matrix Wiring

Data and power connections are shown here, from the inside of the cube.


The data in DI connection, on panel 0, is fed directly from the ESP32C3 micros, GPIO7 output pin. The data out DO connection, on panel 4, is not used in this design. But could be used to extend the LED array further, if needed.

The 8x8 DotStar panels are placed in the Shell Frame, in the correct orientation for wiring. Then the Cube Shell is glued into position on top.

Right face Note this reference **Cube Shell** 8x8 Panel **Shell Frame**

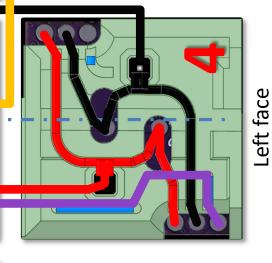Remember, to crop back the pins, once the wiring and solder are done.






Note, that the grey 'data in' wire in the centre, wired to the Top face, needs to be long enough to reach the ESP32C3 micro in the body column. Be generous with its length. It also passes under the top of the body column (blue dotted line), when it is finally in position, and the cube panels are folded up.


Released: 29/01/2025


Front face


Rear face


TechKnowTone

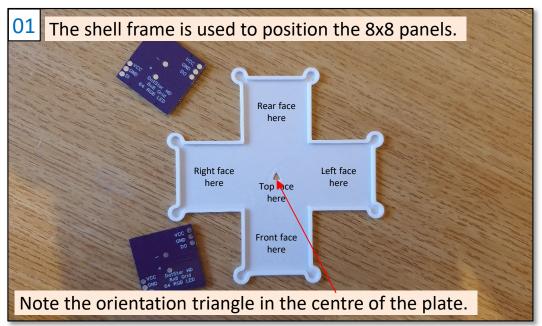


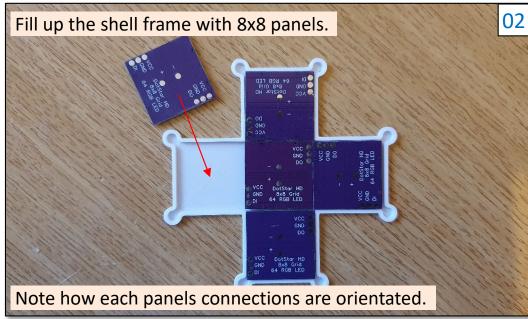


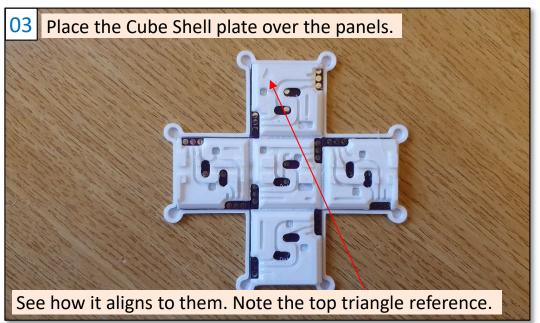


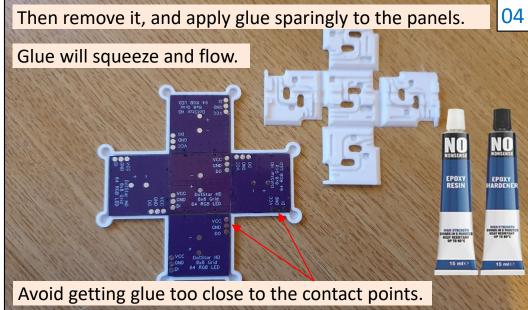


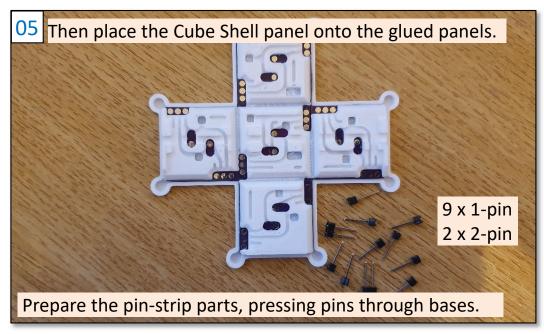

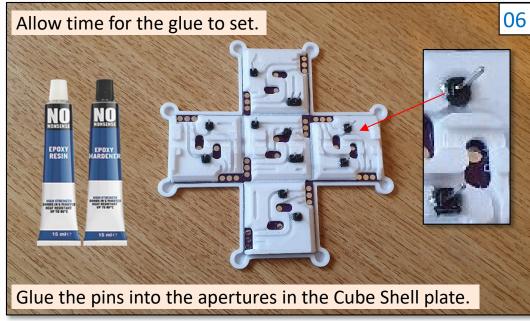


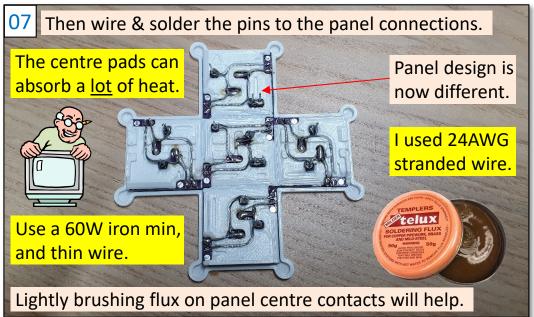


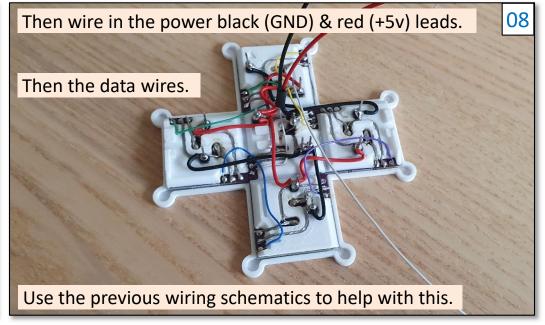


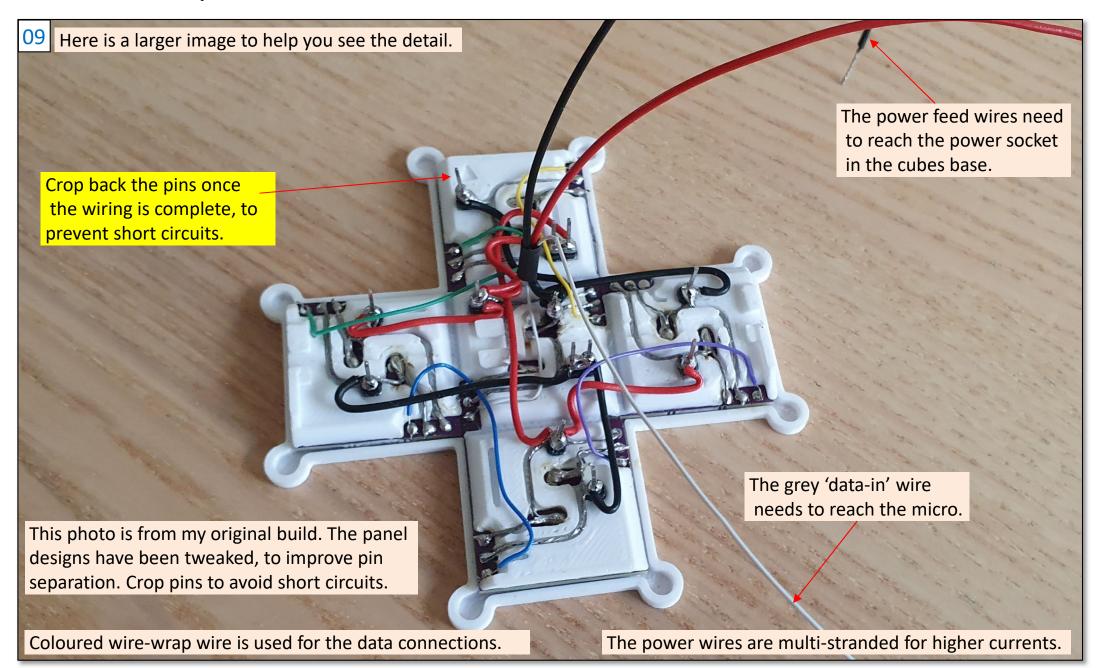




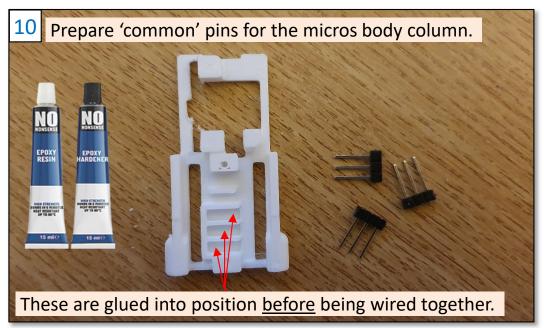


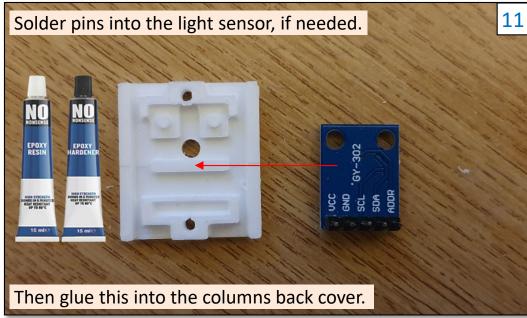


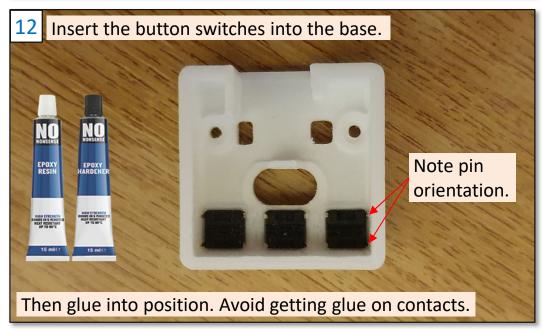


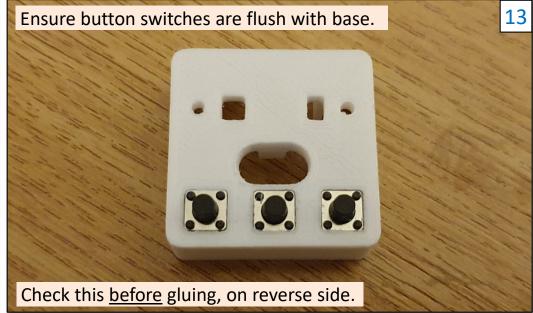



Issue: 1.2

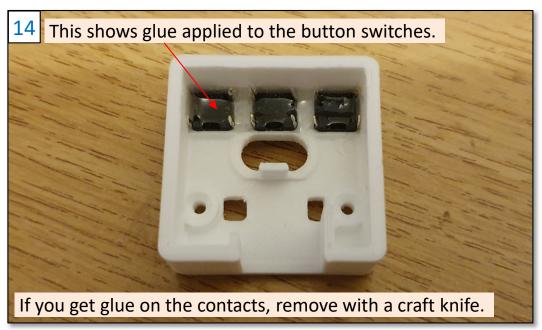


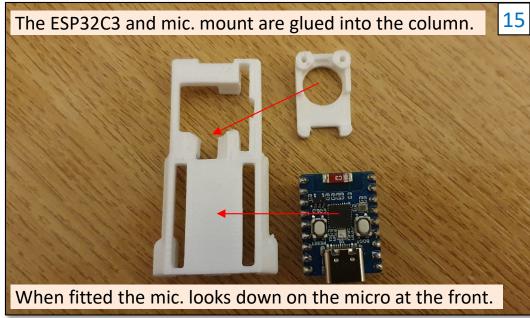


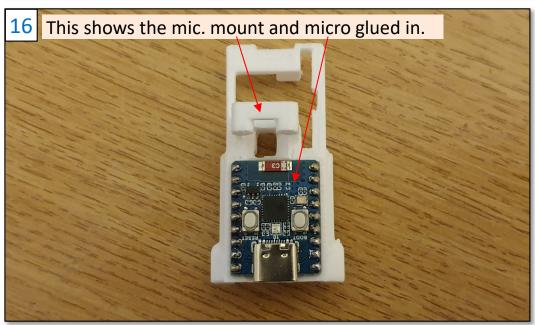


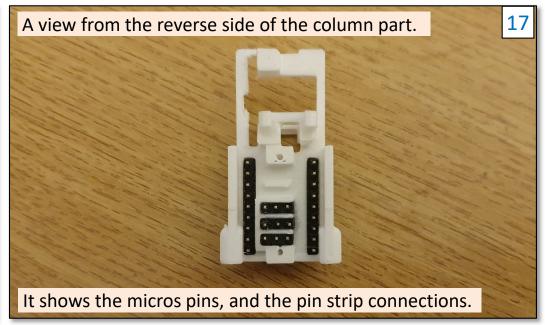


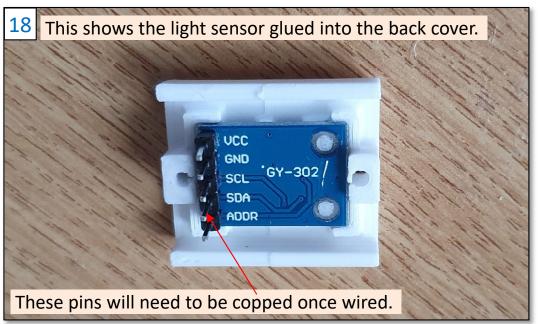


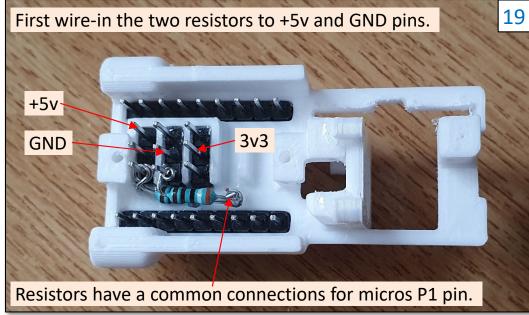


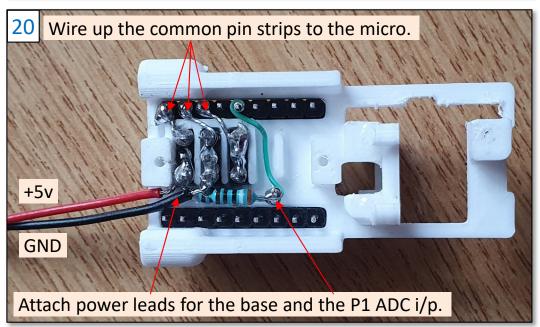


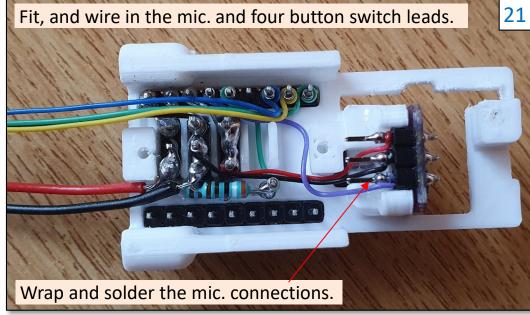


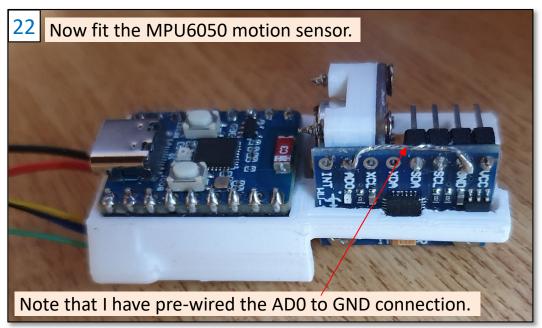


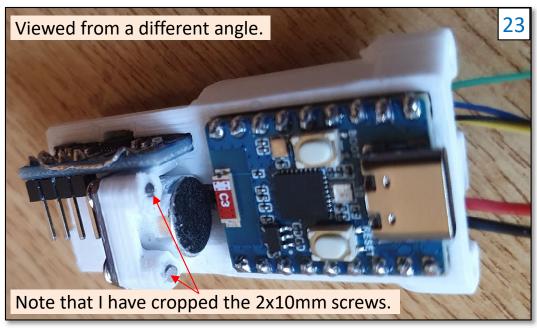


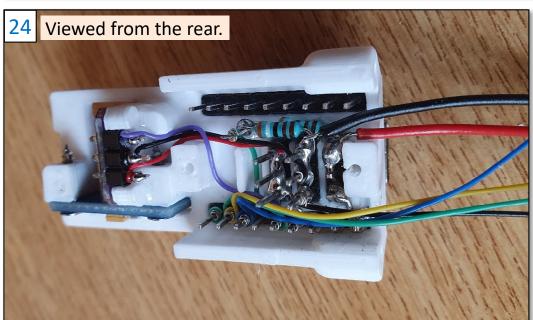


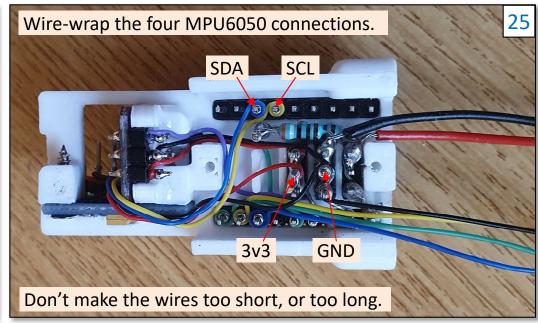


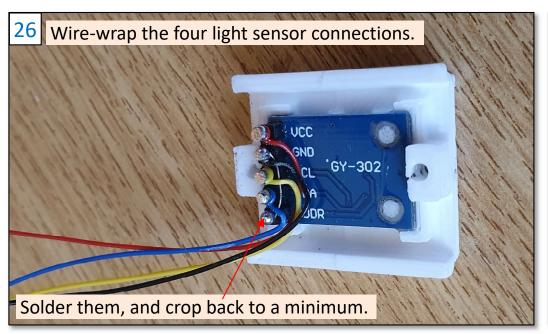


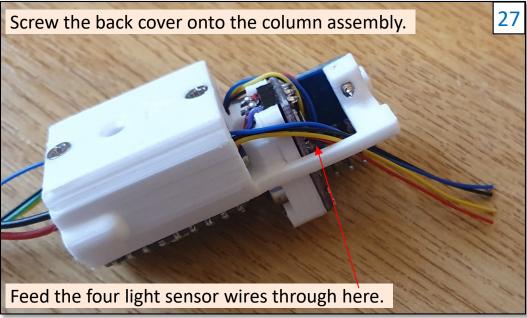


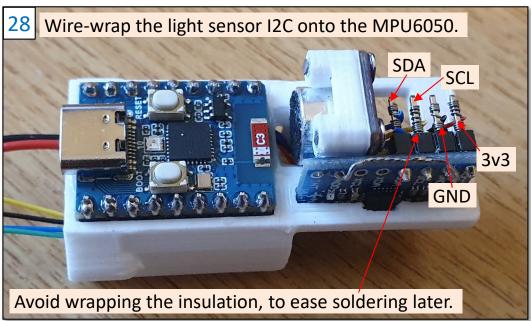


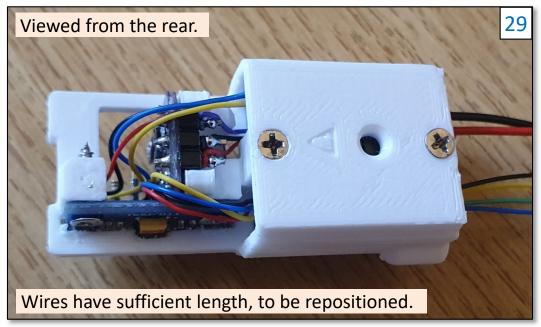


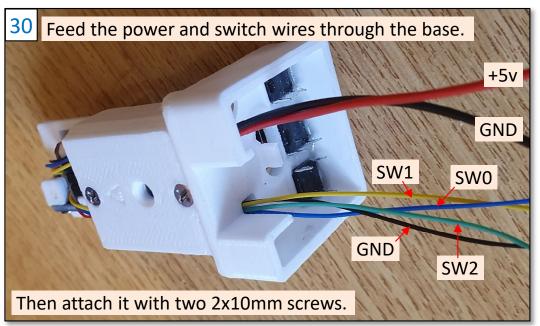


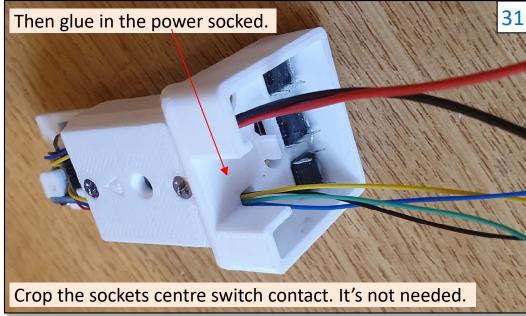


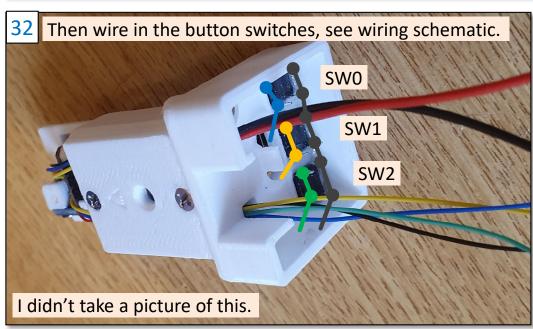


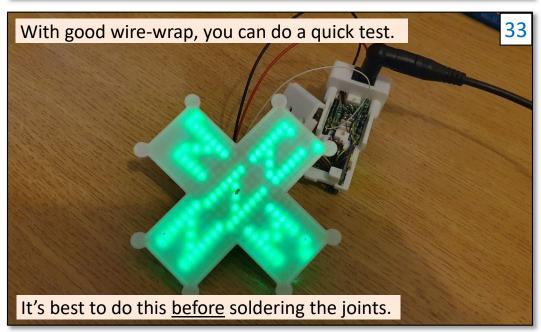

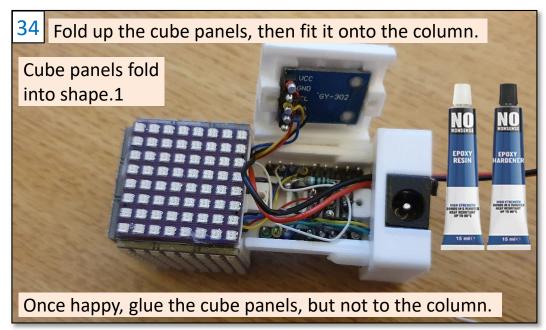

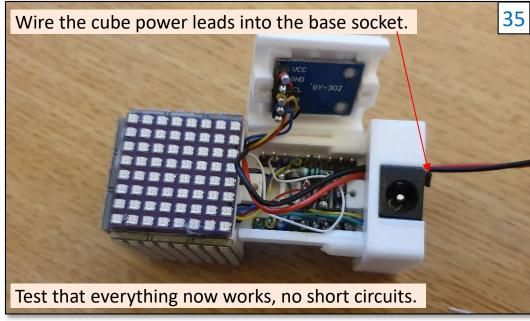


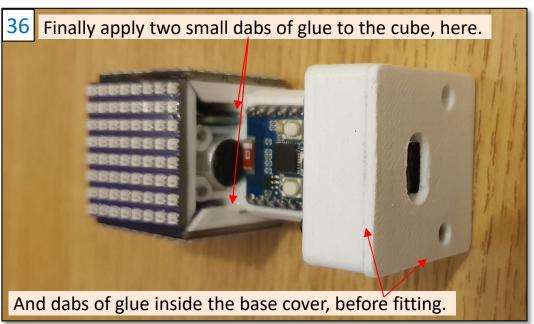


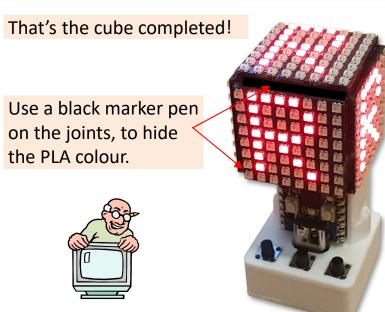



37

Make it outstanding!

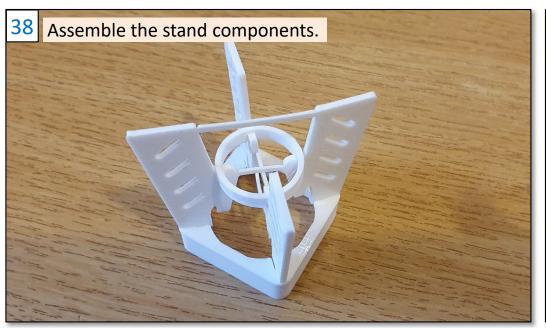

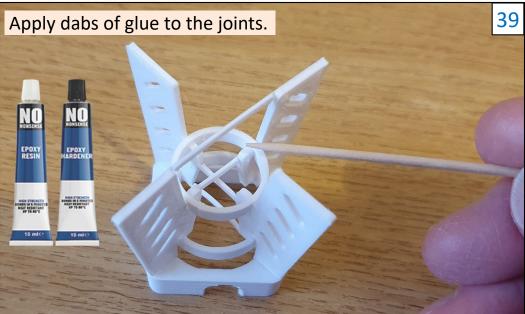

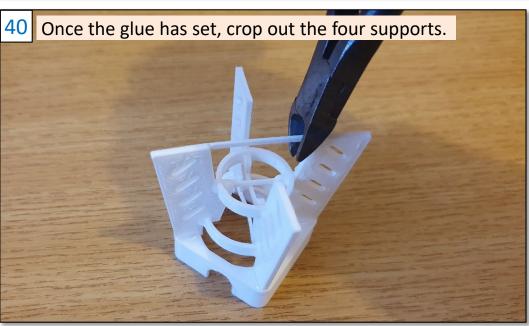

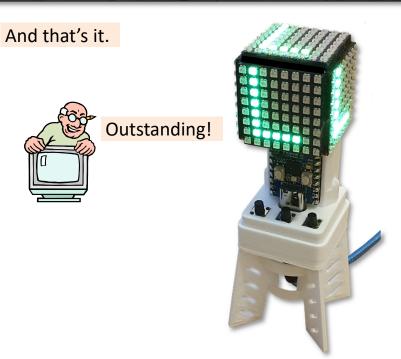

Issue: 1.2 Released: 29/01/2025 **TechKnowTone**

41

ESP32C3 Flashing

If you have not used an ESP32C3 before, then this should help you put code into it using the Arduino IDE.

Within the Board Manager you need to have installed the definitions from **esp32** by Espressif Systems.

Connect the micro to a USB port, and within the IDE select that port and the board type as: **ESP32C3 Dev Module**

The dropped down menu should then display this in **bold** text.

In the Tools menu you should have the following settings:

USB CDC On Boot: "Enabled"

• Flash Mode: "QIO"

• JTAG Adapter: "Disabled"

• Upload Speed: "115200"


Press and <u>hold</u> down the **Reset** button on the ESP32C3 micro.

The board name in the drop-down combo should lose its boldness.

Now press and <u>hold</u> down the **Boot** button.

Then release the Reset button, whilst the Boot button is still pressed, and after a second or two the board listed in the drop-down combo should once again be **bold**, indicating that the board has re-connected to the IDE in Boot mode.

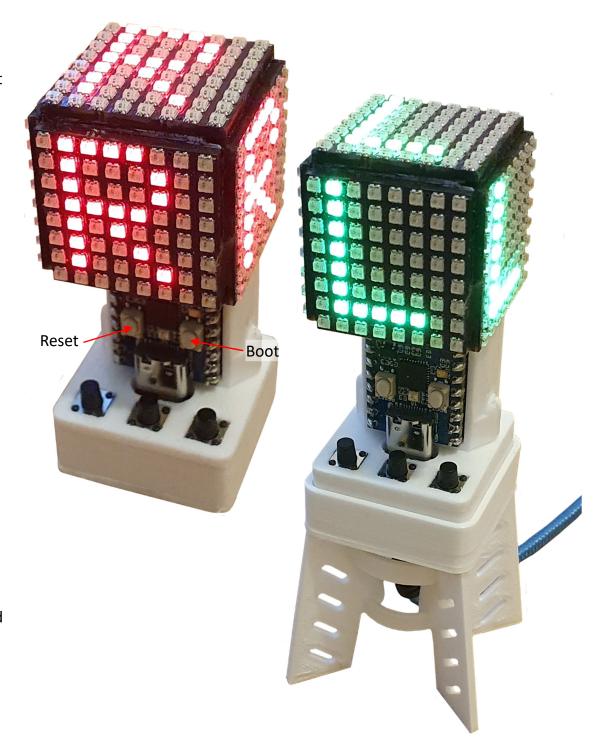
Now release the Boot button. And you can flash the device from the IDE in the usual fashion. Then press **Reset** to run the code, <u>after</u> flashing is completed.





Issue: 1.2 Released: 29/01/2025


TechKnowTone

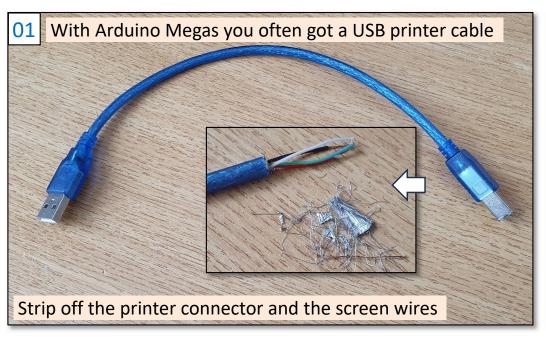USB Cable – made from an old Printer cable



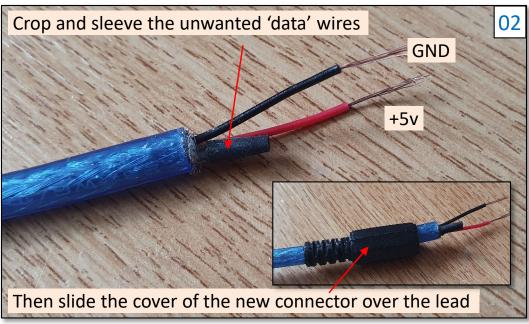

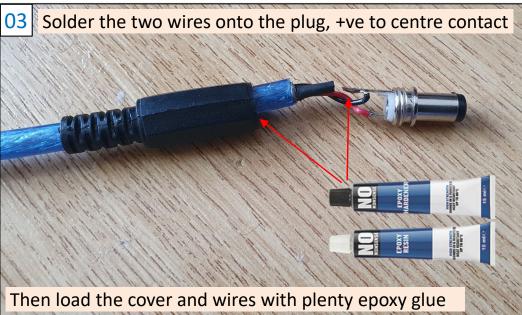

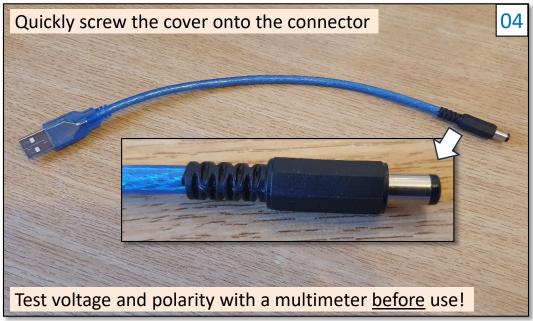

MPU6050 Motion Sensor

The MPU6050 3-axis motion sensor is mounted inside the cube as shown.

The X-axis aligns front to rear. The Y-axis is vertical, and the Z-axis is right to left.

We will define pitch, roll and yaw motions as follows:

Pitch – determined by gyro Z and accelerometer X. Positive pitch, is when the cube is leaning forwards. Gyro Z will be positive, when tipping forwards, and accelerometer X will be positive. When the cube is perpendicular, X is zero.

Roll – is determined by gyro X and accelerometer Z. Positive Roll, is when the cube is leaning to the right. Gyro X will be negative, when tipping to the right, and accelerometer Z will be positive. When the cube is perpendicular, Z is zero.

Yaw – is determined by gyro Y. The Y accelerometer will be reading gravity, and normally outputting a large positive value.

When the cube is in the upright position, the Y accelerometer is +ve and -ve when it is upside down.

