
Project: 3-Wheeled Omni-Bot

Circuits & Wiring

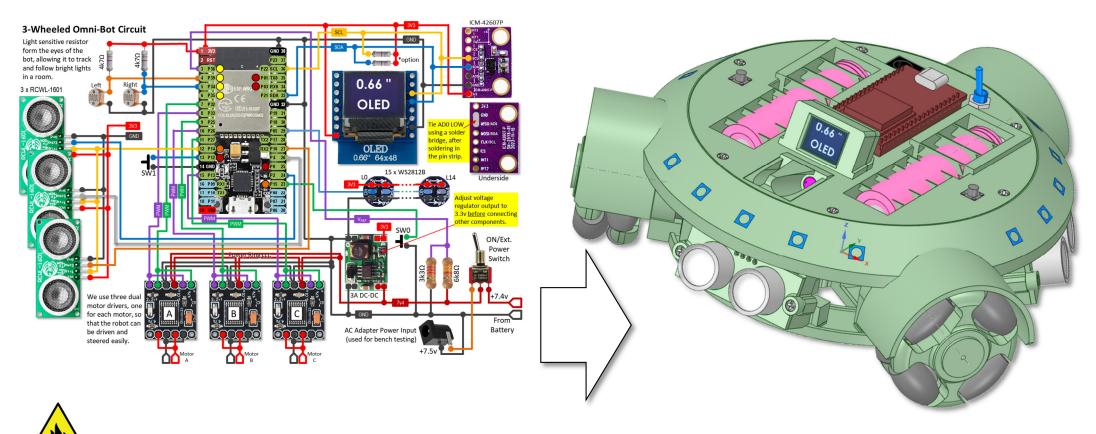





Read through this documentation completely <u>before</u> attempting this project.

Issue: 1.1 Released: 28/11/2025 **TechKnowTone**

CAUTION

Lithium batteries can be <u>extremely</u> dangerous, if not handled and cared for properly. This design does not include any form of current limiting circuit, like a fuse. So, care <u>must</u> be taken to ensure that the wiring guidelines are followed accurately, that checks are made for short-circuits, and that battery polarities are marked, and they are inserted the correct way round. Failure to do so, could result in an explosive fire.



Charging Practices: Always remove batteries from your project to charge them. Use a charger, designed for the battery used, and from a trusted supplier. Choose a flat, non-flammable surface to charge on, away from flammable materials. Never leave unattended when charging. Don't charge overnight. Monitor charging to ensure charge characteristics are as expected. Only pair batteries with similar characteristics. Do not overcharge, or leave charging for prolonged periods. This increases the risk of damage and fire.

Battery care & maintenance: Stop using a battery if it is swollen, damaged, dented or leaking. Never charge a damaged battery. Never allow a Lithium battery to discharge below 3.2 volts, as cell damage will occur.

Avoid extreme temperatures. Do not charge or store batteries in very hot or cold environments.

Don't cover batteries whilst charging, as this can trap heat, causing overheating.

In case of fire: Get out and stay out. If a fire starts, leave immediately, and call the fire brigade. For low voltage Lithium batteries, water is a safe extinguisher.

Built-in Monitoring: Most of my project designs include code, and circuitry, to monitor battery voltage, whilst in use. This code then seeks to alert the operator, when the battery has reached a critical low voltage, before shutting down power consuming circuitry; including the micro. Time should therefore be spent on calibrating this feature, as a precaution, for good battery management and maintenance.

Carefully dispose of batteries that damaged, or discharged below their critical voltage.



Hand Tools:

Recommended:

Fine nosed pliers

Side cutters

1.5 mm Drill

2.0 mm Drill

4.0 mm Drill

Needle files

Screwdrivers

Craft knife



Note: Not all items needed are shown here.

Some printed components act as aids and gauges. Use them.



TechKnowTone

Tools & Materials:

Temperature controlled iron Solder flux Resin cored solder

Hot melt glue gun {optional}

2-part epoxy resin glue

Screw drivers

Tweezers

Wire wrapping tool

Wire wrapping wire 30 AWG

24 AWG stranded wire (red, black & yellow)


Multimeter







Page 4

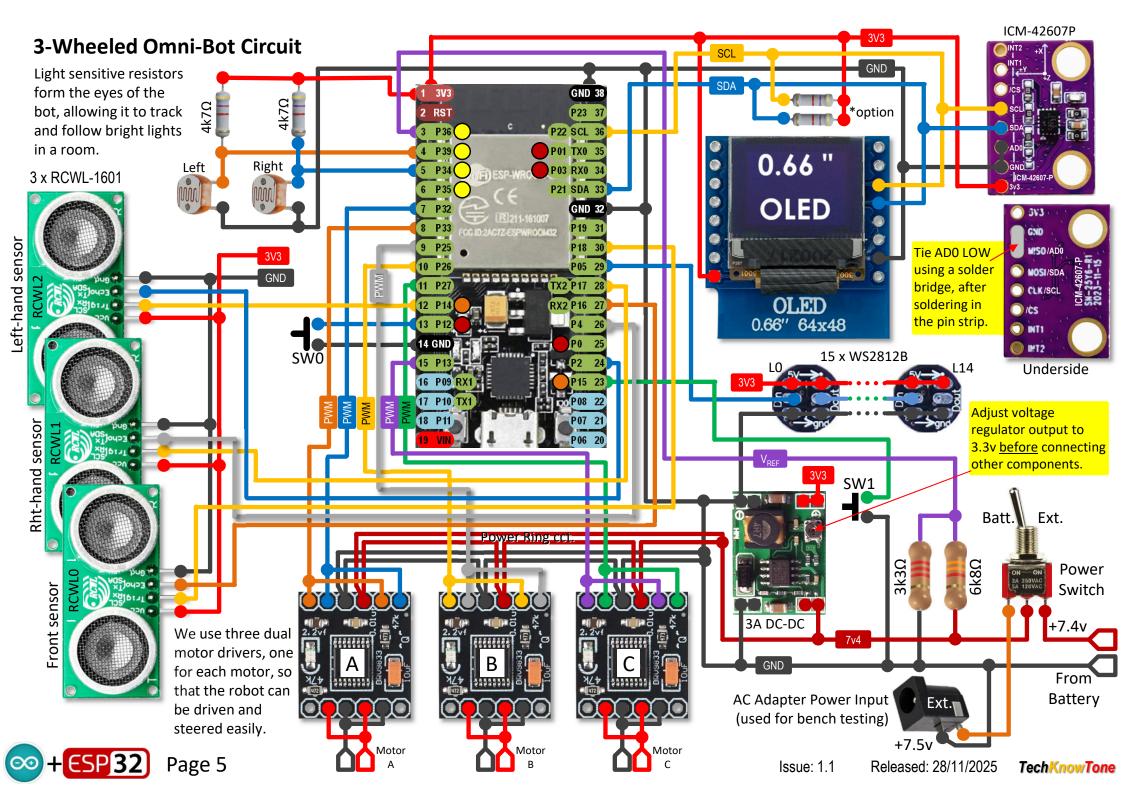

Chassis Base Wiring


This diagram shows the wiring of the chassis motors and their associated H-bridge drivers.

Note that the nominated H-bridge drivers are diagonally opposite the assigned motors. And that the 2-channels are grouped together.

The 7v4 power to the H-bridge drivers is routed in the form of a ring circuits, with the open ends of each ring being terminated at the voltage regulator on the micro plate.

The PWM drive signals also return to the microplate, from the centre region of the chassis plate. The PWM drive signals are wired to drive both channels of the H-bridge driver, thereby combining their current capability.

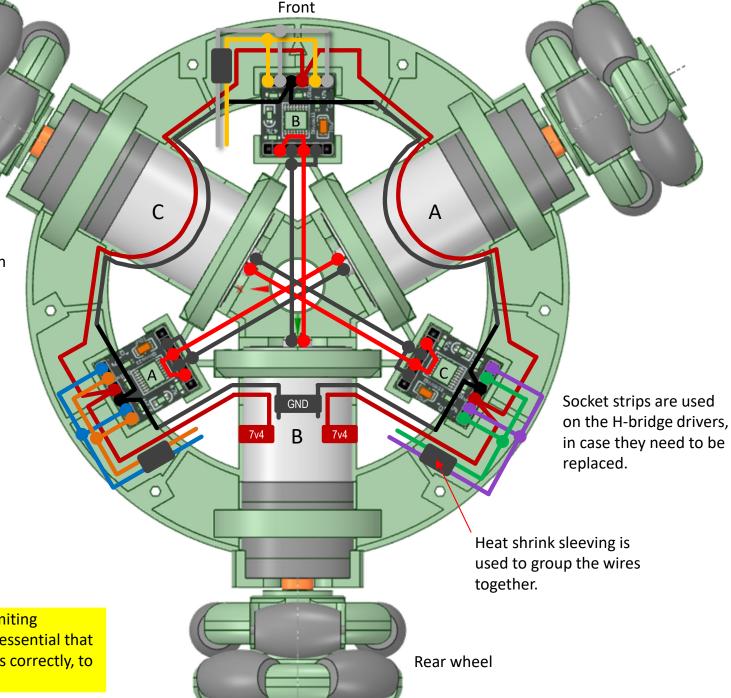The diagram is shown, as if viewed from above, through the microplate.



Issue: 1.1

Released: 28/11/2025

TechKnowTone

Viewed from above

Front right wheel



WARNING: There is no current limiting protection in this design. So, it is essential that you wire the dual H-bridge drivers correctly, to avoid damage.

Front left wheel




DC Motor Wiring


Each motor is wired to its opposite H-bridge driver board. To keep the wire lengths to a minimum, and nice and tidy, it is recommended that you prepare red and black wire leads in the following manner.


The overall wire lengths are 85mm. At the H-bridge end the insulation is removed for 20mm, and at the motor end 10mm. I used multi-stranded tinned copper wires, which I stripped, twisted and tinned with solder, to stiffen them. That makes it easier to form them on the end of the 4-pin socket strip.

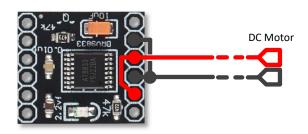The four wire, 2-channel, outputs of the dual H-bridge are combined in a specific manner, to increase the current capability of the driver. If these are wired incorrectly, then damage can result.



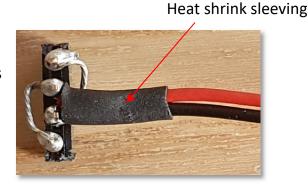The red and black wires are formed and soldered to the pins as shown. Always check your wiring with a multimeter for short circuits.



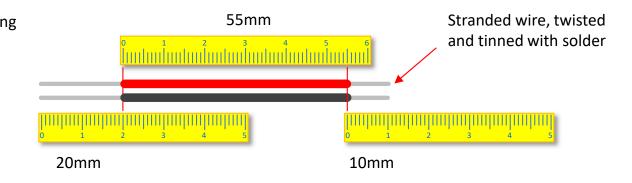





Voltage Regulator

A 3 amp switch-mode voltage regulator is used in this design, given the amount of circuitry connected to the 3v3 rail. The linear regulator fitted to the ESP32 may not cope well with this, and tends to overheat. I wanted long pins on this part, so I used 4 x 2-pin strips, with the insulated bodies pressed to one end.

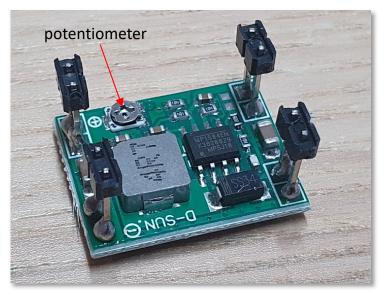Apply a small amount of flux to the pins, before inserting them into the pcb. These can be difficult to solder if your iron is not of sufficient wattage, or set too low a temperature.




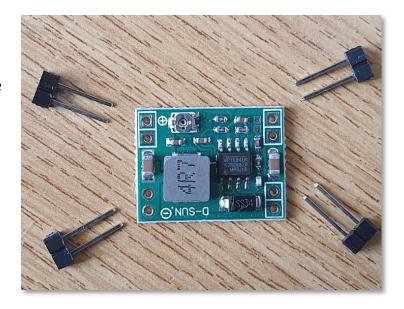

Once they are soldered into the board, the plastic body ends were removed, to gain better access for wiring. Note that soldering the pins can be a challenge, particularly the negative connections, as the board can absorb quite a lot of heat. You may need to turn up the heat on your soldering iron, and use a broader tip, to achieve good heat flow.



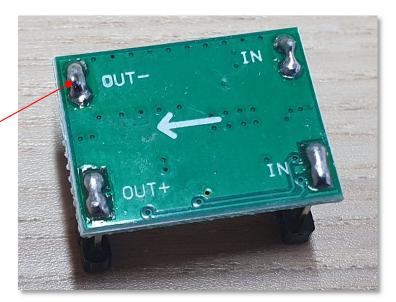On the underside of the pcb I also applied solder, to bridge the 2-pin connections, to improve connectivity. Connect this regulator to a 7.5-8.5v DC supply, and adjust the potentiometer to be in the range 3.3-3.4v, before fitting it into the Omni-Bot. Note, prior to adjustment, the voltage may be high initially, so don't have it connected to other devices, until it has been set up.




Issue: 1.1 Released: 28/11/2025

TechKnowTone

Micro Plate Power Wiring

This diagram shows the initial wiring of the micro plate, where we run in the power wires, from the batteries and external socket, to the voltage regulator. Note, that the voltage regulator should be set to 3v3 before the micro, and other electronic components, are inserted. See photos later in this document.

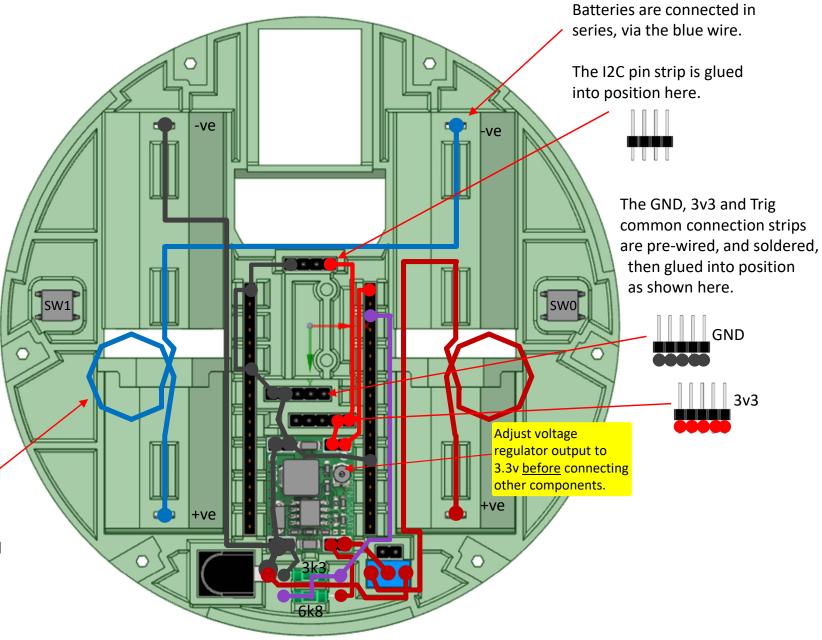Wires from the positive ends of the batteries are looped, so that there is sufficient length to allow the case to slide up and out, for the batteries to be removed and inserted.




Light Sensor Wiring


The light sensor assembly , is wired like this. The light sensitive resistors are first selected, then glued into the filter body, with their leads coming through the rear. And two 4k7 resistors, are glued into position, in wells, as shown.

The part is then pre-wired with wire wrap wire, prior to being glued into the underside of the top micro plate, as shown below.

The two light sensitive resistors are first selected from a group, as the closest matching pair. Under normal room lighting conditions, you are looking for matching values, in the range between 5 - $6k\Omega$.

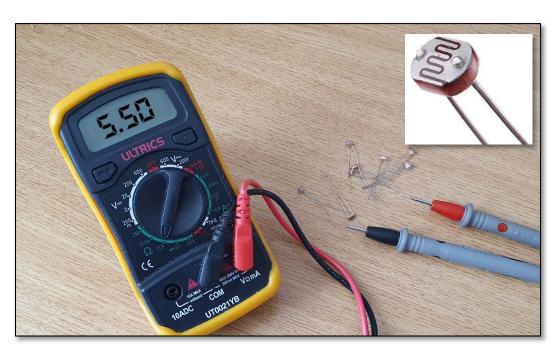Wires are wrapped and soldered onto the sensor, before gluing it into the micro plate.



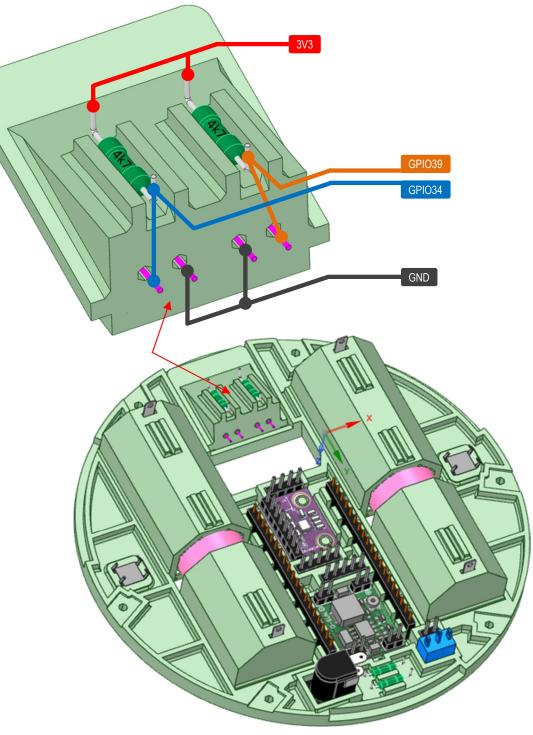

Issue: 1.1

Released: 28/11/2025

TechKnowTone




Micro Plate Wiring Continued

This diagram shows the next phase of wiring. Most of the previous connections have been omitted, to prevent the diagram from becoming too cluttered. I just show the connection points here.

Here the I2C connections are wired to the 4-pin strip common connection points, and then onto the display and ICM motion sensor.

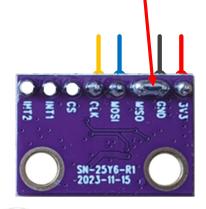Solder the ICM AD0 pin to GND. It is recommended that you test the ICM sensor before gluing it into the case. I have supplied code for this.




3v3

The display assembly is pre-wired before gluing it into the micro plate.


It is recommended that you wire-wrap the pins. Then test the display. Then crop back all pins to about 3mm, so that the back cover will fit. The pins will be too long otherwise. Solder the wire-wrapped pins before closing the assembly

Note that my code package, contains small and simple test programs for all sensors. Which can be used throughout the build process, to confirm functionality, as the build progresses.

Micro Plate Wiring Continued

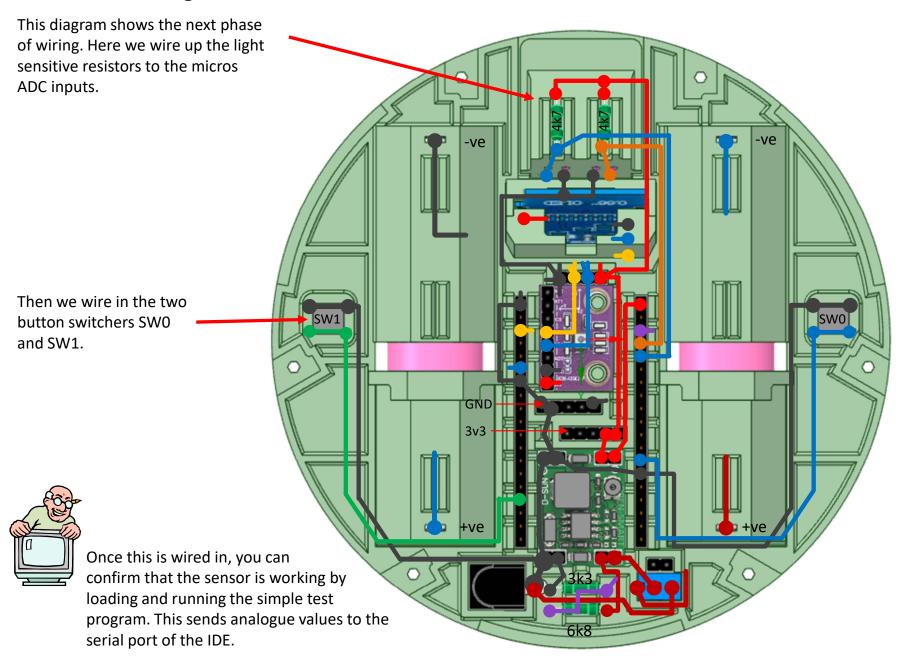



Released: 28/11/2025

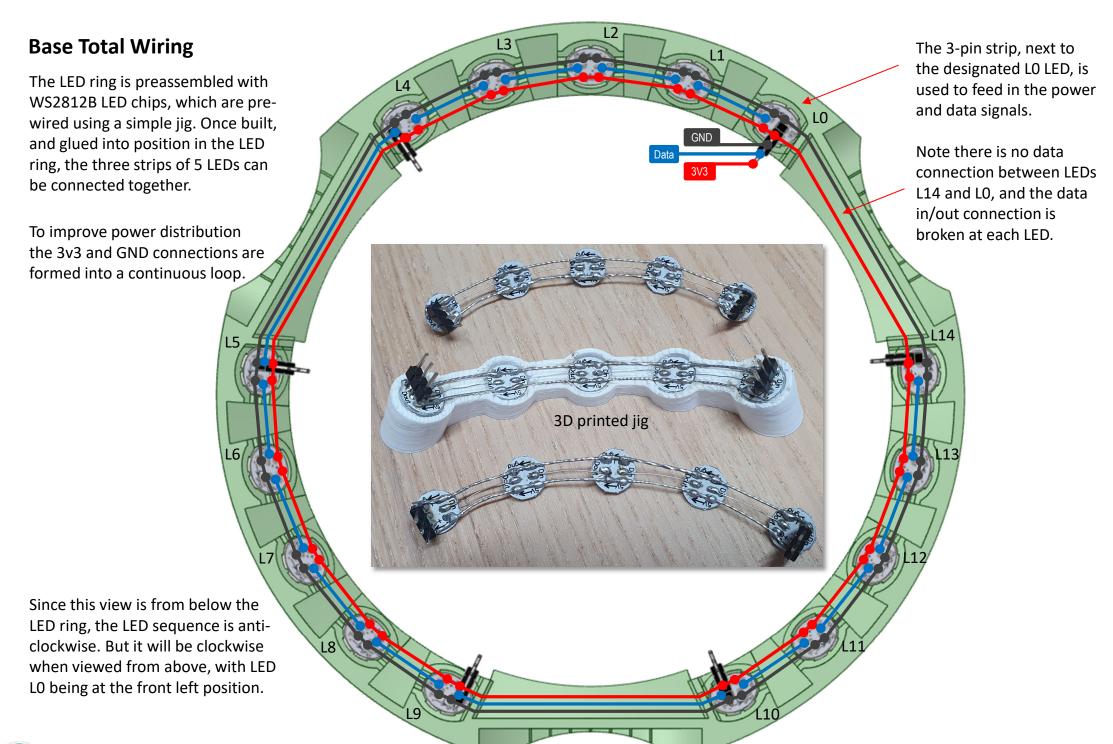

• + ESP 32 Page 13

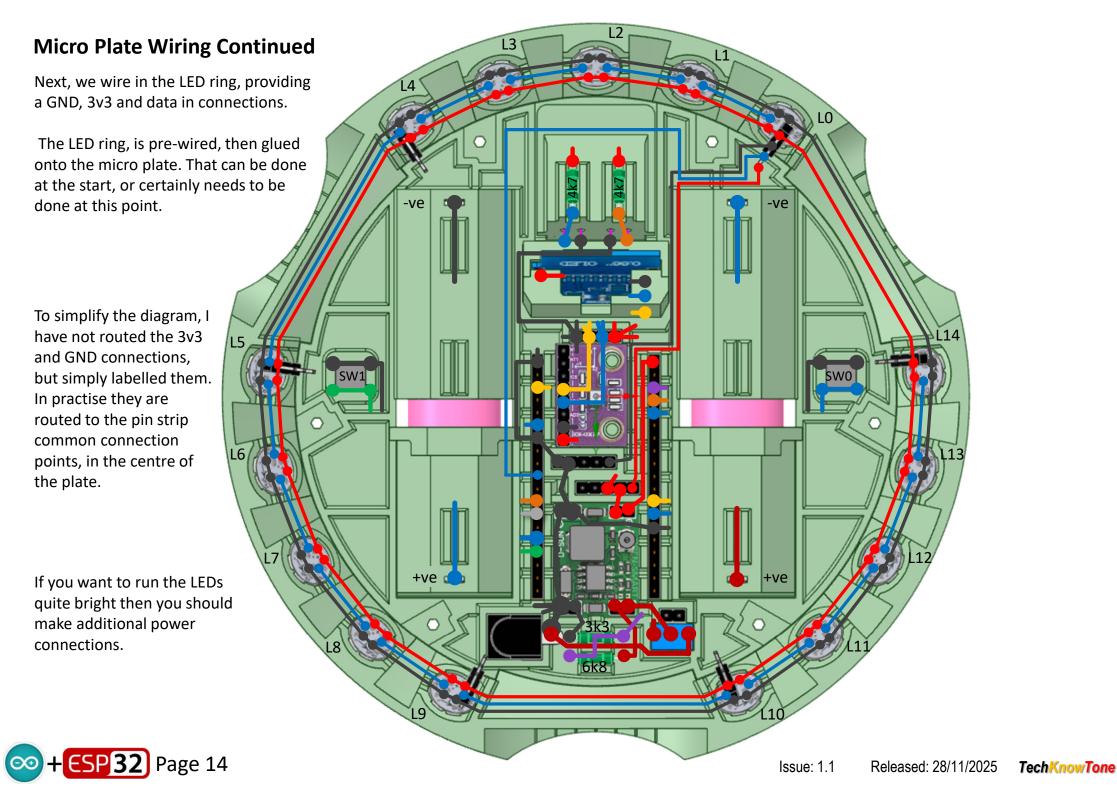Issue: 1.1 Released: 28/11/2025 **TechKnowTone**



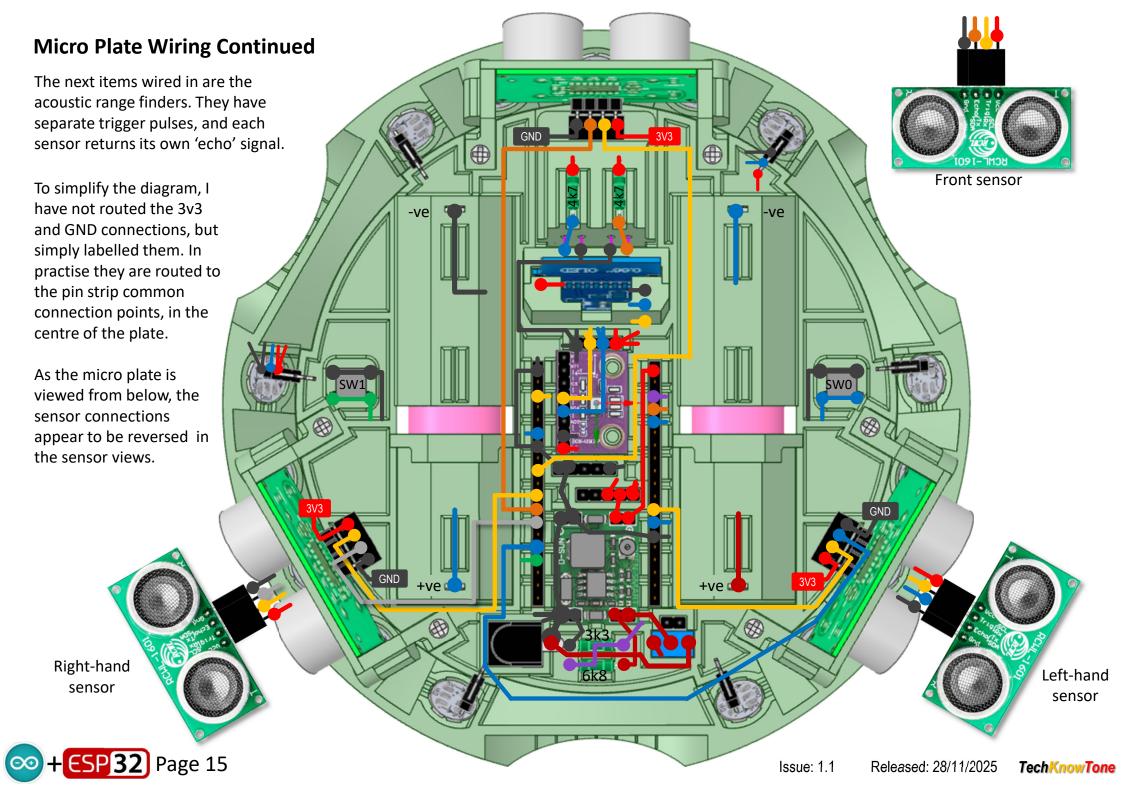


Micro Plate Wiring Continued


The harness, made for the chassis wiring, is now flipped over, left to right, and placed within the micro plate, so that the power connections can be made to the voltage regulator, and the GPIO PWM wires can be wired onto the micros pin strip connections.


In this diagram, the 6-pin sockets appear to be facing away from view, but in practise they would be facing towards you; and the chassis plate, were it in place.


The micro plate and its wiring appear as a faint background image, in order to make the chassis wiring clearer.

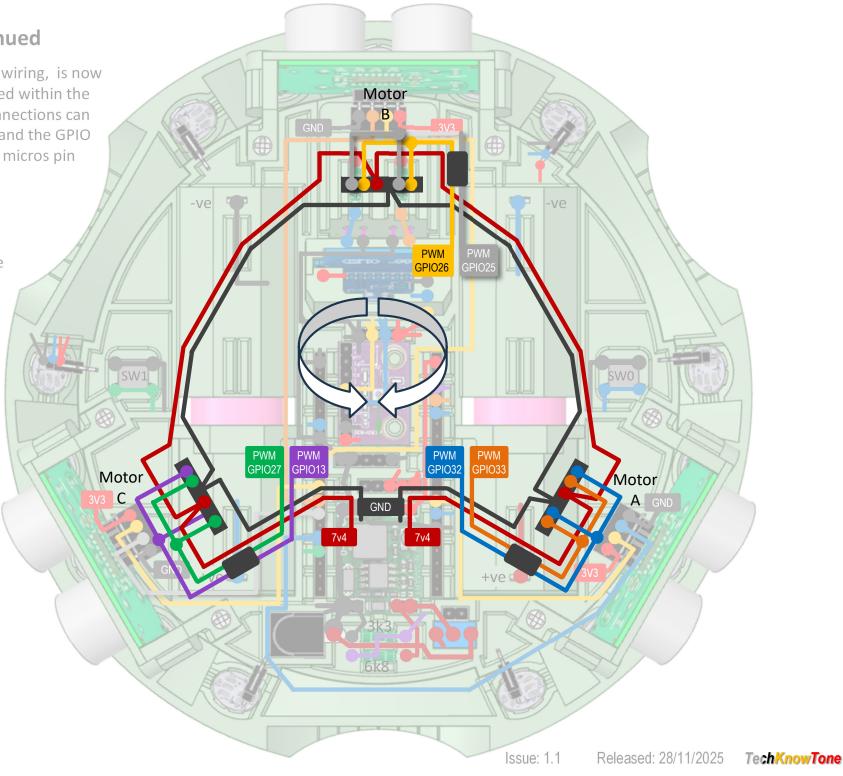
Making these connections, completes the wiring process, and the Omni-Bot is ready for testing, with the full version of code loaded.




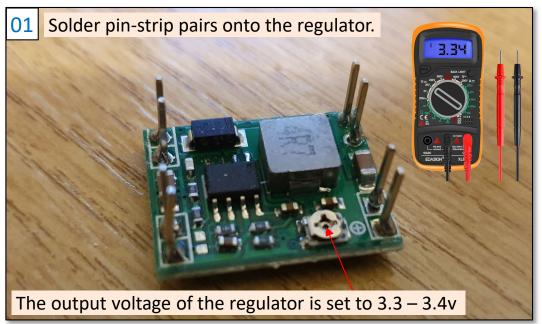


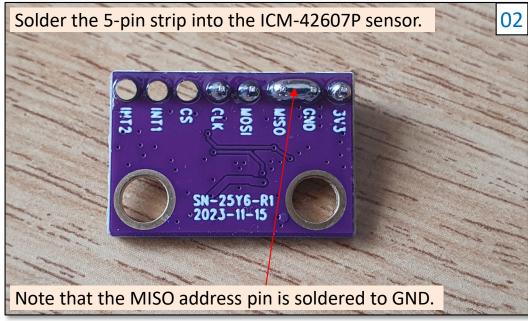


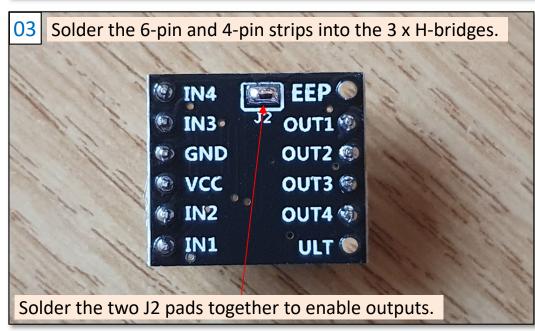


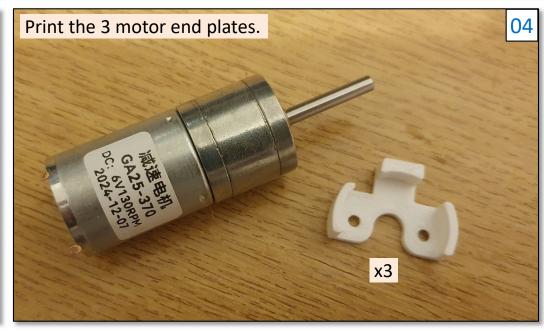


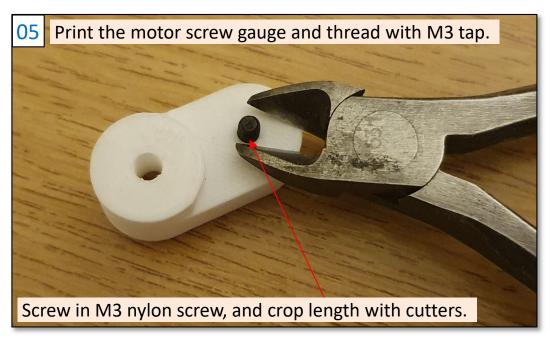


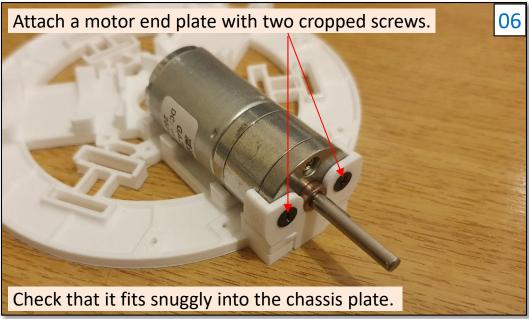


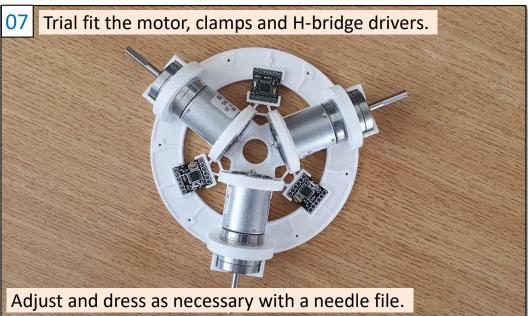


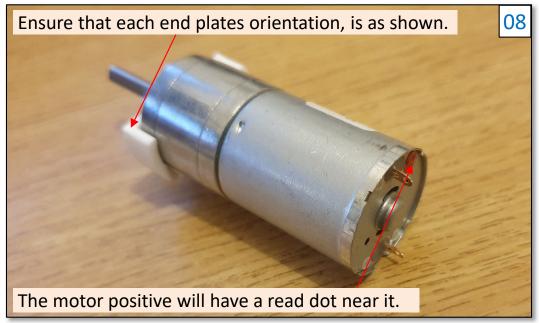

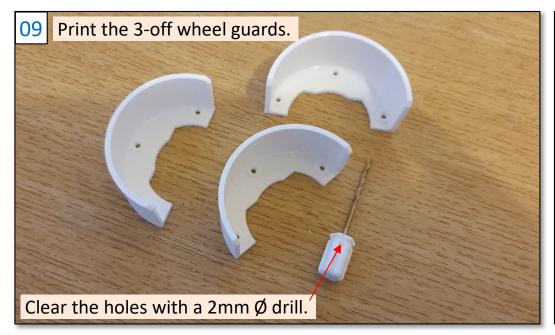


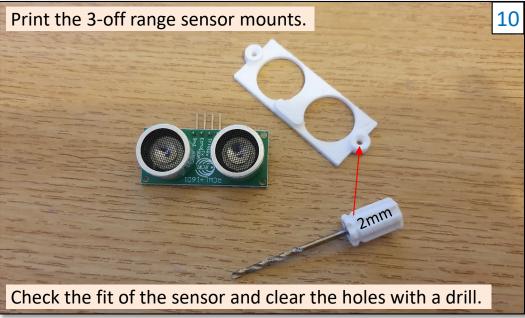


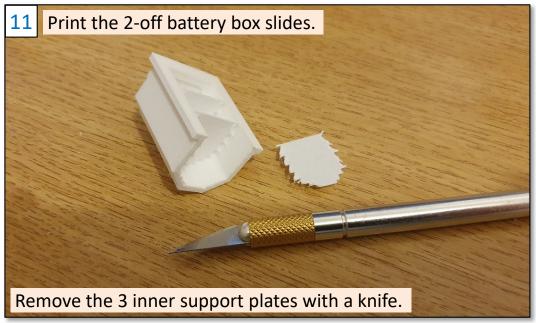


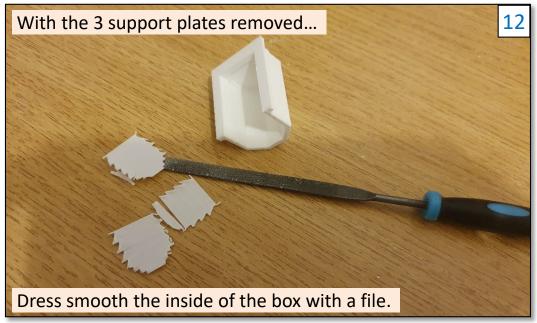


Issue: 1.1

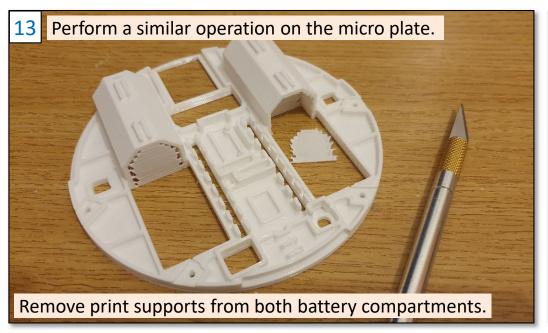


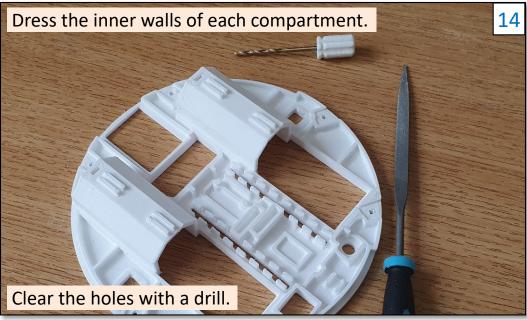


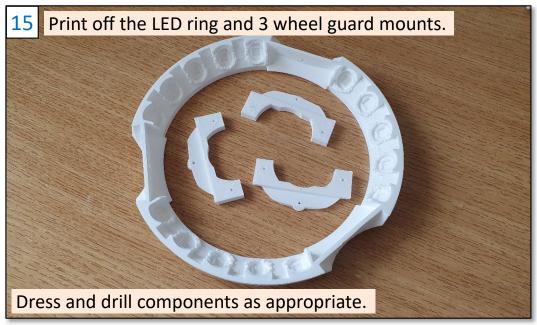





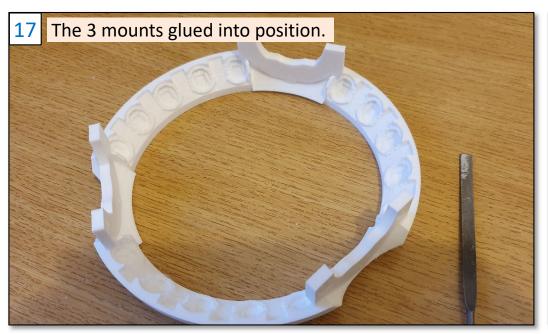

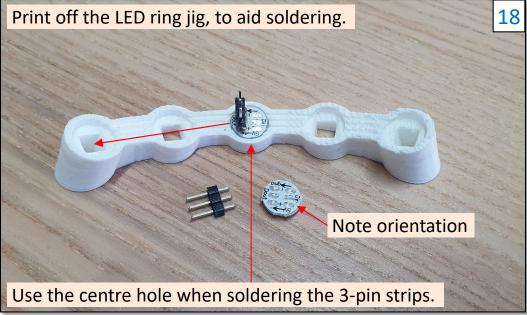


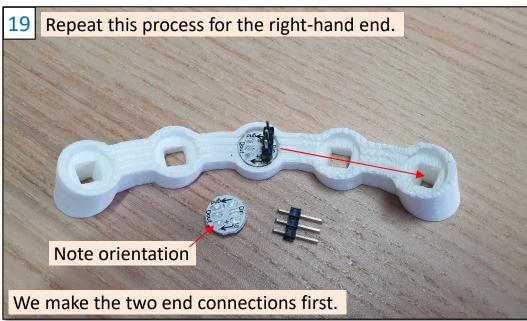


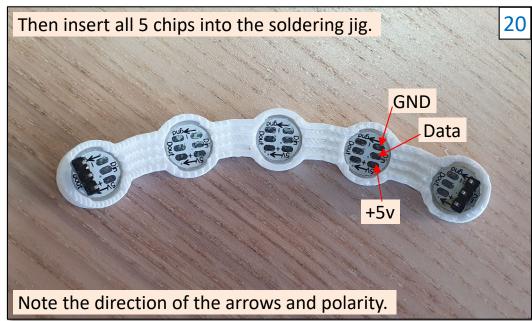


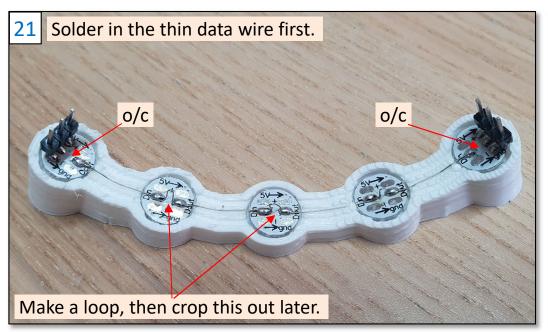





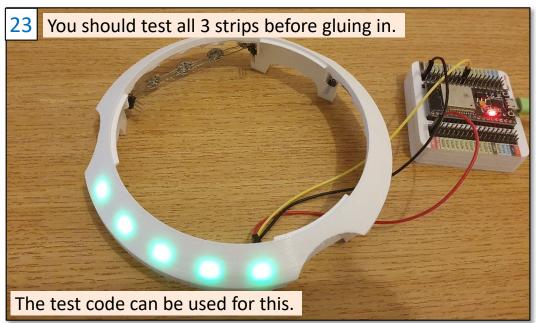


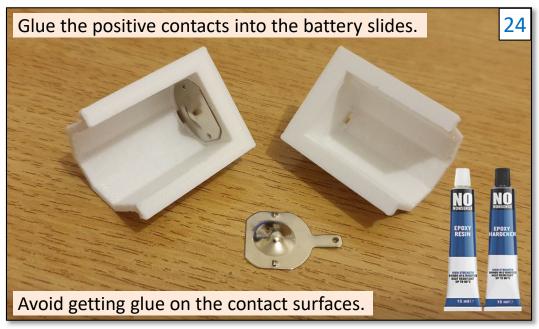


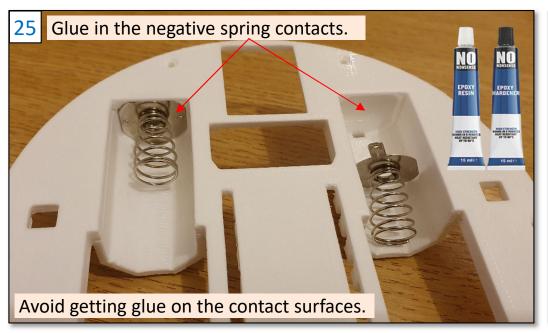


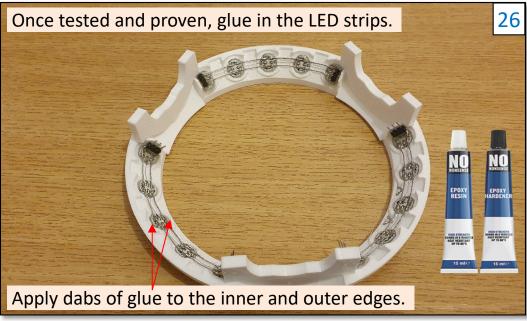


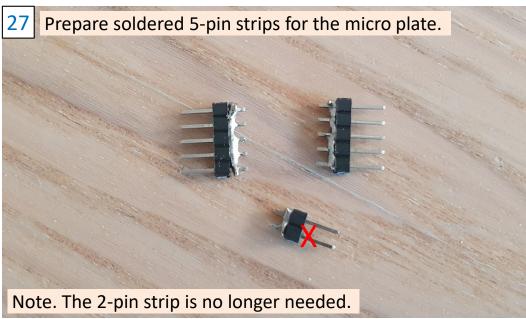


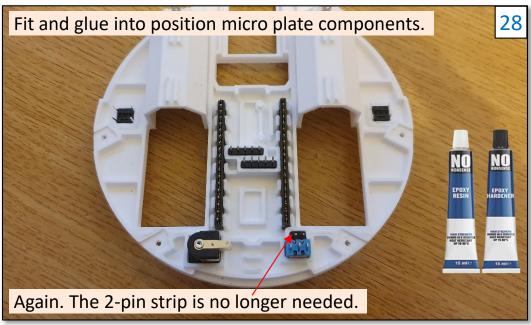


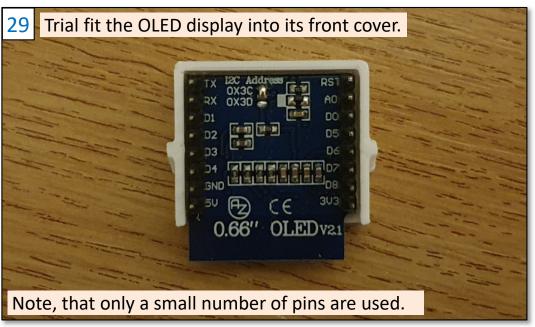

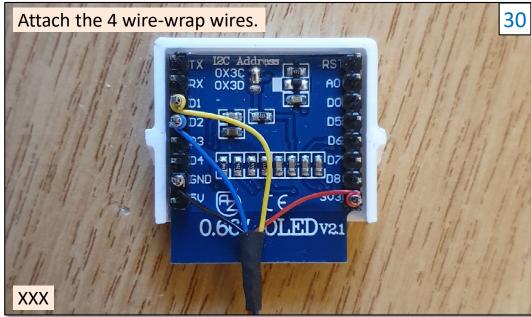


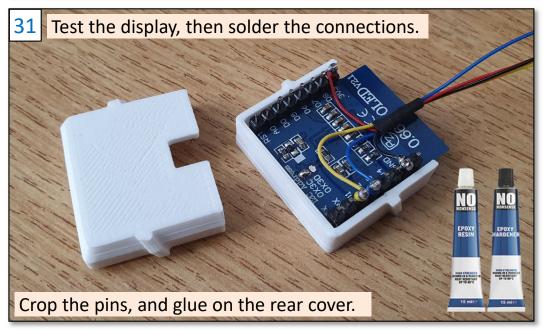


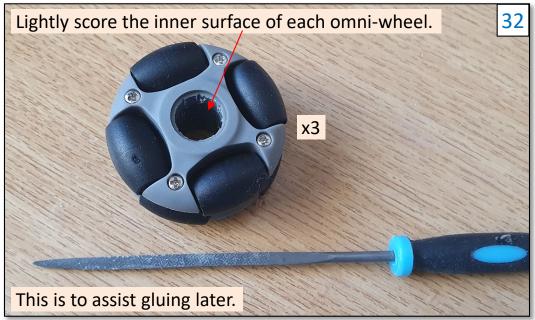


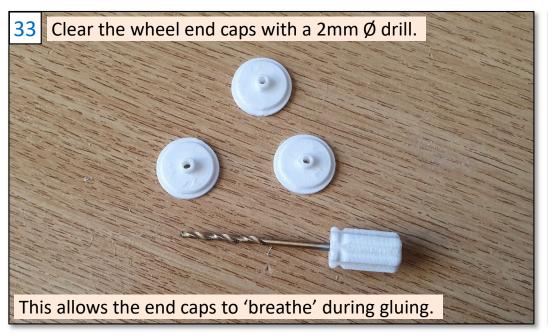





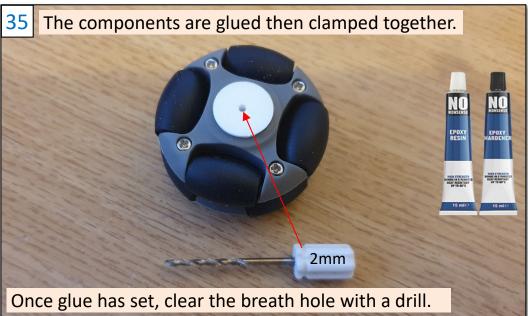


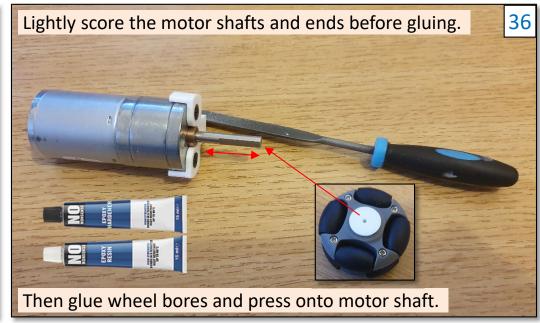


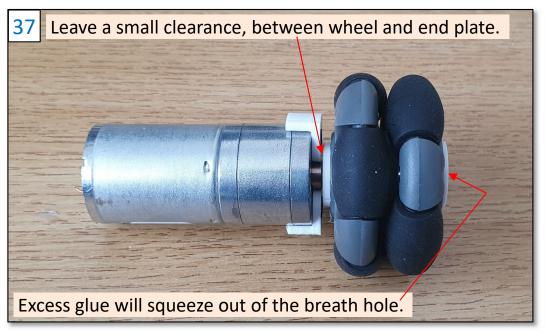


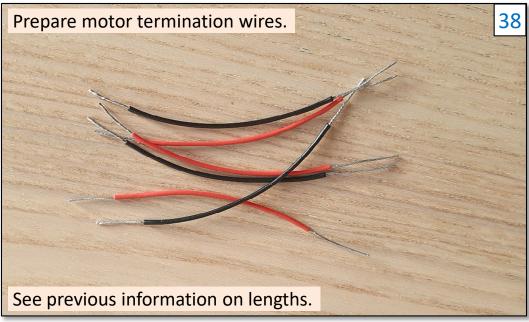


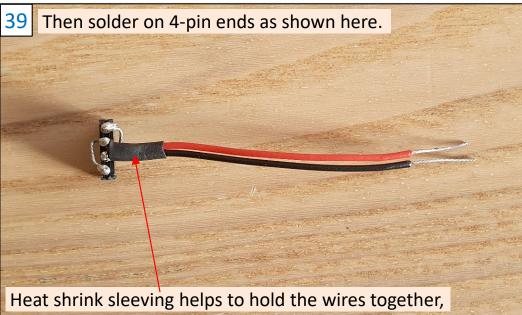


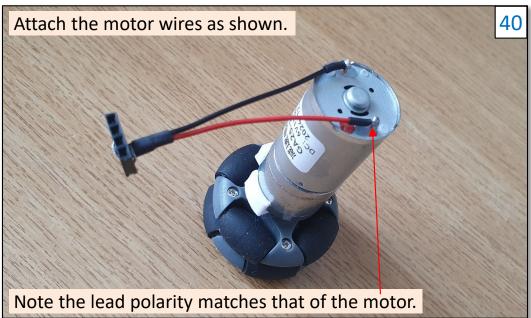


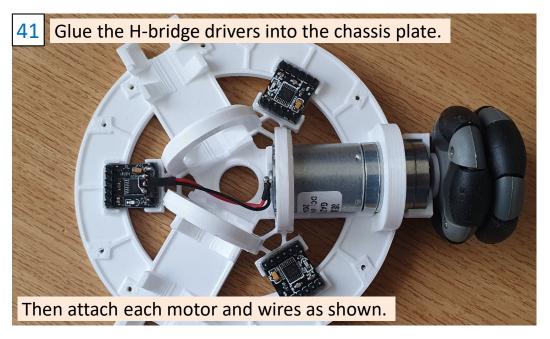


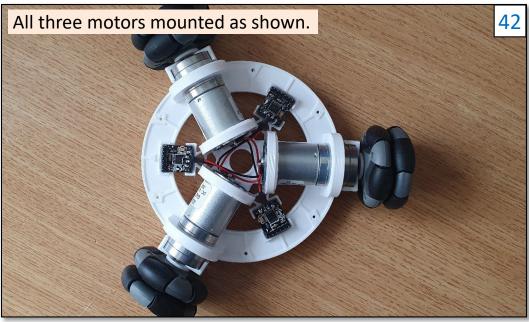


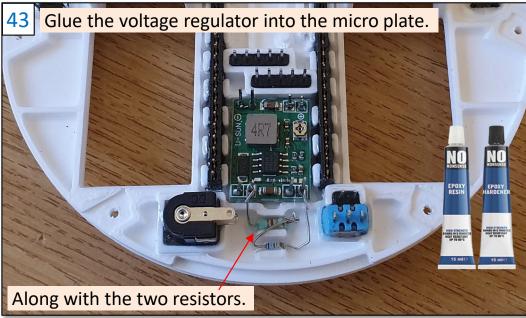


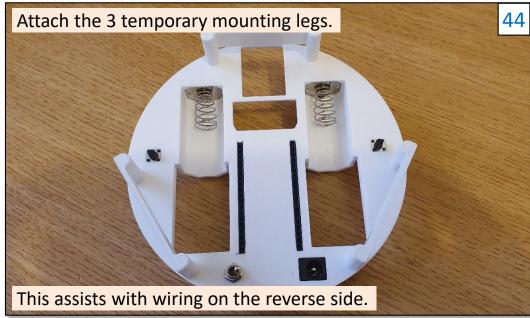


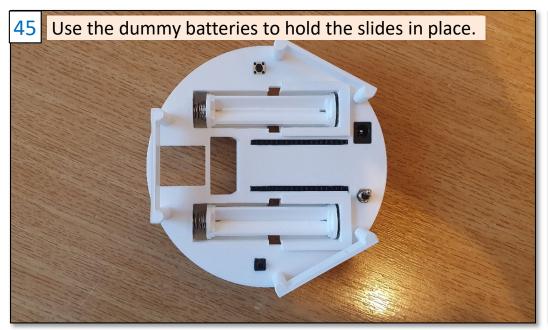


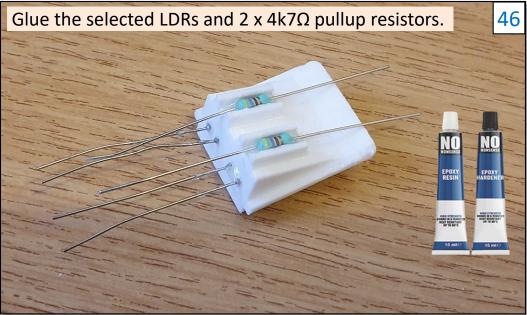


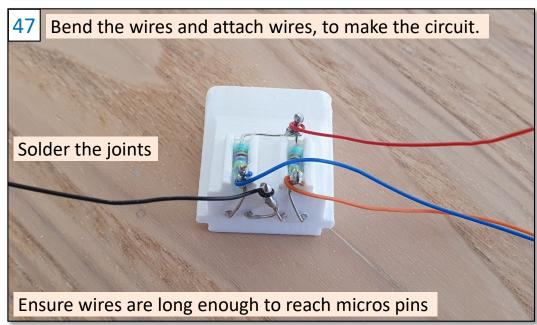


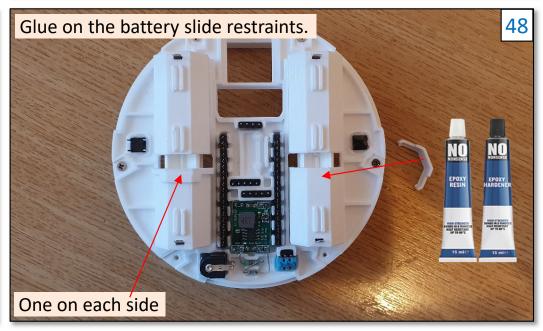

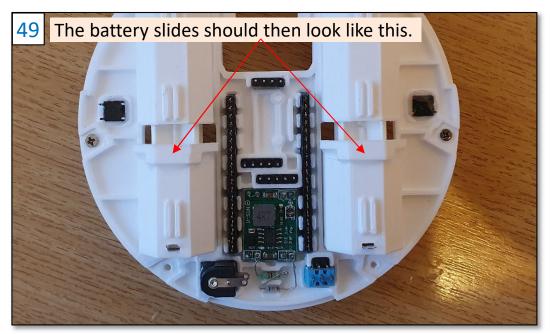


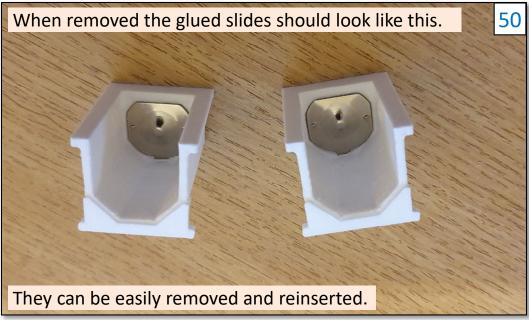

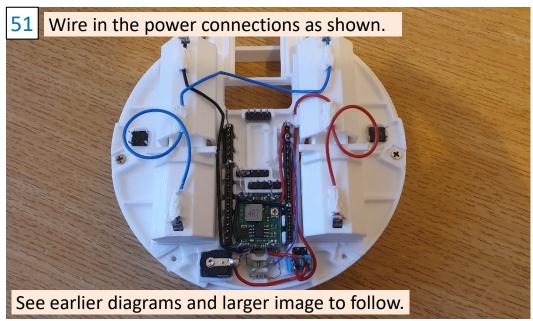


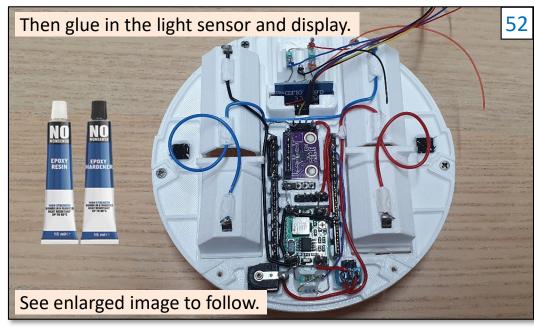


Issue: 1.1

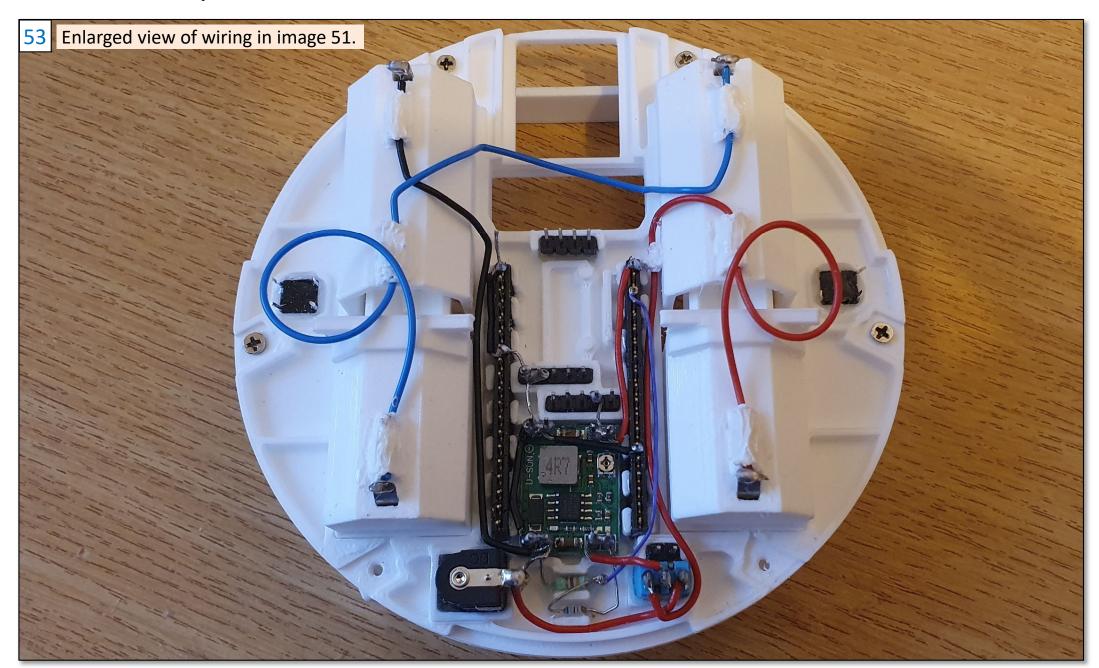



Released: 28/11/2025

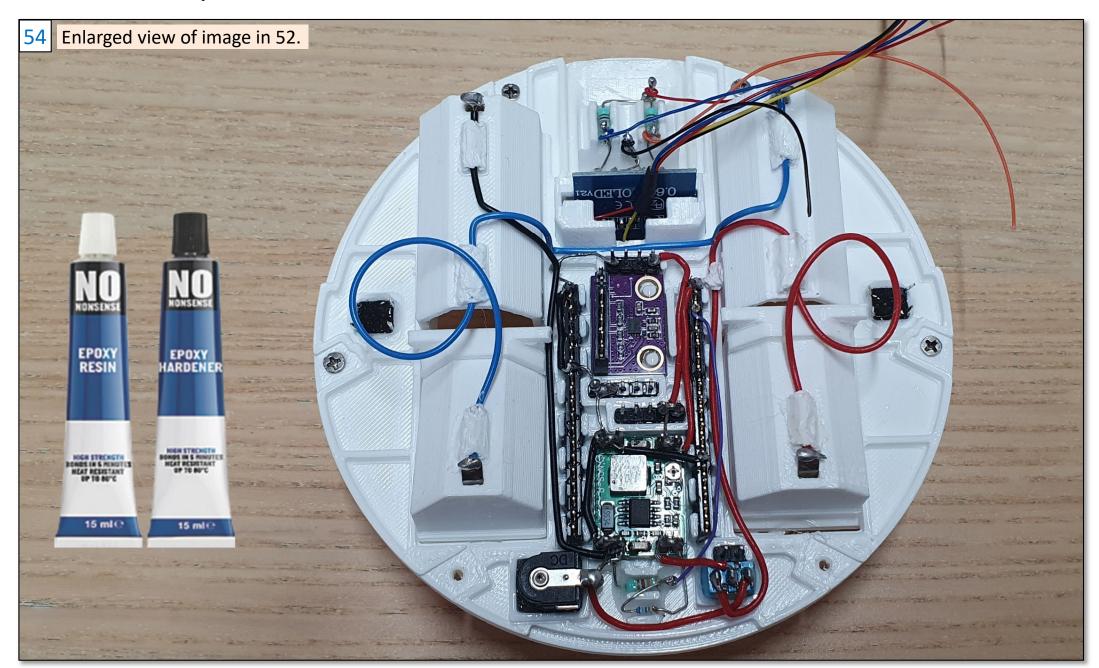



Released: 28/11/2025

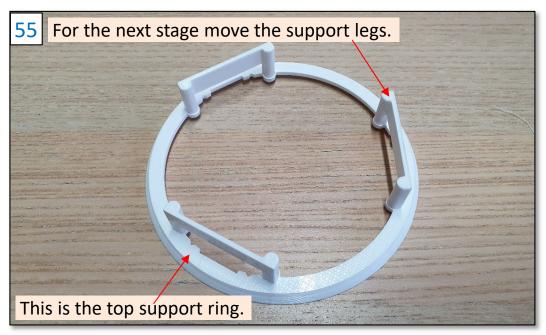

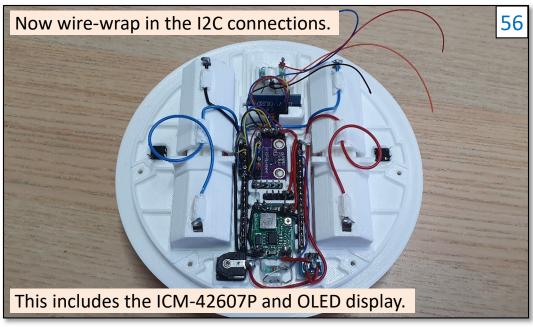

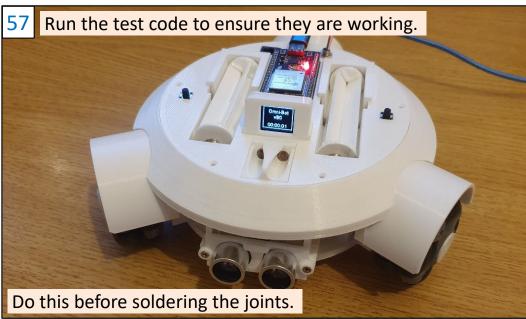


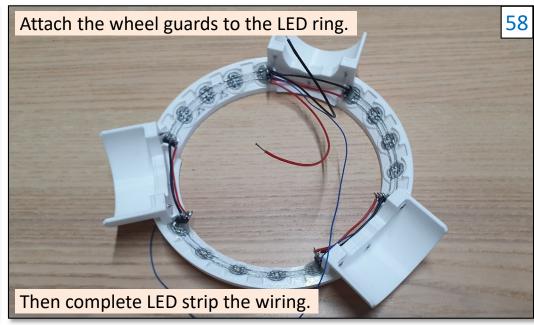

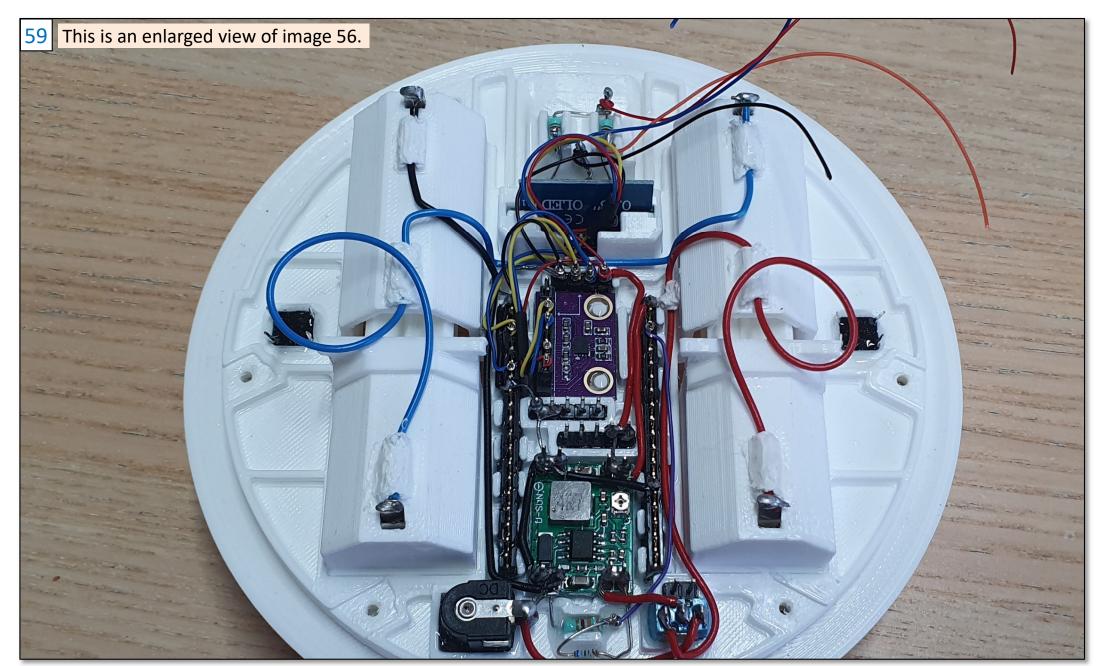






Released: 28/11/2025

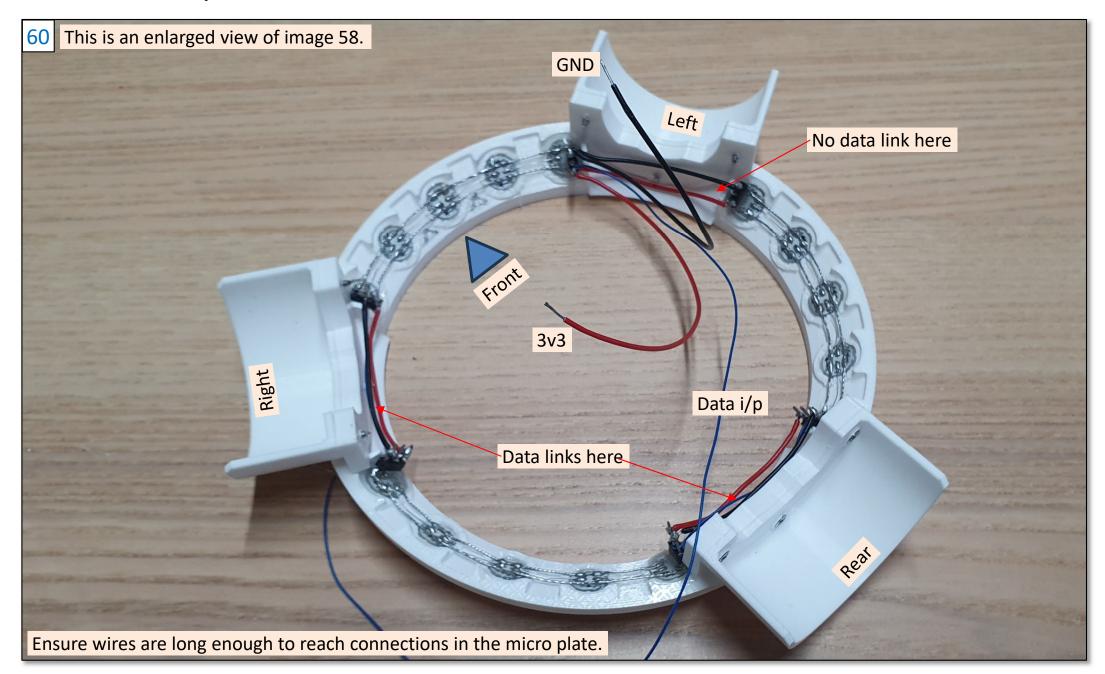



Released: 28/11/2025

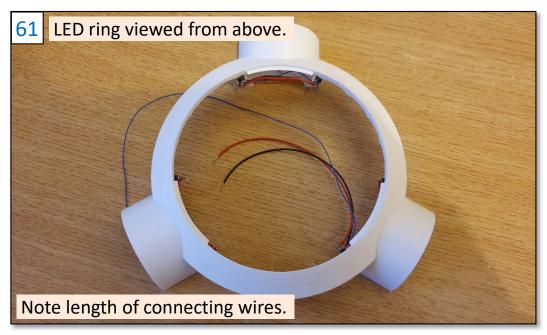

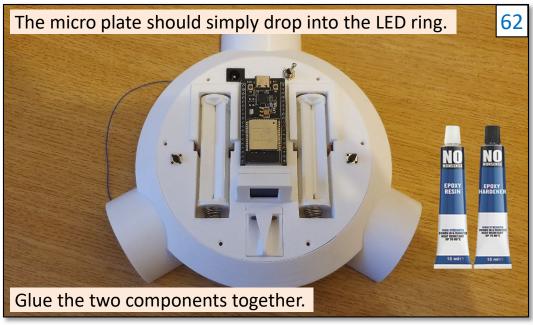


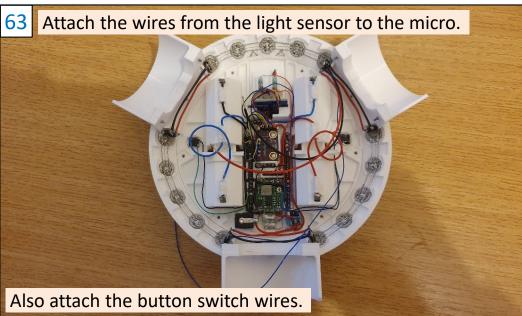


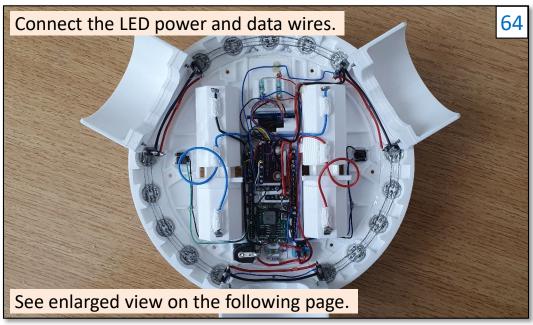


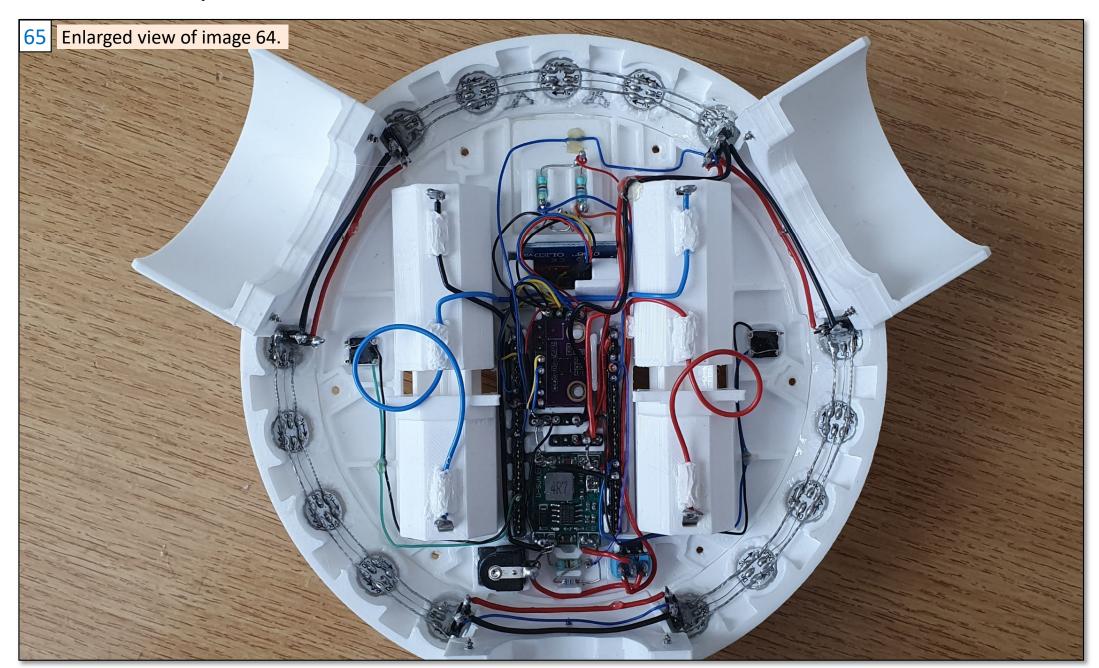



Released: 28/11/2025

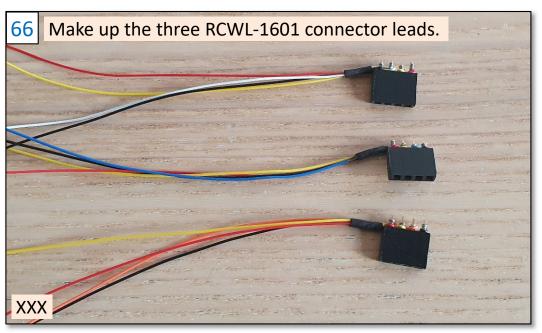

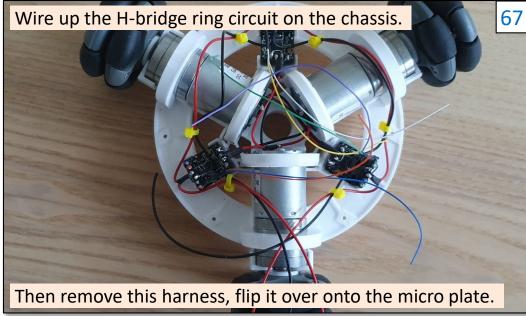


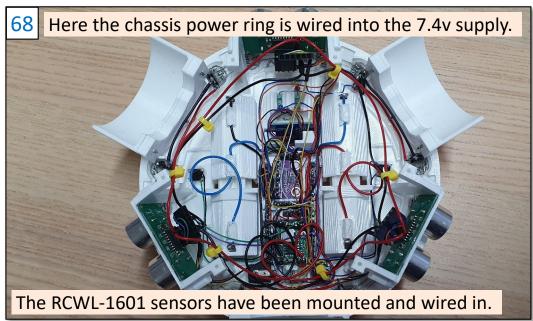


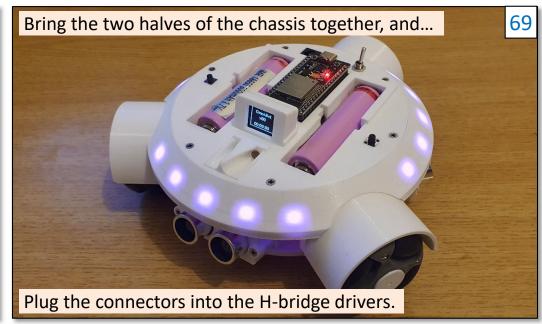

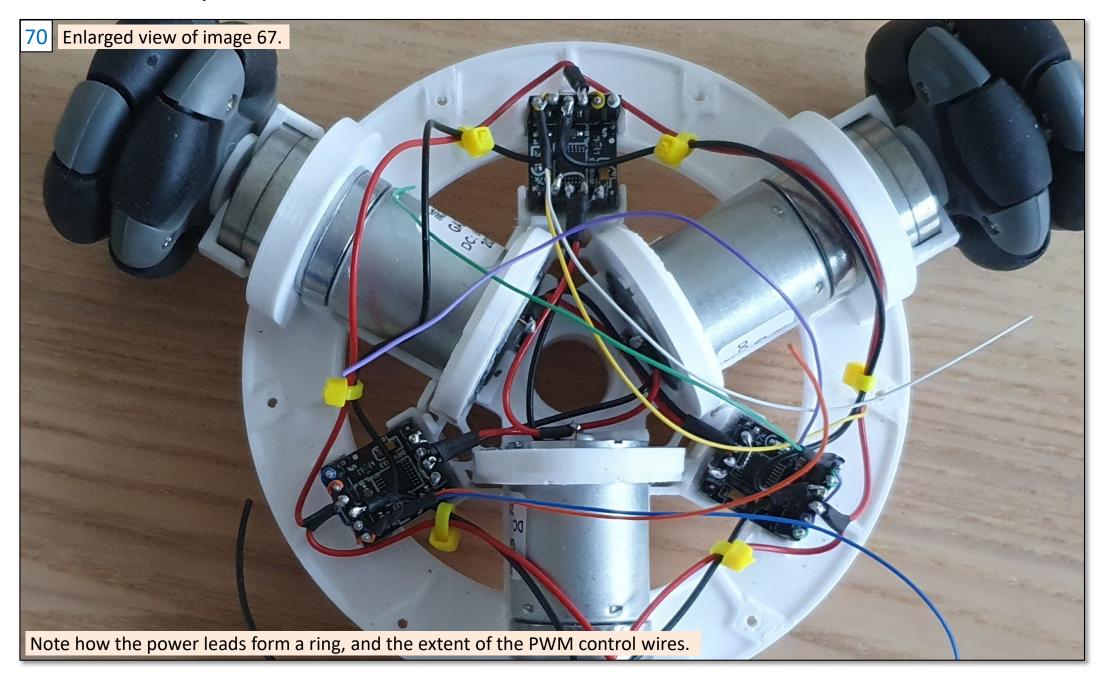



Released: 28/11/2025

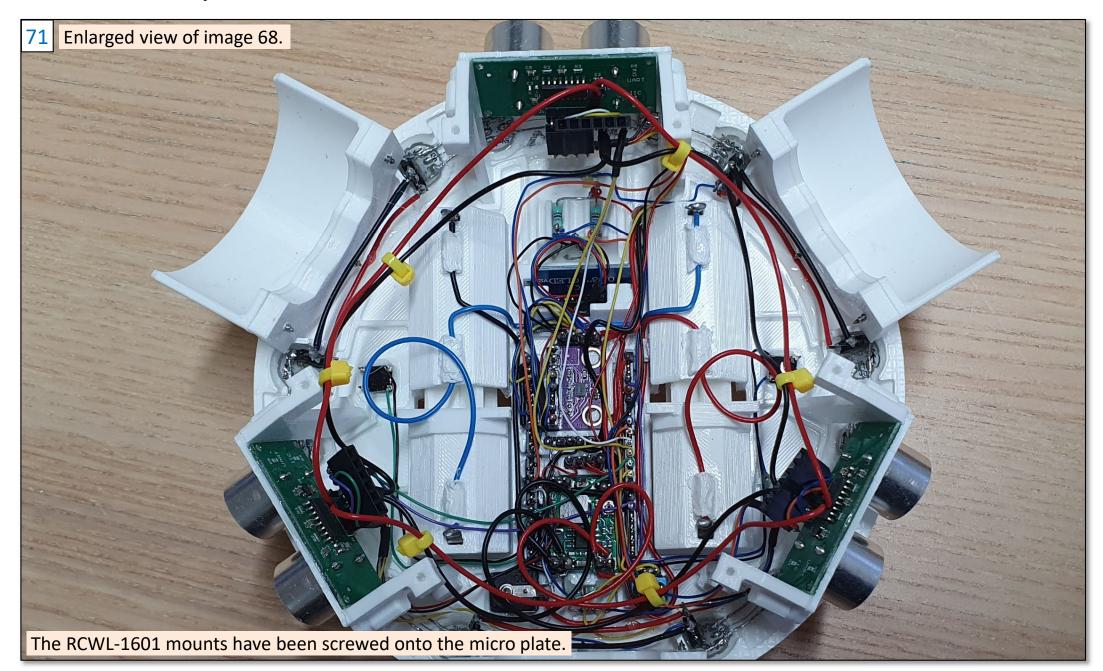

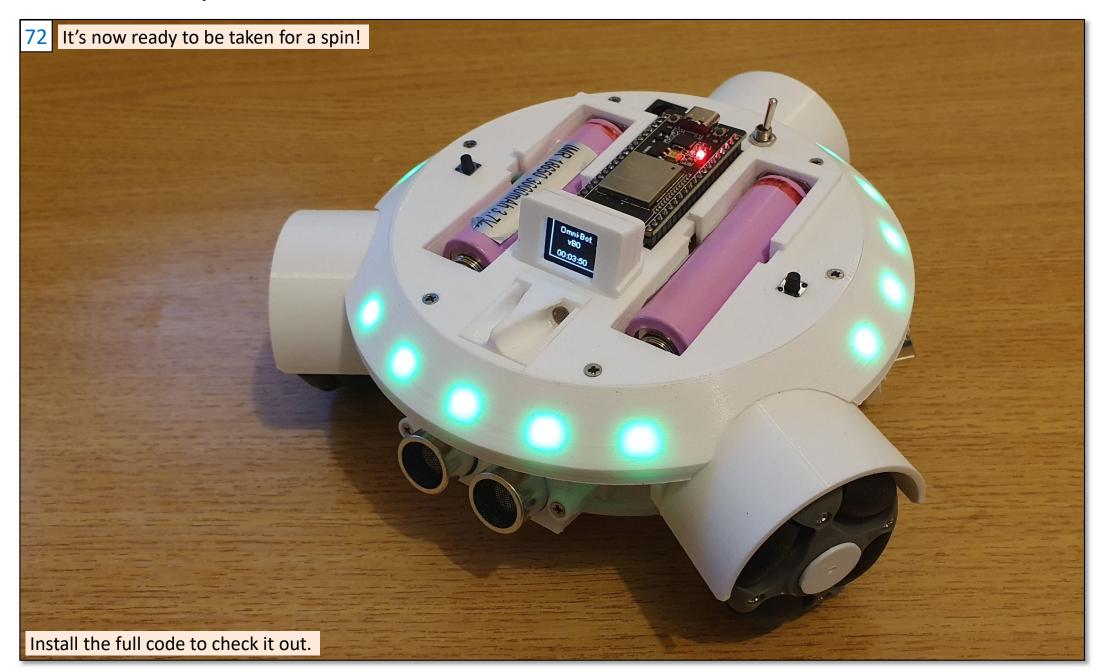

Released: 28/11/2025

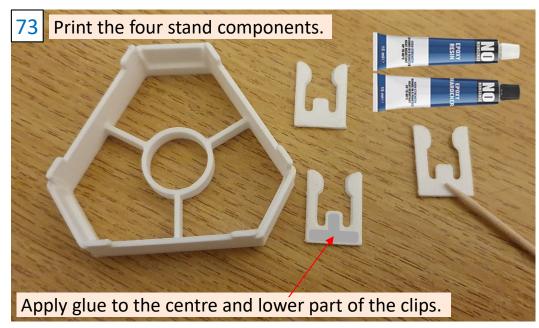

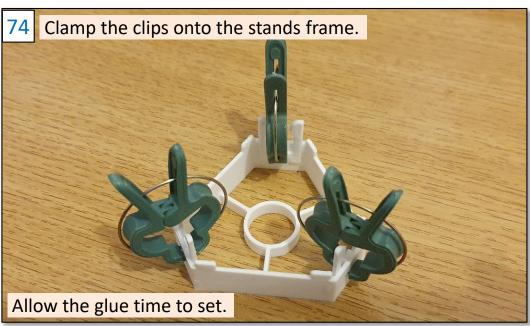



Dual H-bridge Wiring


In this design I used one DRV8833 H-bridge dual channel controller for each motor, and combined each channels 2A max current capability, and halved their MOS-FETs on-channel resistance. Giving a more efficient drive signal for each motor.

This is achieved by wiring the controllers as shown here. Both the input pins and output pins are connected together as shown. Make sure that you wire the controllers correctly, or you are likely to damage the controller, and draw excessive current from the batteries.


The nSLEEP and nFAULT pins are not connected; however, the nSLEEP pin is pulled HIGH by an on-board $47k\Omega$ resistor when you bridge J2 with a blob of solder, as shown. Do this **first**, before soldering in the pin strips to the boards.

You will find more information on the DRV8833 driver on a later slide. This should enable you to understand how the code producing the PWM signals in the ESP32, controls the motion of the DC motor. For each direction of travel, one PWM input pin is held HIGH, whilst PWM signals are applied to the other.

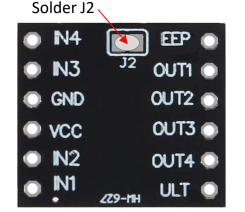As the supply voltage affects motor speed and torque, the code monitors the battery voltage and adjusts the applied PWM to give a maximum average voltage of 7.6v.






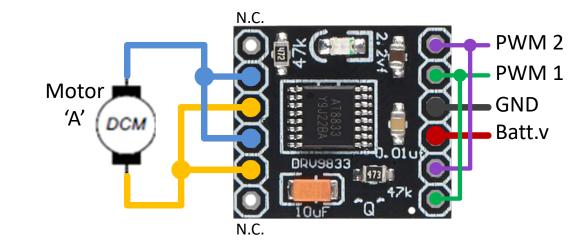





CAUTION – This design does not include any form of current limiting protection (like a fuse). Incorrect wiring can result in large currents, which can cause damage and even the risk of a **fire**. Check and double check your wiring before inserting the batteries.

DRV8833 H-bridge Driver

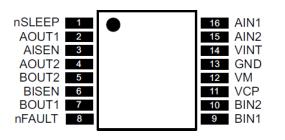

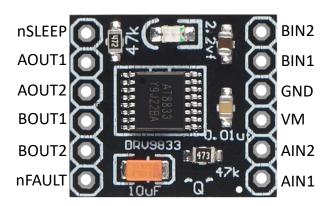

Combined H-bridge.

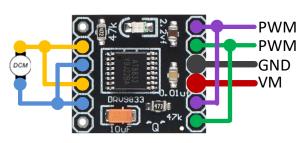


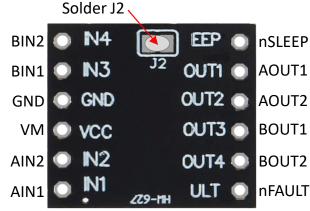


Table 1. H-Bridge Logic

xIN1	xIN2	xOUT1	xOUT2	FUNCTION
0	0	z	Z	Coast/fast decay
0	1	L	Н	Reverse
1	0	Н	L	Forward
1	1	L	L	Brake/slow decay

Table 2. PWM Control of Motor Speed

		_
xIN1	xIN2	FUNCTION
PWM	0	Forward PWM, fast decay
1	PWM	Forward PWM, slow decay
0	PWM	Reverse PWM, fast decay
PWM	1	Reverse PWM, slow decay

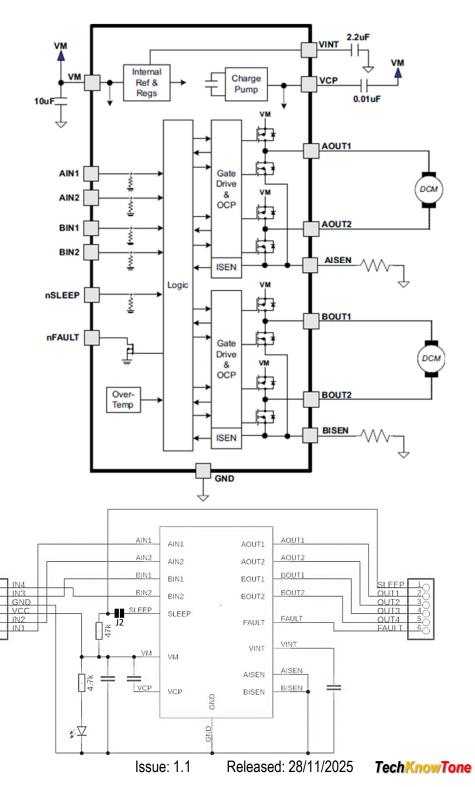



Motor Control Testing

The Omni-Bot code included commands that can be sent over the serial interface, either directly from the Arduino IDE or via a custom Windows app. The 8-Channel Controller app uses the serial interface to send these commands.

The DRV8833 H-bridge dual channel drivers, one for each motor, each receive two PWM control signals from the micro. Hence the 8-Channel controller groups these channels into four pairs; A0 & A1, B0 & B1, C0 & C1 and D0 & D1. In this application we only require the first three pairs and ignore the D channels.

The app presents sliders for each of the PWM channels, ranging from 0 to 255 in value. Simply click on a channel reference (like A0) to enable/disable a channel pair. Then move the sliders to send commands to the OMNI-Bot. The wheel motors should respond to these changes, and turn in an appropriate direction.

Note that the controller logic assumes one channel will be held at either LOW (0) or HIGH (255), whilst the other channel is in the range 0-255. The app slider logic therefore does not allow simultaneous use of both channels. So, one slider must be at its extremes, whilst the other is somewhere in the middle of its range.

You can experiment with values, to look at things like direction of motor rotation, and minimum PWM start values.










Sensor Features

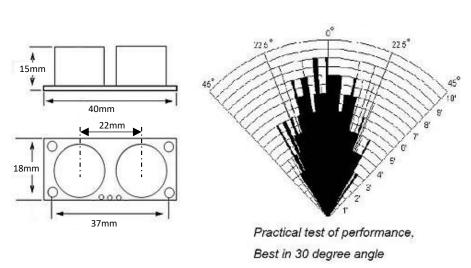
- Low cost < £2.00
- Low power 2.2mA static current
- 8 cycle 40 kHz sound burst
- Detection range 2cm 450cm
- Sensor angle 15 degrees
- High precision +/- 3mm
- Easy to use?
- Provide 10µs HIGH trigger pulse
- Measure width of returned 'Echo' pulse



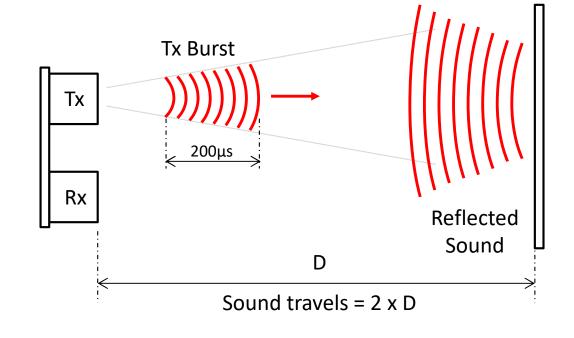

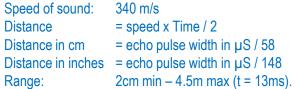



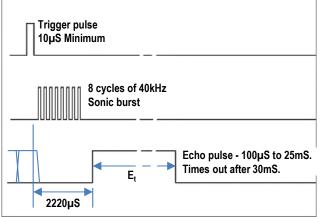

Echo pin state is undefined prior to triggering. Code looks for positive edge, to time $E_{\rm t}$. Practical measurements up to 400mm take 5ms.



Battery Voltage Calibration

See Lithium discharge curve obtained from the internet. In this analysis the lipo battery consists of two identical batteries connected in series.

Assume fully charged 8.2v battery max voltage is $V_{BM} >= 8.4v$ max (charging)

Set battery warning point at $V_{BW} = 7.2v (2 \times 3.6v)$

Set battery critical point at $V_{BC} = 6.6v (2 x3.3v)$

The ESP32 is powered via a 5v voltage regulator, connected to the V_{in} pin, but the 6k8 supply sampling resistor is connected to source V_{Batt} .

For ESP32 $V_{ADC} == 4095$ on 12-bit converter (4095 max).

If we use a 6k8 resistor feeding A0 and a 3k3 resistor to GND, we get a conversion factor of 10.1v == 4095, or 2.47mV/bit, or 405.4 bit/v

Using a Multimeter and a variable DC supply, I determined the following V_{ADC} values for corresponding threshold voltages:

MAX. O.C $V_{OC} = 8.4v$, gave A0 = 3226 On V_{ADC} (2 x 4.2v)

MAX: (100%) $V_M = 8.2v$, gave A0 = 3136 on V_{ADC} (2 x 4.1v)

HIGH: (80%) $V_H = 7.6v$, gave A0 = 2872 on $V_{ADC}(2 \times 3.8v)$


WARNING: (20%) $V_{BW} = 7.2v$, gives A0 = 2710 on V_{ADC} (2 x 3.6v)

CRITICAL: (0%) $V_{BC} = 6.6v$, gives A0 = 2460 on V_{ADC} (2 x 3.3v)


The code will sample the battery voltage on power-up to ensure it is sufficient, then at every 40ms interval, calculating an average (1/50) to remove noise. It also detects no battery as USB mode.

In the code I have assumed a discharge curve ranging from 8.2v (100%) to 6.6v (0%) capacity, using the overlay lines shown. The rate of discharge is monitored and used to predict the life of the battery in use.

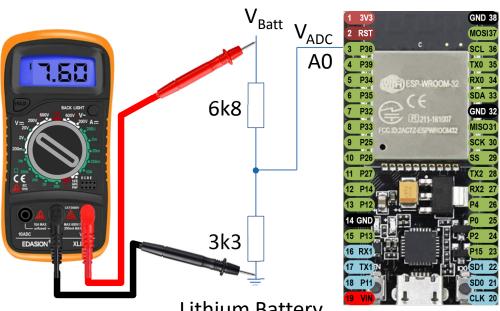Note: If connected to USB port with internal battery switched OFF the ADC will read a value 5 volts (A0 = 1919) or less. So, if the micro starts with such a low reading it knows that it is on USB power.



Lithium Battery
Discharge Profile

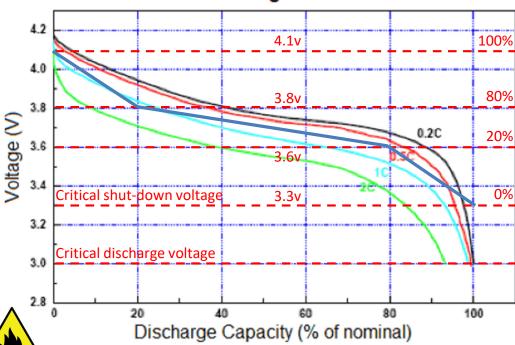

Discharge: 3.0V cutoff at room temperature.

Released: 28/11/2025

TechKnowTone

Issue: 1.1