
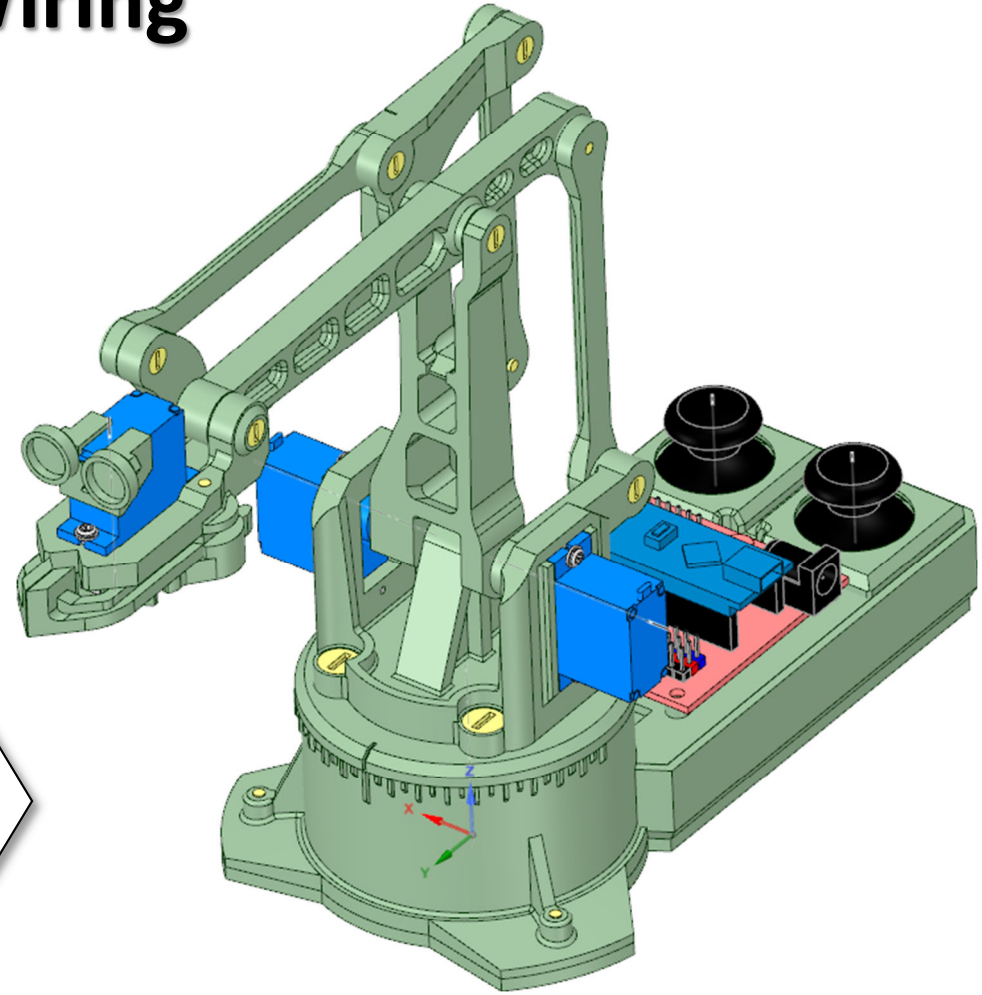


Reach Robot NANO

Circuits & Wiring

Reach Robot NANO Wiring

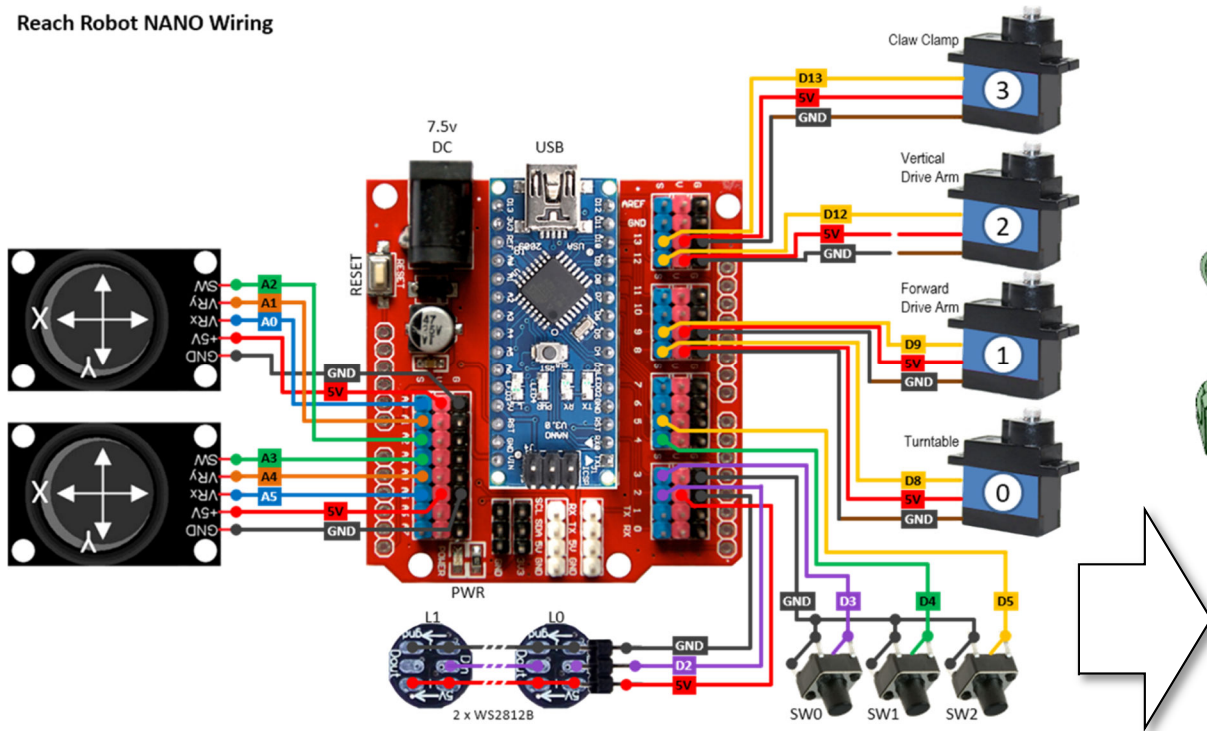

Hand Tools:

Recommended:

- Fine Nosed Pliers
- Side Cutters
- 1.5 mm Drill
- 2.0 mm Drill
- 4.0 mm Drill
- Needle Files
- Screwdrivers
- Craft Knife



Note: Not all items needed are shown here.


Tools & Materials:

- Temperature controlled iron
- Solder flux
- Resin cored solder
- Hot melt glue gun
- 2-part epoxy resin glue
- Screw drivers
- Wire wrapping tool
- Wire wrapping wire 30 AWG
- 24 AWG stranded wire (red & black)



Reach Robot NANO Wiring


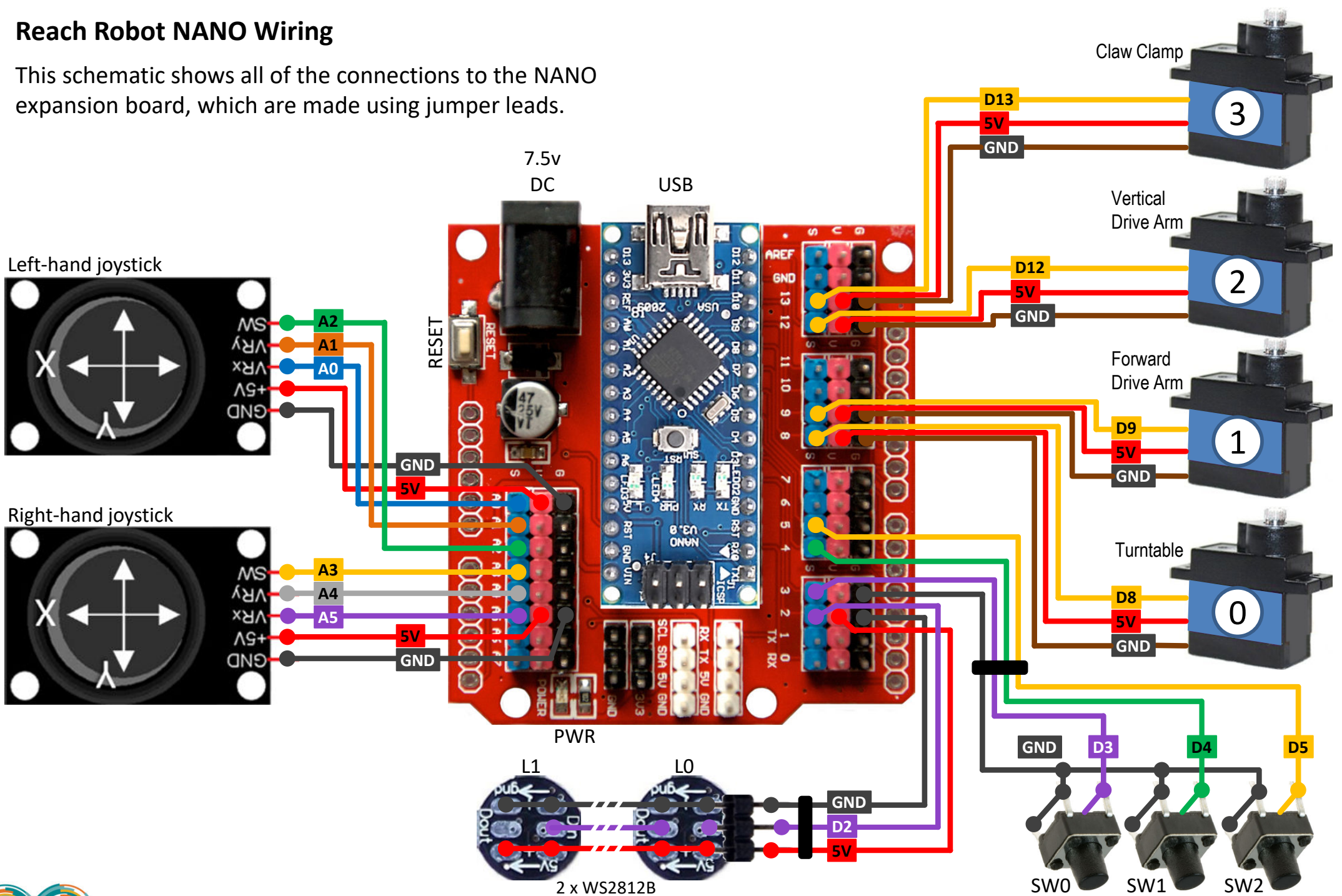
This schematic shows all of the connections to the NANO expansion board, which are made using jumper leads.



Base Wiring



The three button switches are wired to a 6-pin strip (end pins removed). Jumper wires can then be used to connect to the NANO expansion board.

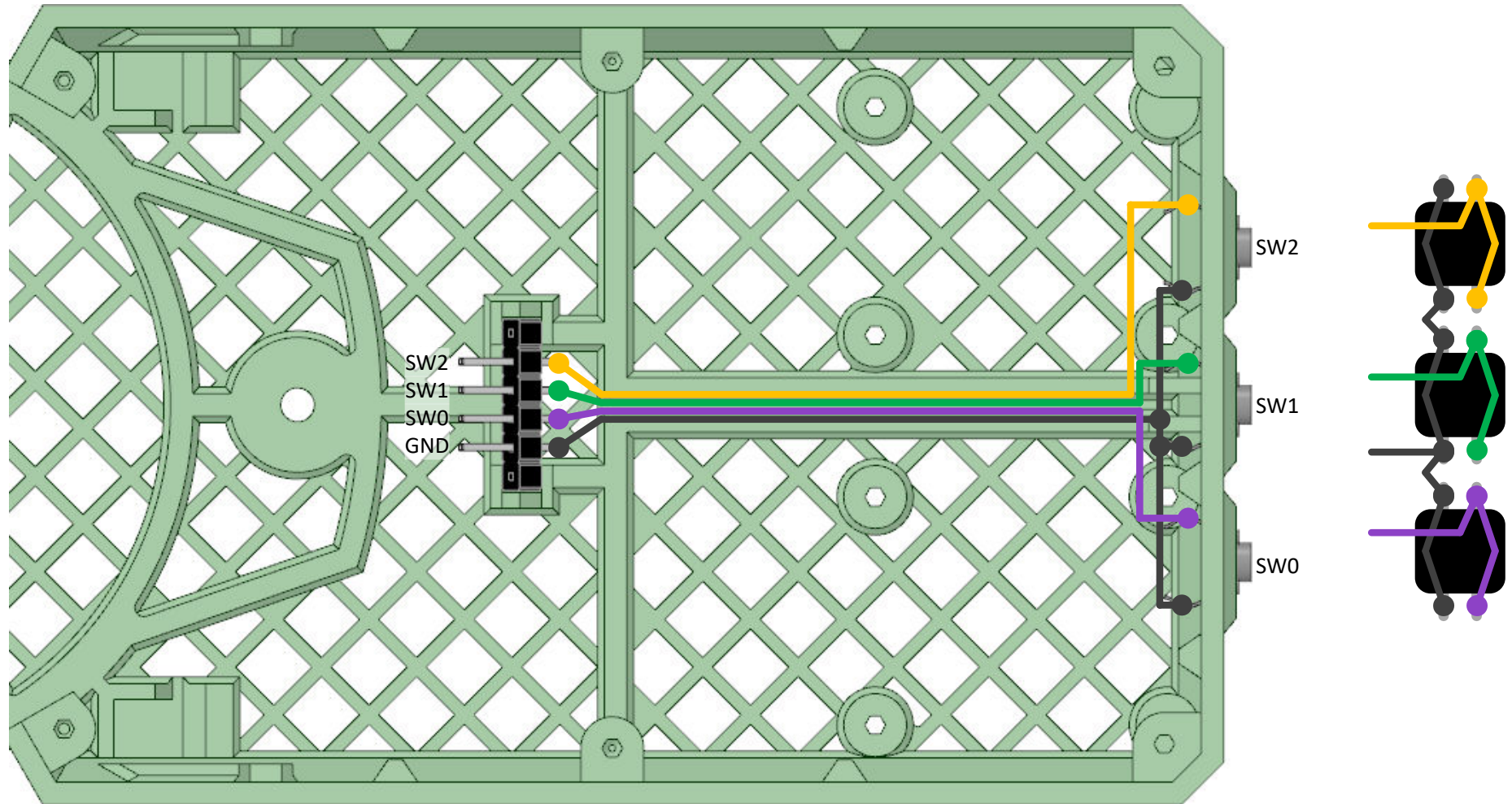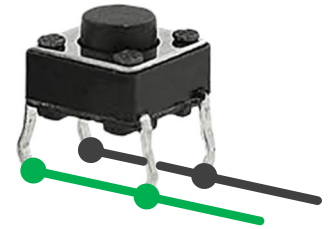Button switch connections are like two staples, so they are wired like this.





WS2812B Wiring

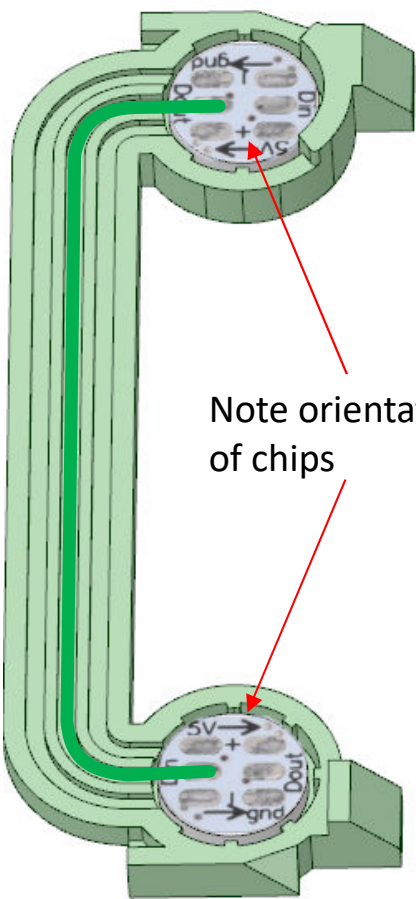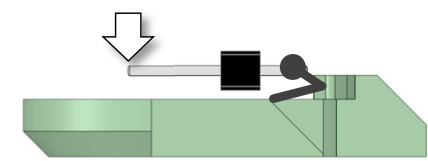Follow this sequence to complete the WS2812B mount:



Note orientation of chips

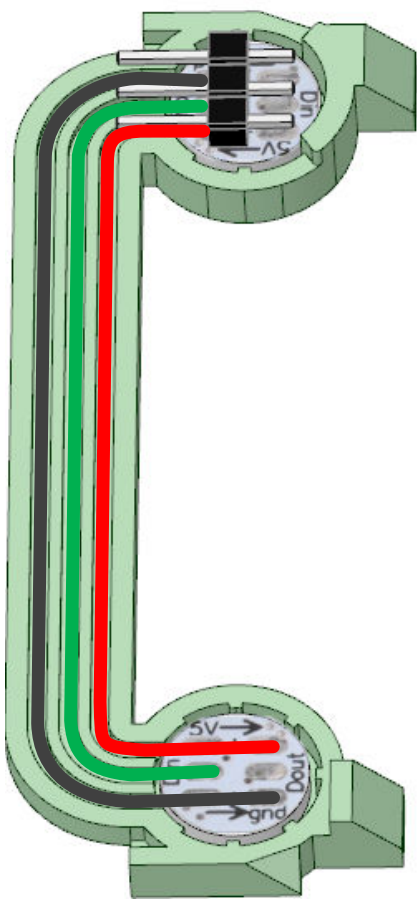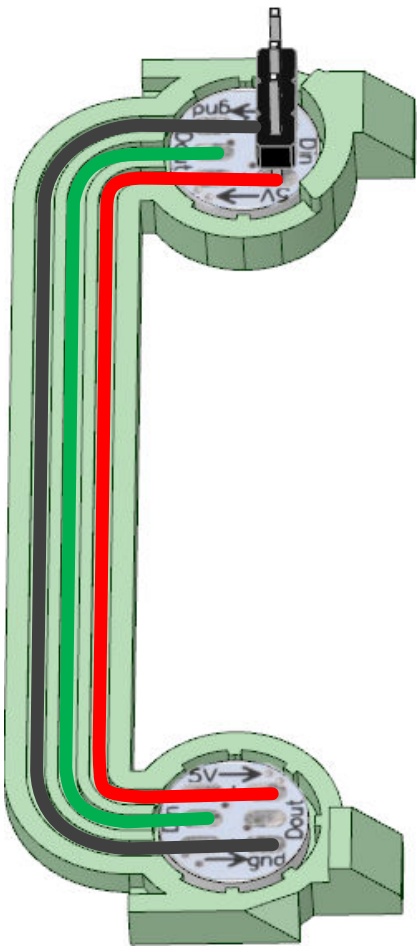

Attach two wires to the outer pins of the 3-pin strip. They don't need to be insulated.


Connect the centre data wire, by soldering it onto the pads. It runs from D_{out} to D_{in} , and fits into the centre of the printed guide rail.

Attach the 3-pin strip and wires as shown, by soldering the wires onto the pads, not the pins onto the pads. See why in next step.

This allows the wires to be bent, as the pin strip is pushed down towards the chip. Once tested apply glue to the 3-pin strip and wires.

Expansion Board Wiring

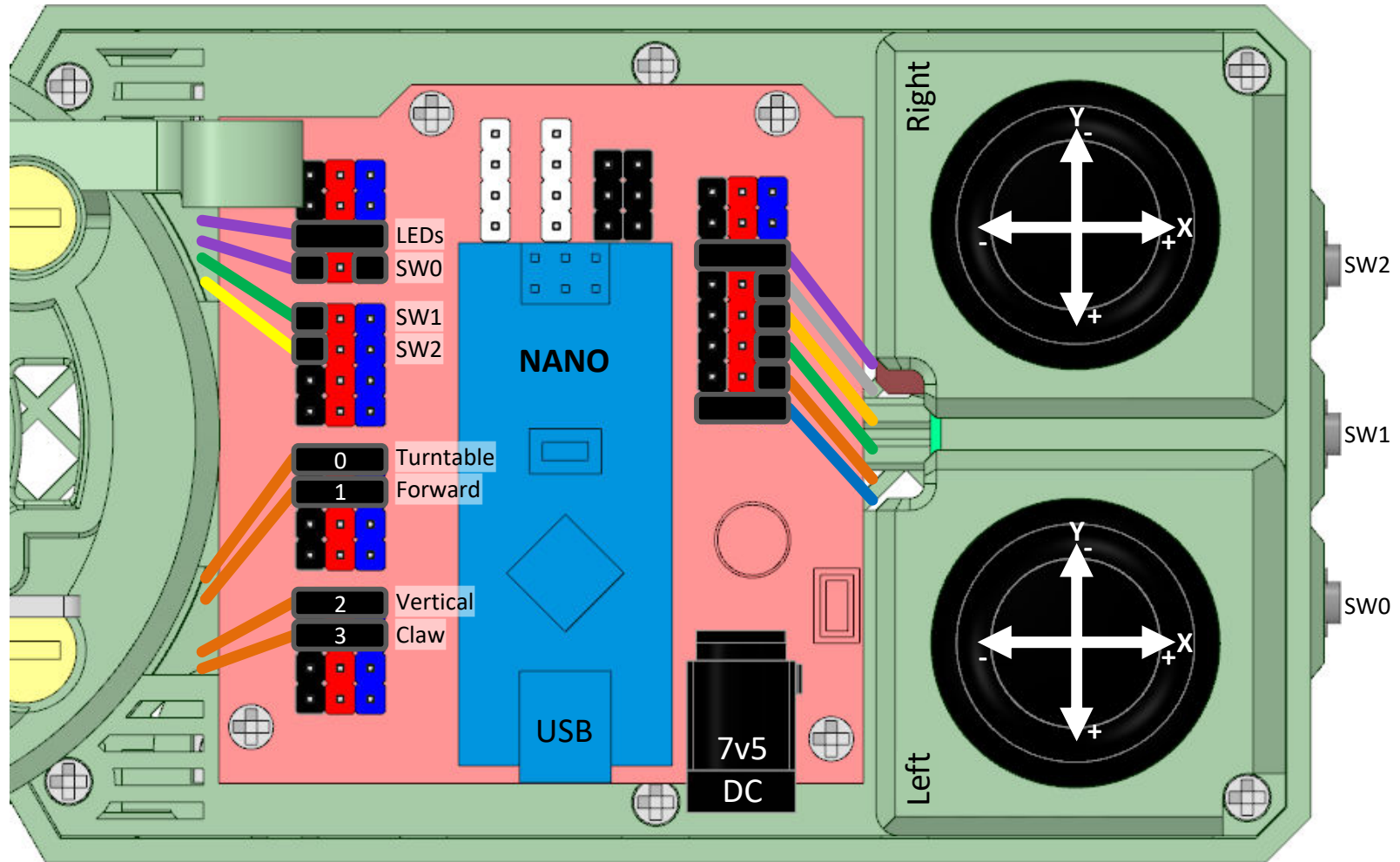
The colour of jumper wires used to connect to NANO expansion board do not need to match this diagram. Use the wiring diagram to determine the connection points.



Note that, due to their orientation, the joystick values are effectively reverse, and one would think of Y direction being X, and vice versa. Your code will need to correct for this.

Photos From Wiring Sequence

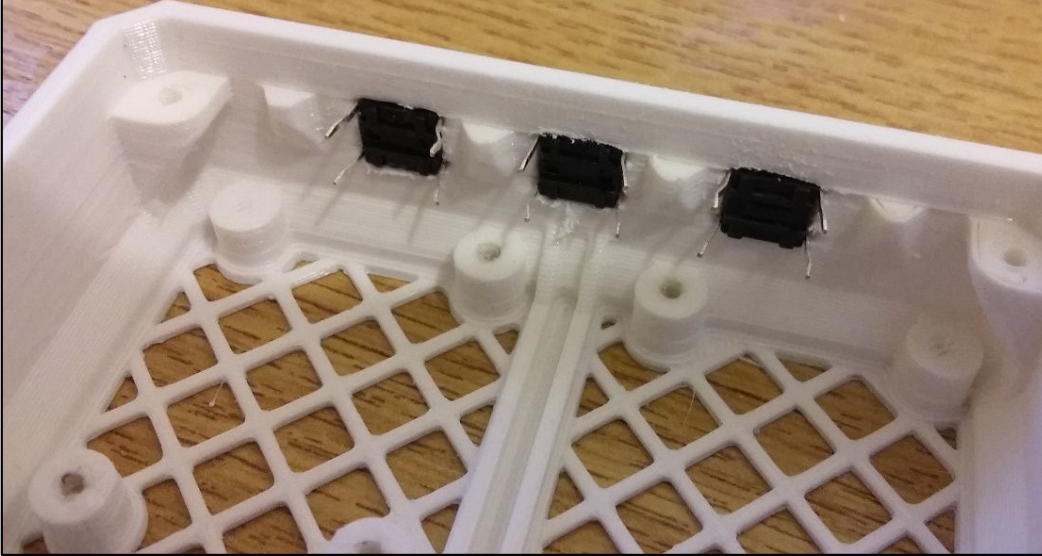
01 Button switches pressed into case before gluing




02 RGB LEDs glued into position and data wire attached



03 RGB LEDs wired to 3-pin plug

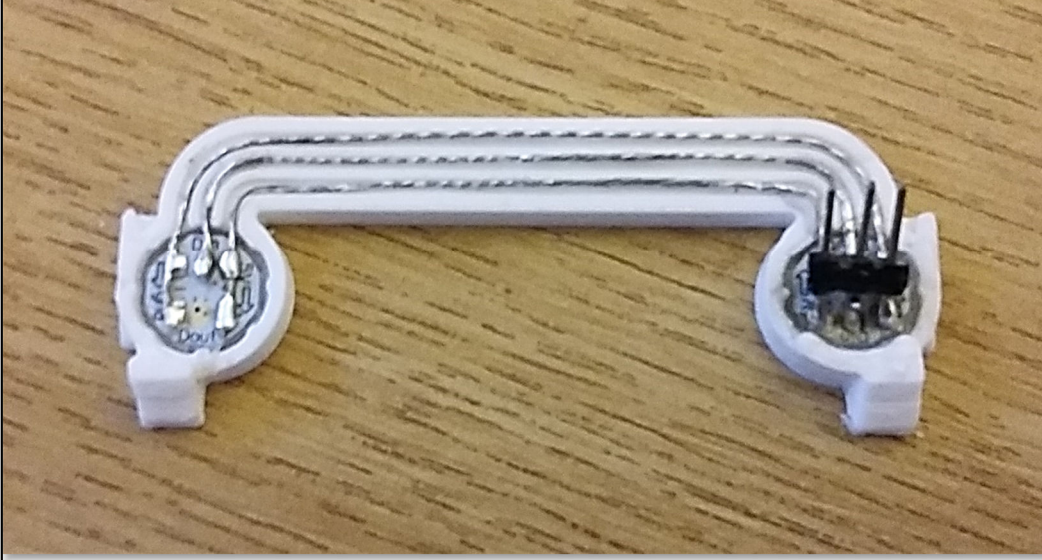

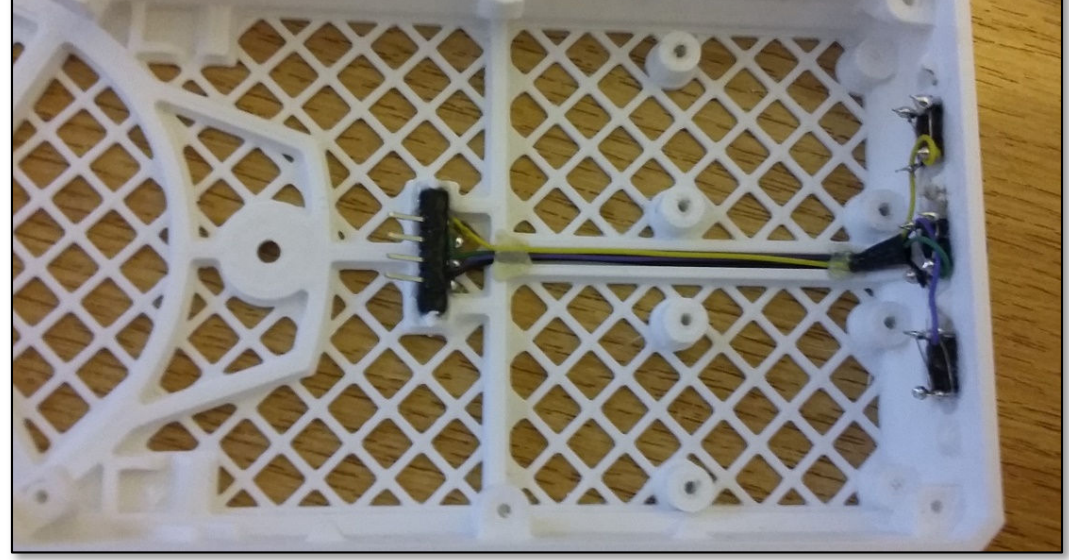04 Button switches wired to 3-pin plug in base




Wiring Sequence

05 Jumper wires are looped and tied



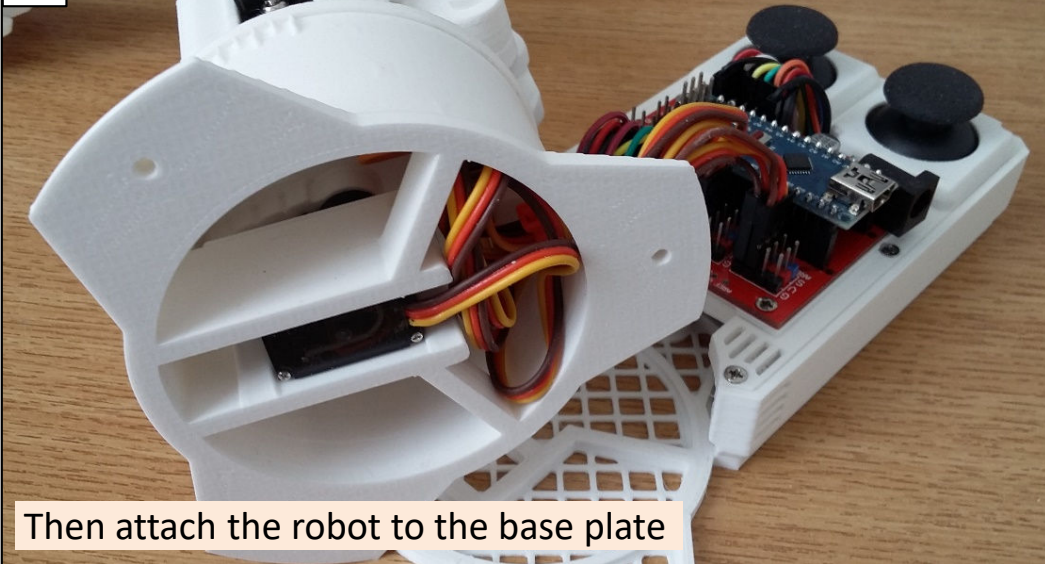06 Gather servo wire excess at rear of robot



Then attach the robot to the base plate

07

