
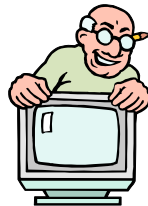
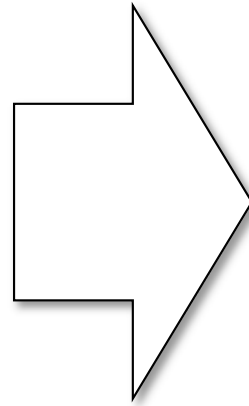


Wii WEMOS D1 Transceiver Mk1

Circuits & Wiring

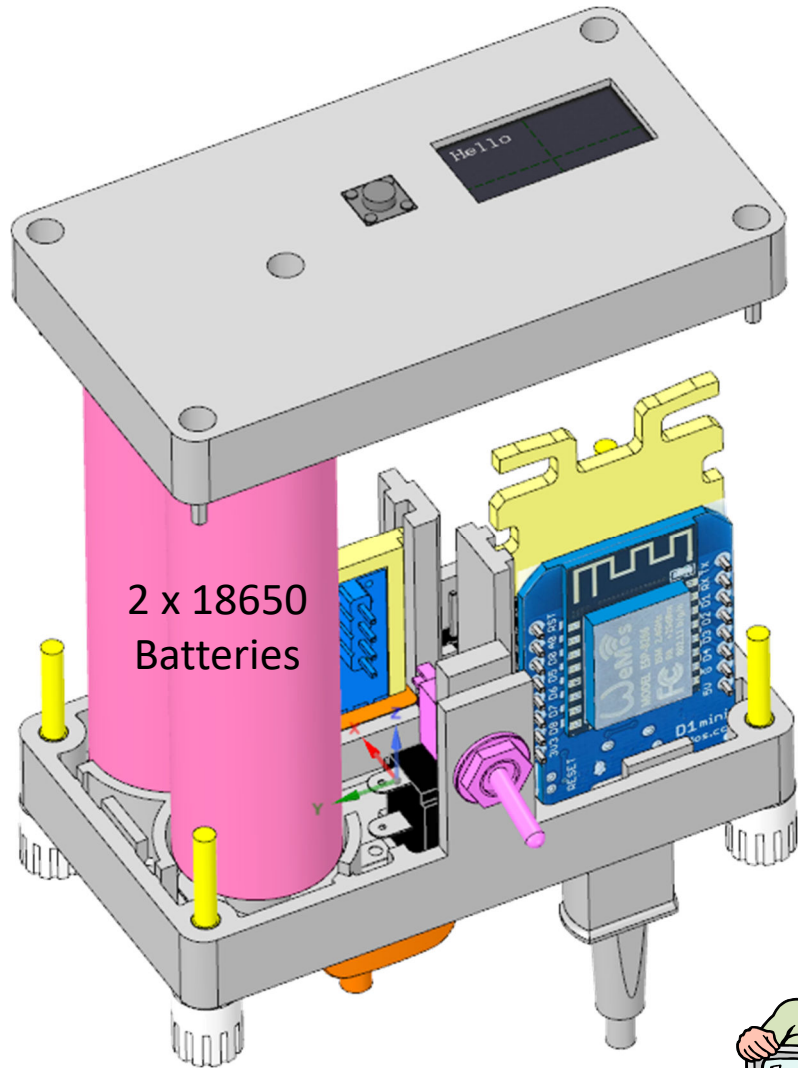

Read through this document before starting.

Hand Tools:

Recommended:

- Fine Nosed Pliers
- Side Cutters
- 1.5 mm Drill
- 2.0 mm Drill
- 4.0 mm Drill
- Needle Files
- Screwdrivers
- Craft Knife



Note: Not all items needed are shown here.

Tools & Materials:

- Temperature controlled iron
- Solder flux
- Resin cored solder
- Hot melt glue gun
- 2-part epoxy resin glue
- Screw drivers
- Wire wrapping tool
- Tweezers
- Wire wrapping wire 30 AWG
- 24 AWG stranded wire (red & black)



Test Equipment:

You will need a multimeter to:

- set up the 3v3 voltage regulator
- check/calibrate the WEMOS battery measurement
- check wiring continuity and for unwanted shorts circuits



It is useful to have one which makes a noise when a short circuit is detected, when checking the integrity of joints, so that you don't need to keep looking at the display.



Wii WEMOS D1 Transceiver Wiring

Pin	GPIO	Pin	GPIO
A0	A0	Tx	1
D0	16	Rx	3
D5	14	D1	5
D6	12	D2	4
D7	13	D3	0
D8	15	D4	2

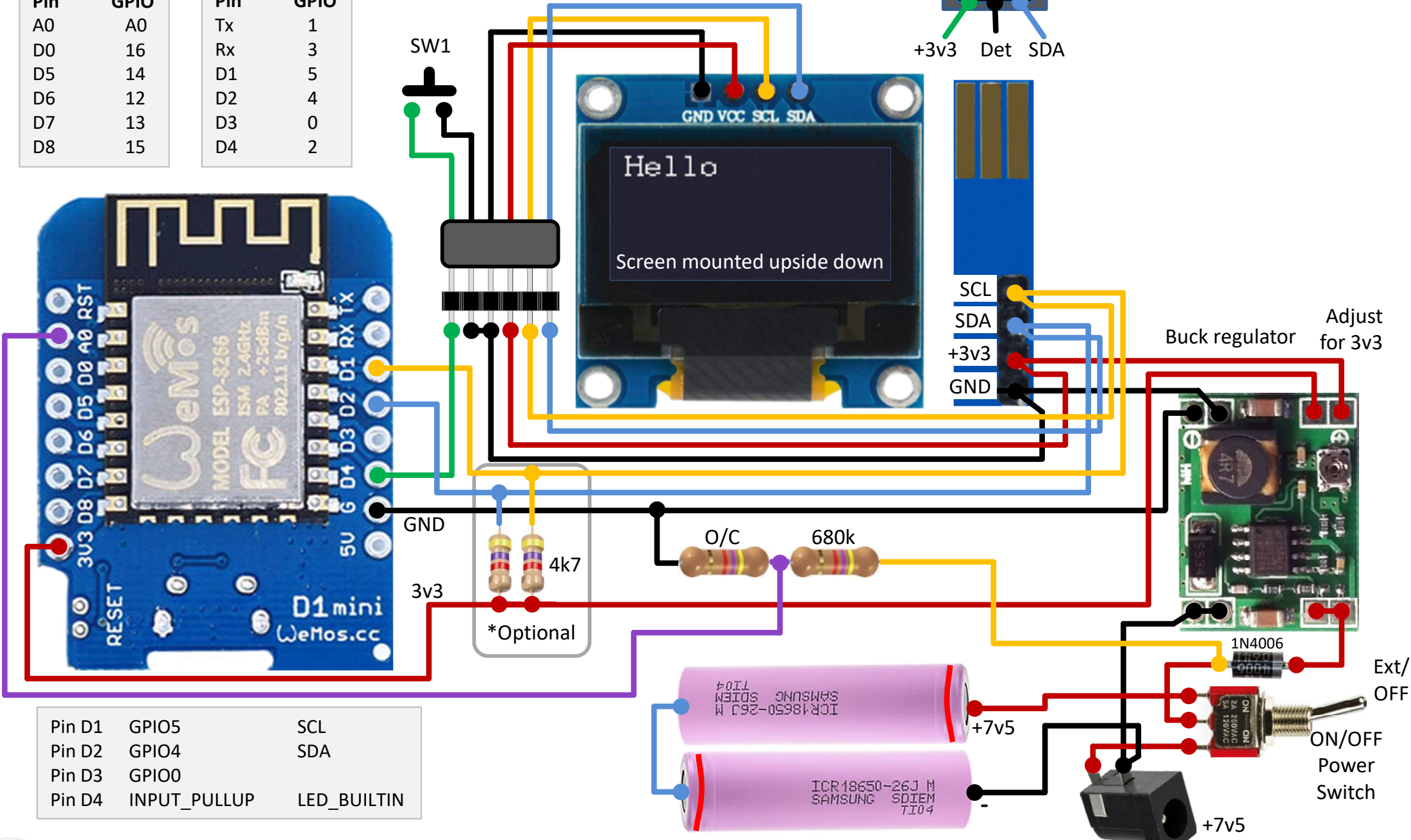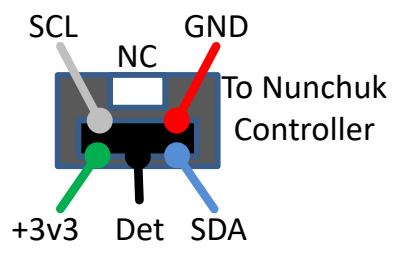Display connections can vary, ensure power Vcc and GND are of correct polarity!




Pin D1	GPIO5	SCL
Pin D2	GPIO4	SDA
Pin D3	GPIO0	
Pin D4	INPUT_PULLUP	LED_BUILTIN


WEMOS Plate Wiring

The 3v3 regulator is set up prior to gluing it into the WEMOS plate.

WEMOS D1 mini viewed from underneath

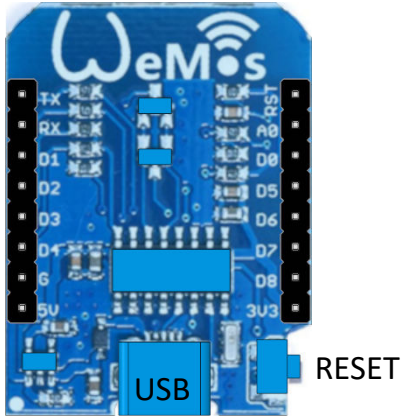


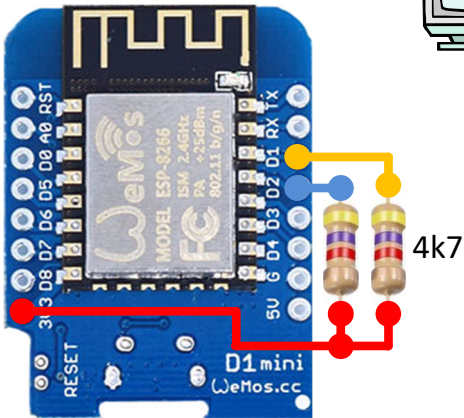*Optional I2C pullup resistors may be needed with some Wii controllers. Add if data errors are evident. Value between 2k – 10kΩ




8-pin strip, with end pins removed

SW1 OLED Display

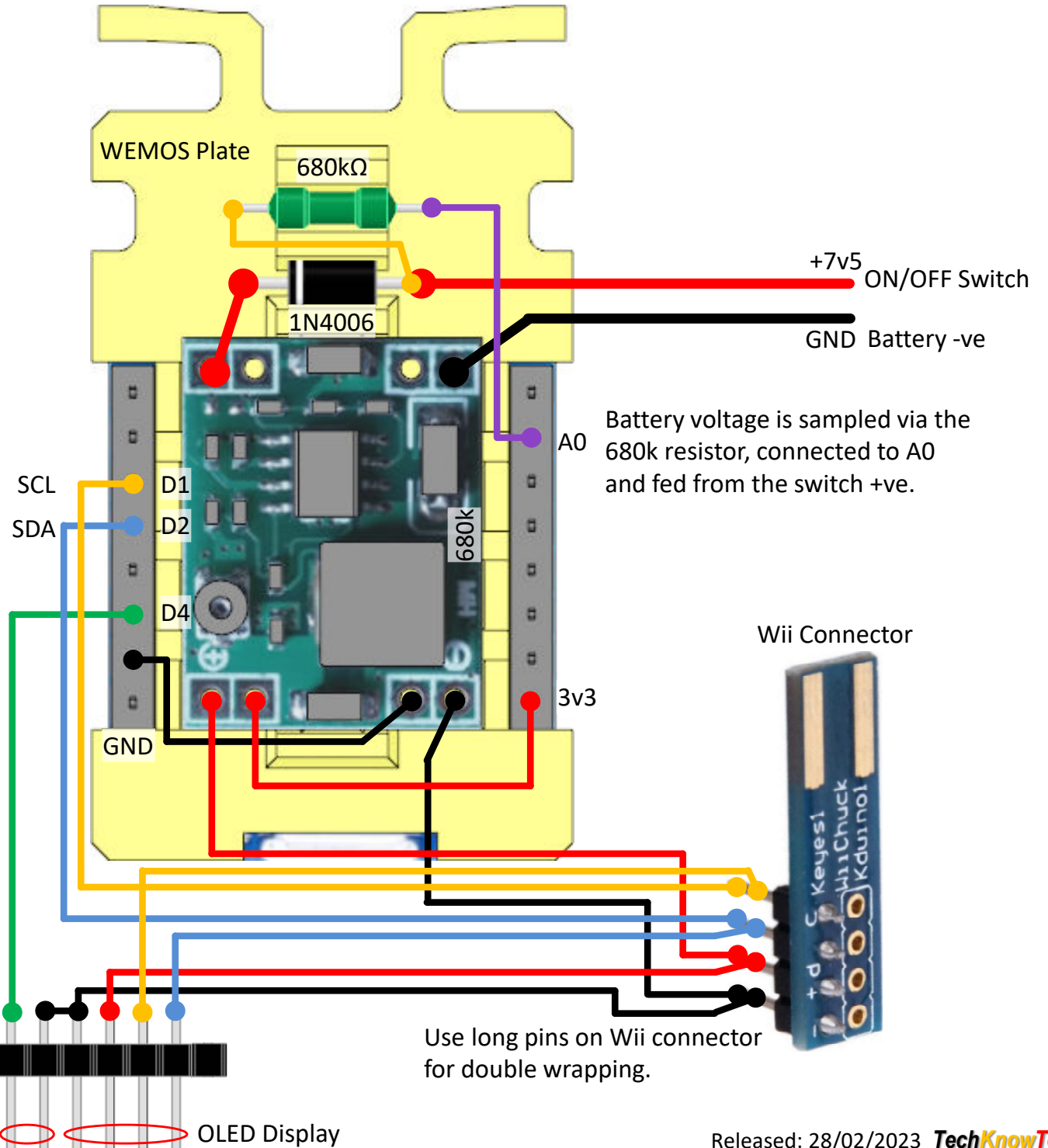

WEMOS Plate Wiring

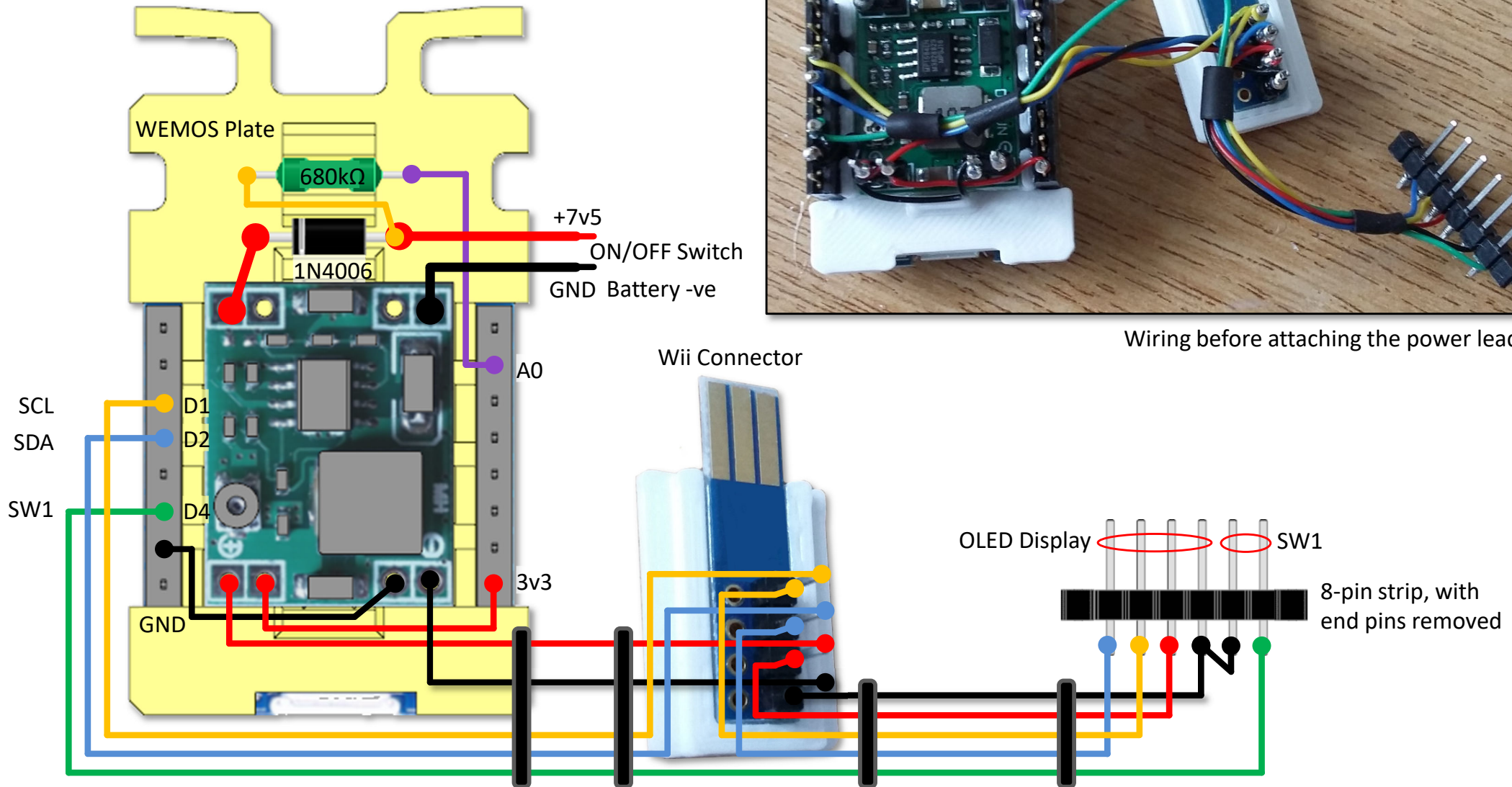These components are wired in this way before being glued into the box base.



Wiring before attaching the power leads

Use long pins on Wii connector for double wrapping. Wrap 1st set, solder then wrap the 2nd.



18650 Battery Clip Wiring

Battery -ve goes directly to the buck regulator.

Battery +ve goes to the ON/OFF switch, then to the 1N4006 diode, then the buck regulator.

DC power socket is wired to the other side of the switch, so that power is either from the battery or the socket.

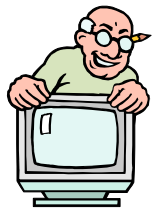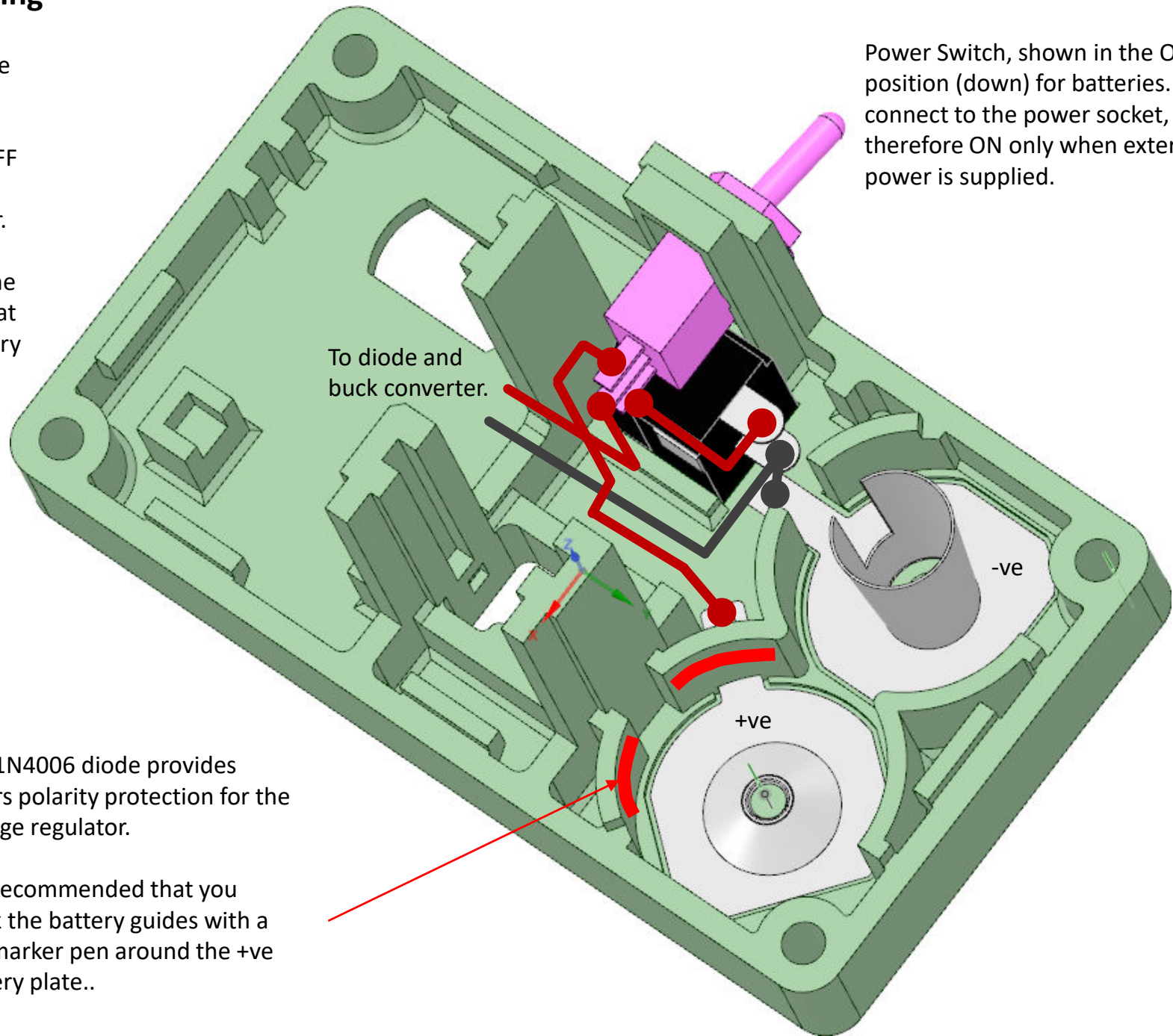Power Switch, shown in the ON position (down) for batteries. Up will connect to the power socket, and therefore ON only when external power is supplied.




The 1N4006 diode provides reverse polarity protection for the voltage regulator.

It is recommended that you mark the battery guides with a red marker pen around the +ve battery plate..



Box Lid Wiring

Pre-solder the tabs on the two battery clips separately, then apply a smear of flux to the freshly soldered connections, before gluing the clips into the box lid.


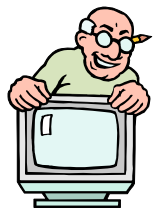
Once the glue has set, load some solder onto the end of a hot iron and use it to fuse the two tabs together.



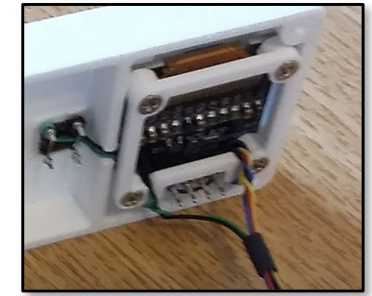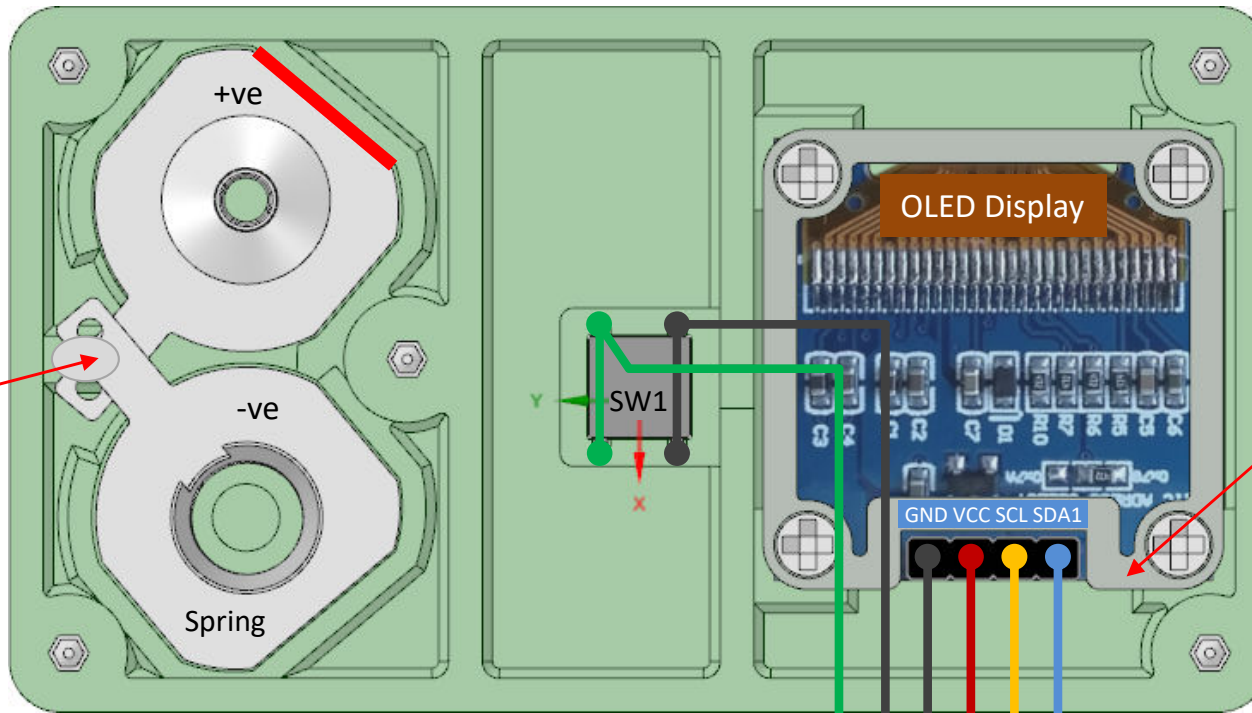The I2C harness must be at least the depth of the case. Excess length, can easily be stored in the void of the case.



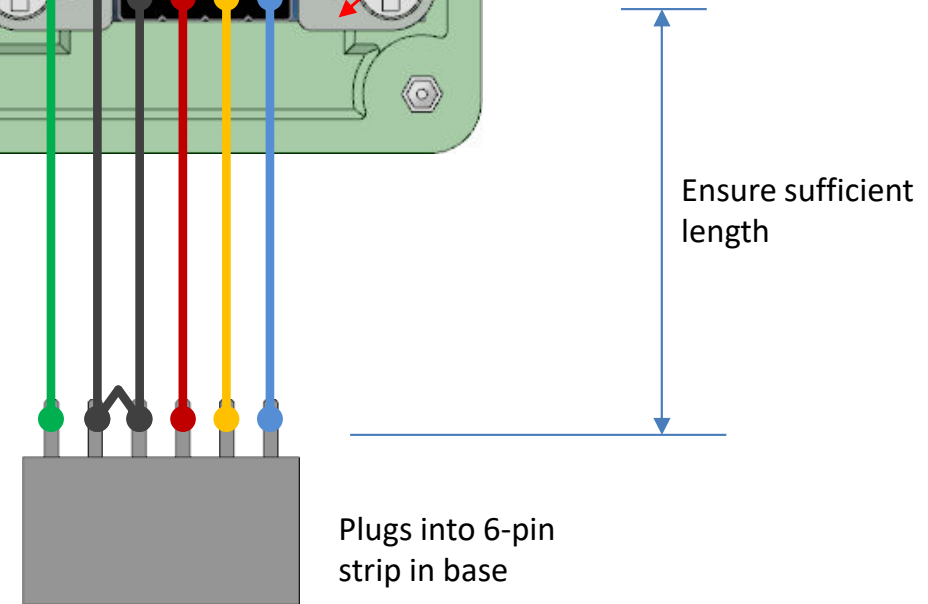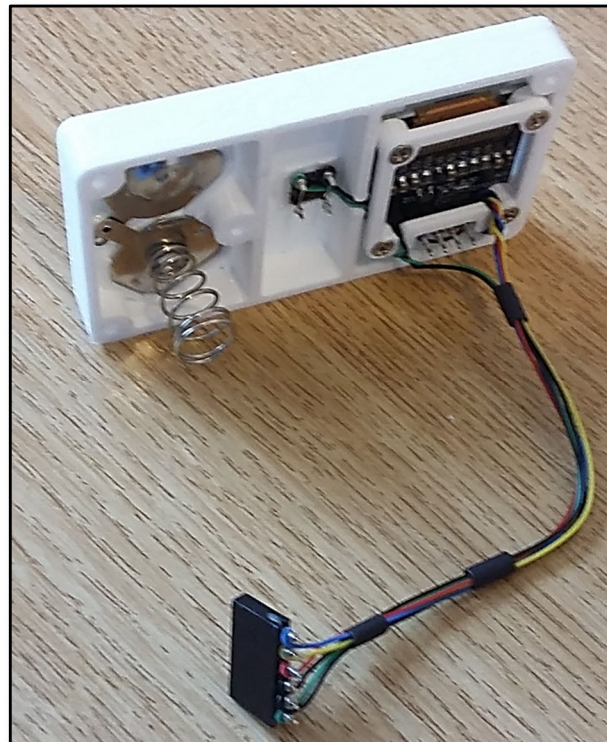
Loop wires around display strap to relieve strain.




Plug can be removed from base to allow separation from body when charging batteries if needed.

Wiring Sequence Photos


01 Solder 2-pins into the DC to DC converter

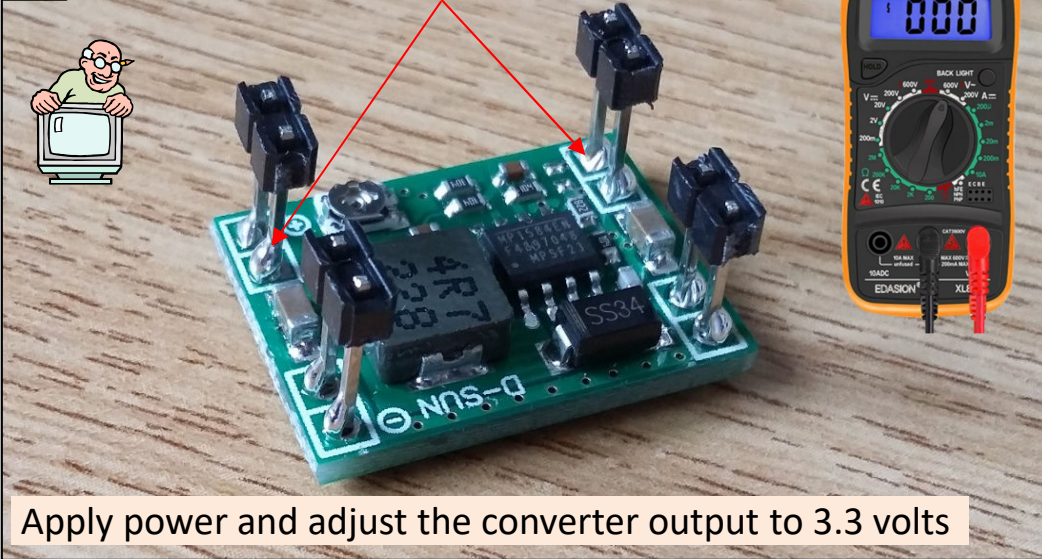

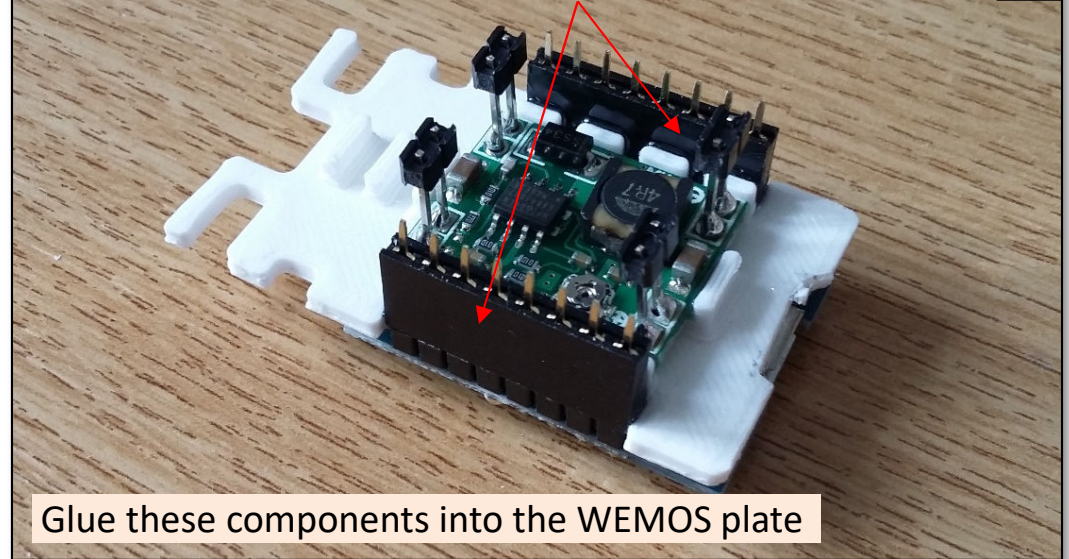
02 Attach socket strips to the WEMOS D1 micro



03 Viewed from other side

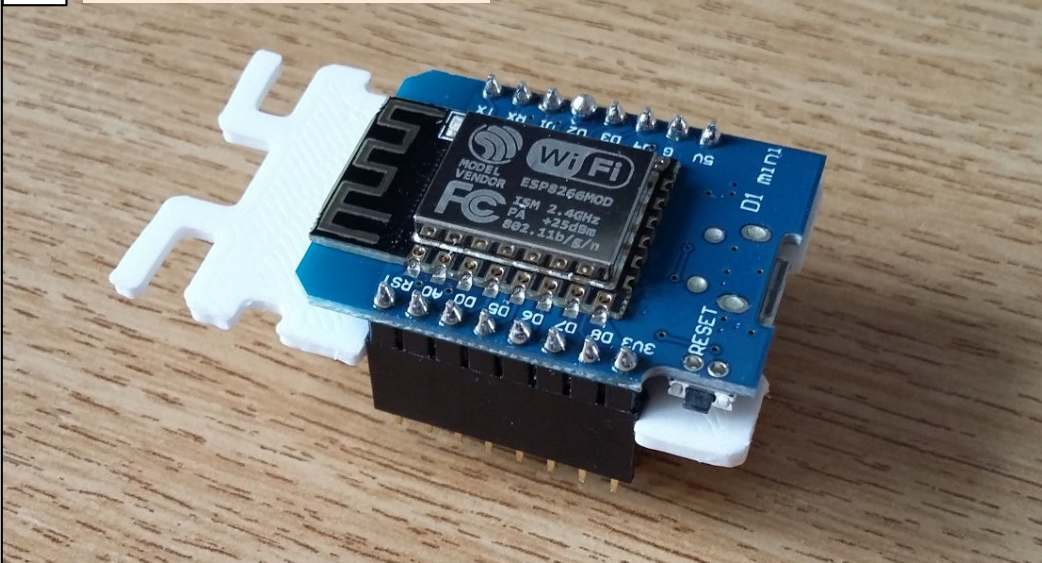


04 Glue the Wii adapter into the plate

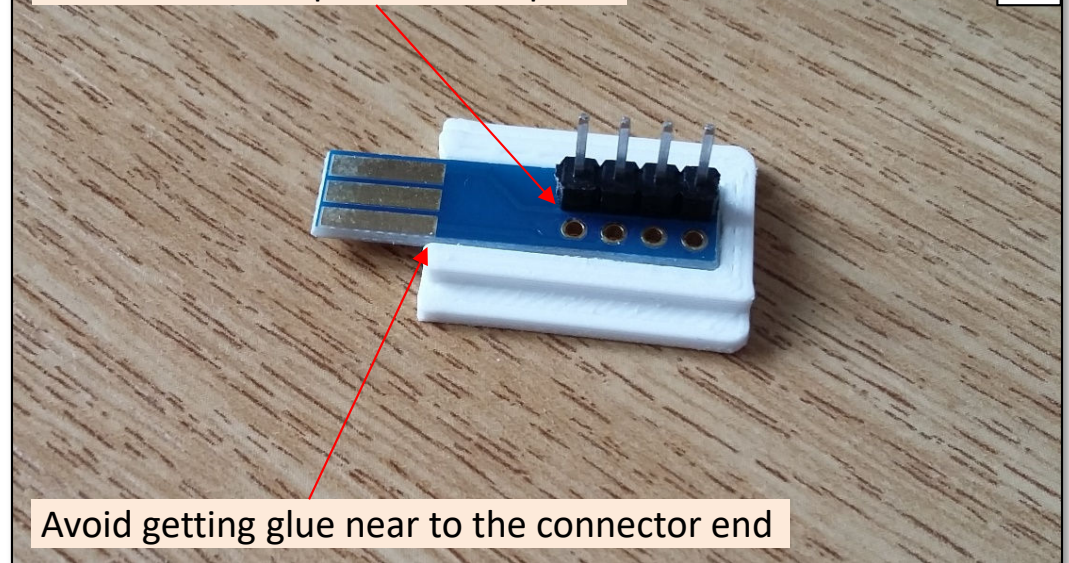


Wiring Sequence

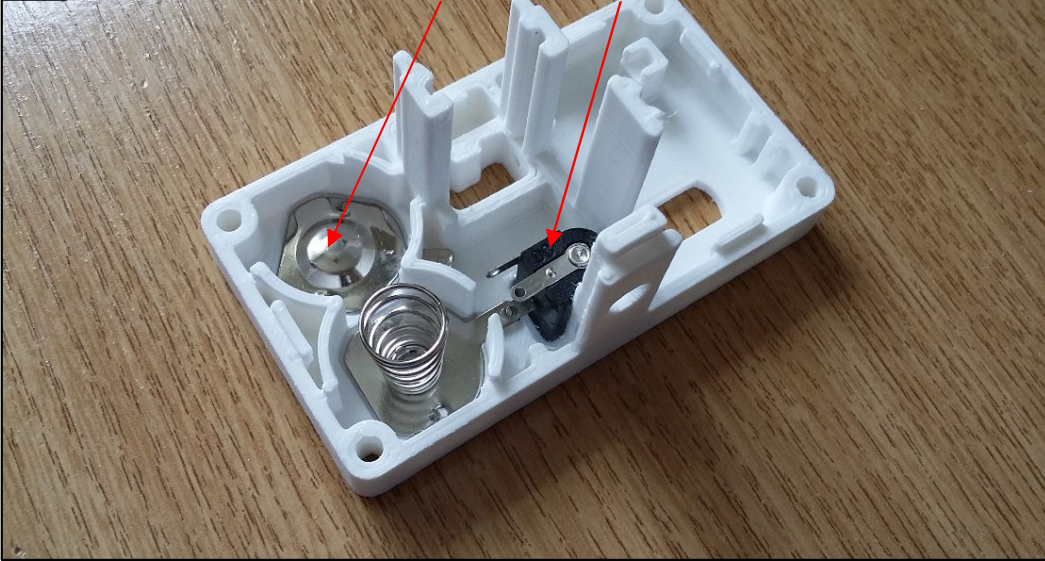05 Glue in battery connector and power socket




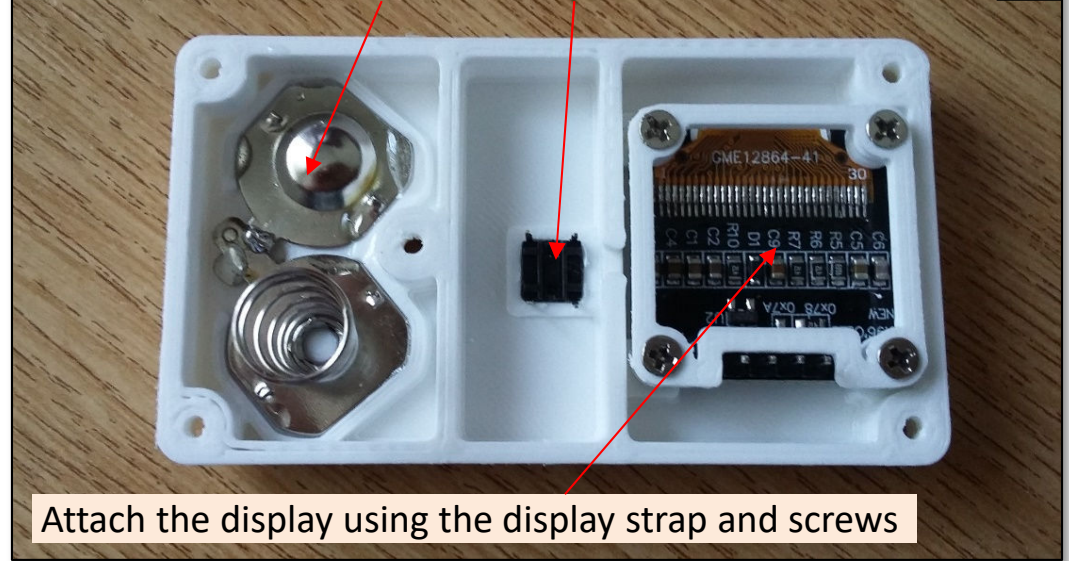06 Glue in battery connectors and button switch SW1




Attach the display using the display strap and screws

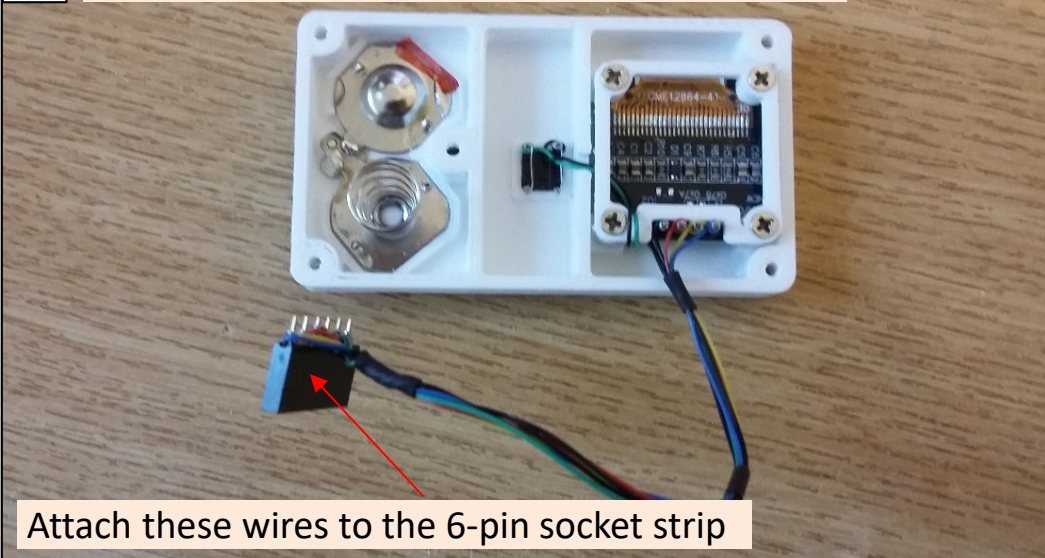07 Attach wires to the display and button switch




Attach these wires to the 6-pin socket strip

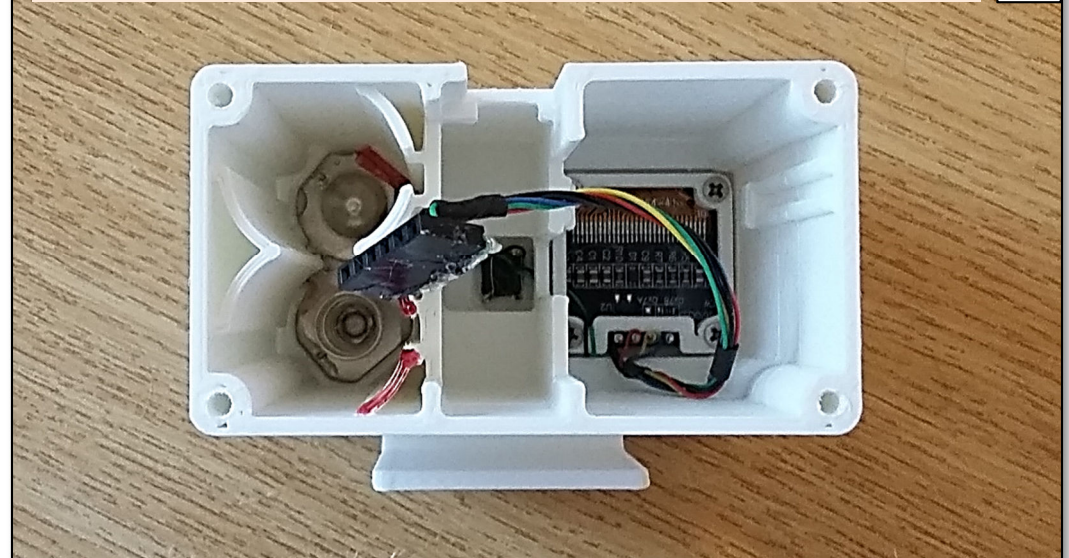08 Attach the lid to the box body using 5 self tapping screws




Wiring Sequence

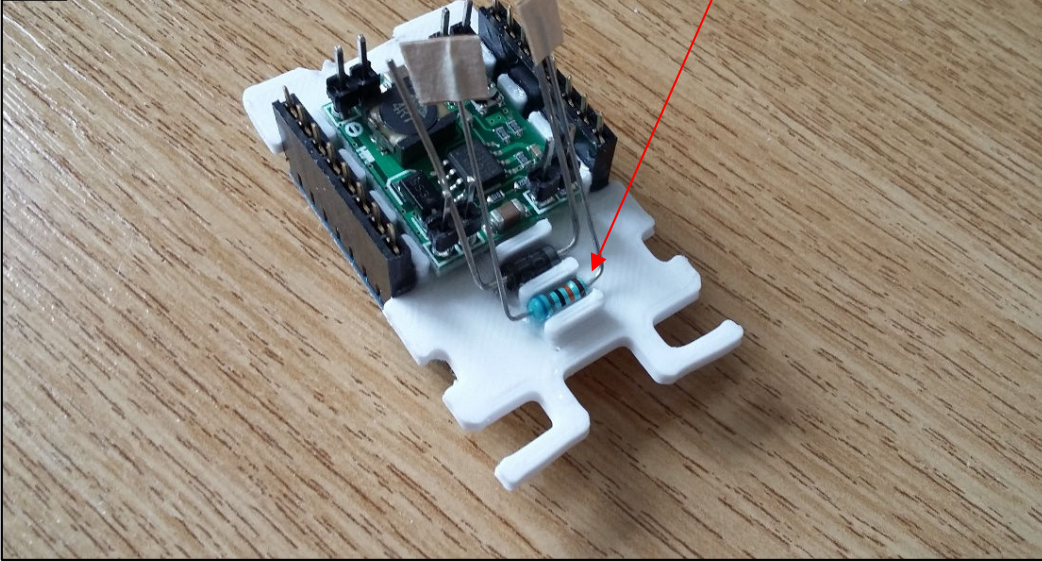
09 Glue in 1N4006 diode and 680k Ω resistor



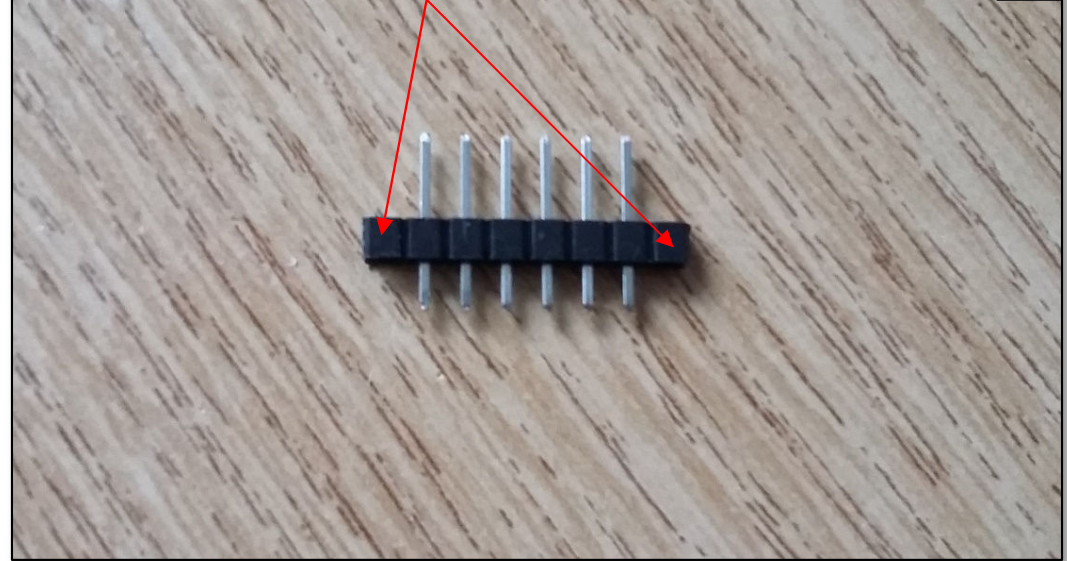
10 Remove the end pins from an 8-pin strip



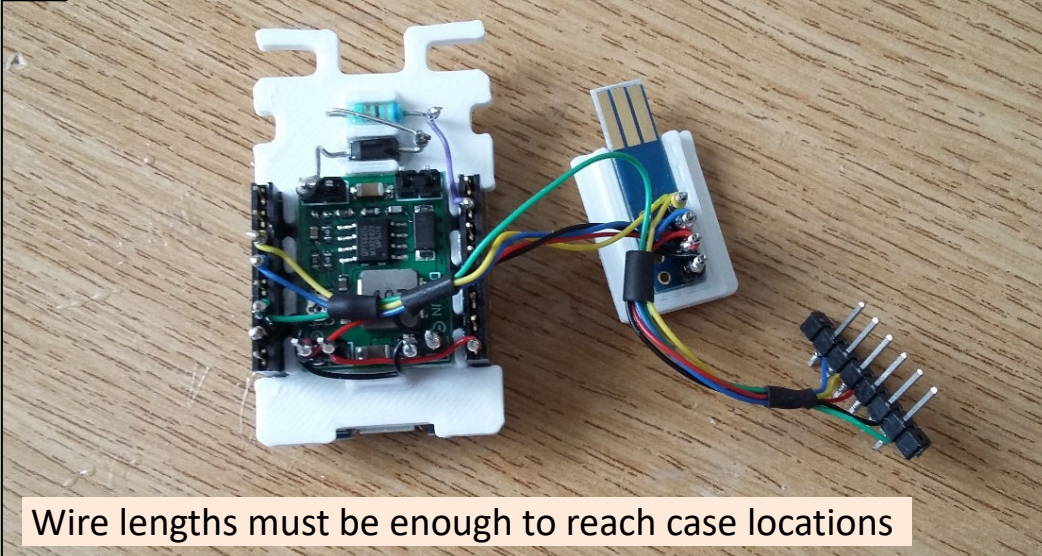11 Make the harness connecting the three components




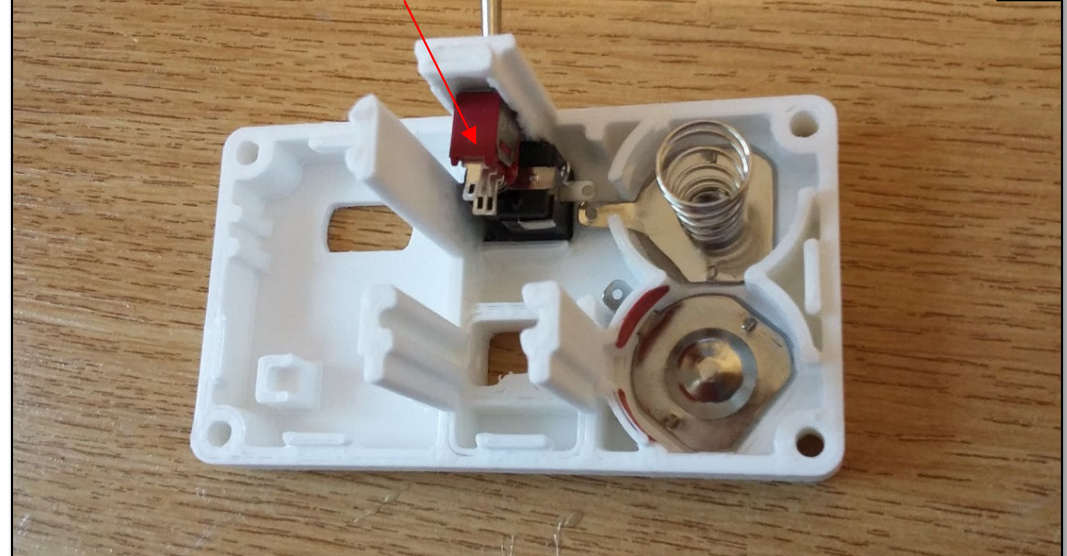12 Mount the ON/OFF switch into the base plate




Wiring Sequence

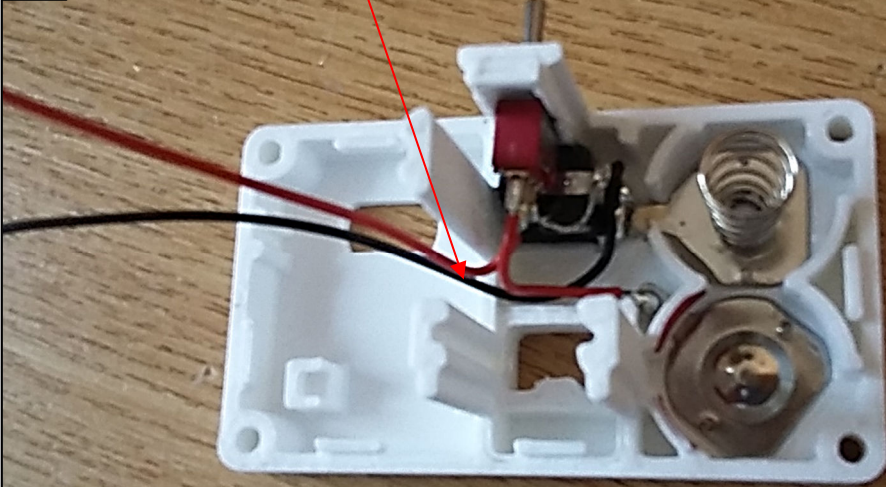13 Attach wires to the switch, socket and connectors




See earlier diagram as a guide

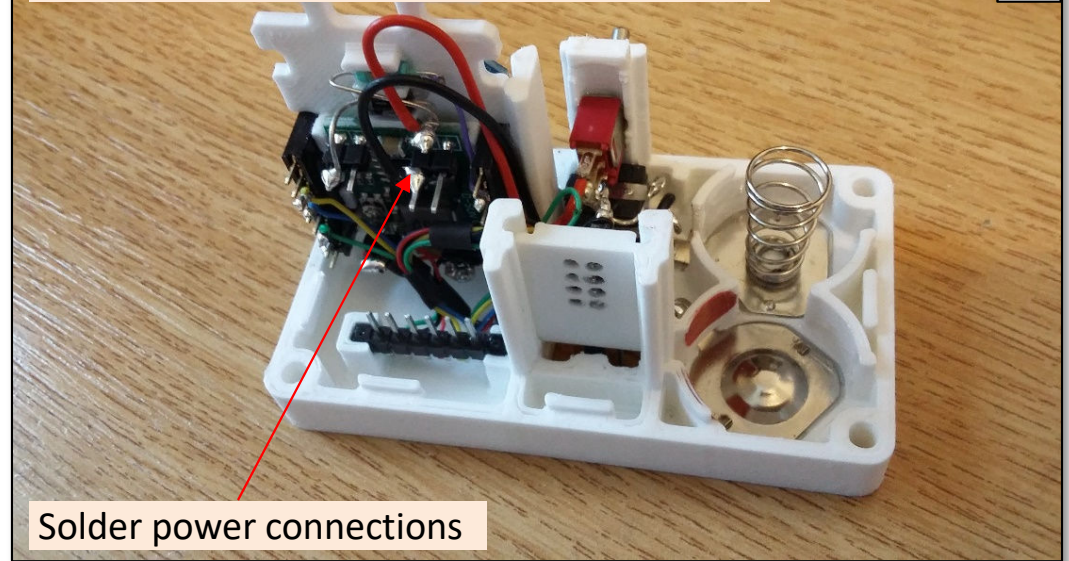14 Insert the micro and Wii connector harness




Solder power connections

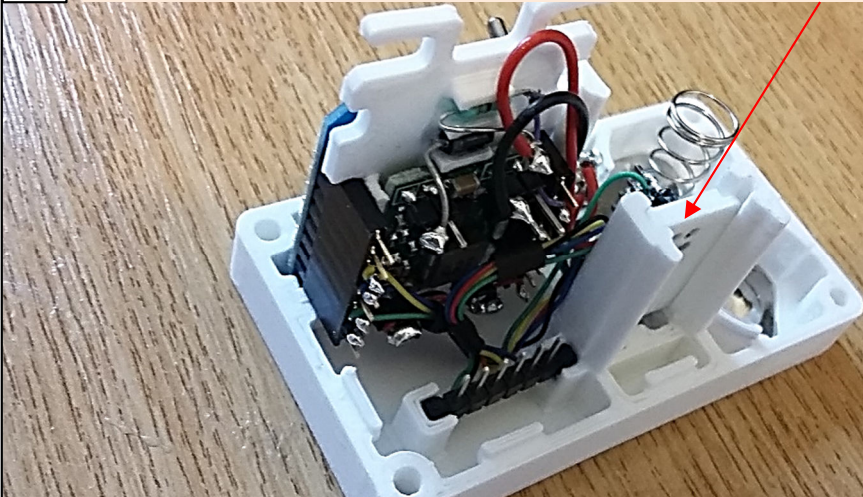15 Plug in a Wii controller, to mate with the connector



Then glue in the Wii connector plate and other components

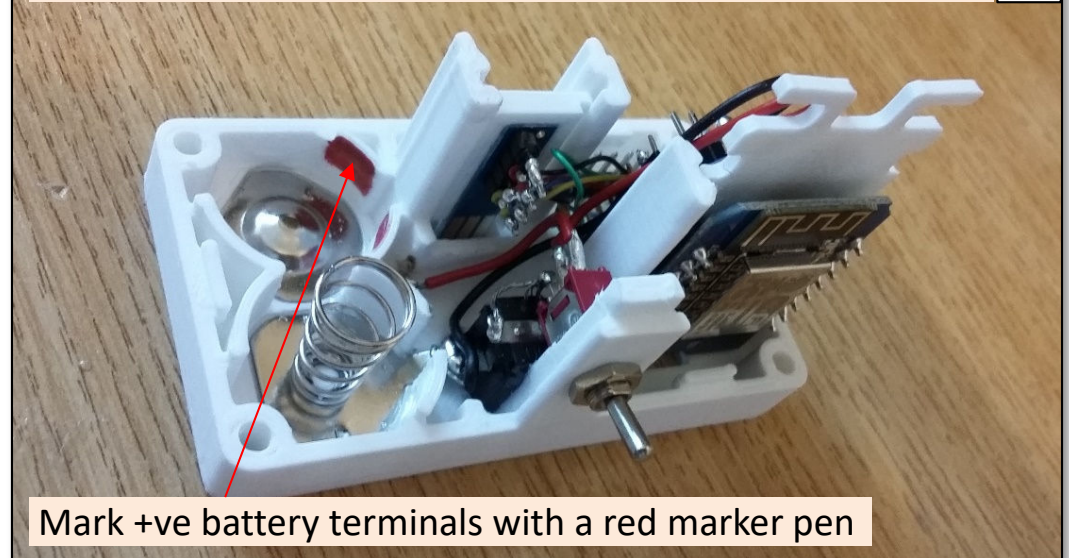16 Ensure that glue does not run onto the Wii controller plug




Mark +ve battery terminals with a red marker pen

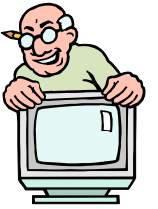2.4GHz



ESP NOW

All done, and ready for final testing.
Note that the benefit of using wire wrap is that
you can test during the build process.



Battery Voltage Health Monitoring

See 18650 discharge curve obtained from the internet. In this analysis both batteries are identical and connected in series,

Assume fully charged batteries max voltage is $V_{BM} \geq 8.2v$ max

I measured fully recharged 18650 at 8.4v when connected and ON.

Set battery warning point at $V_B = 7.00v$

Set battery critical point at $V_{BC} = 6.60v$

WEMOS D1 is powered from DC-DC buck converter at 3.3v

It has internal resistor network of 220k + 100k, so 3.2v at A0 pin gives 1.0v at $V_{ADC} == 1023$ on 10-bit converter (1023 max).

If we use a 680k resistor feeding A0 we get 10.0v == 1023

Using a Multimeter I determined the conversion factor to be 1030

MAX: $V_M = 8.2v$, gives A0 = 839 on ADC ($V_M * 102.3$)


WARNING: $V_B = 7.0v$, gives A0 = 716 on ADC ($V_B * 102.3$)

CRITICAL: $V_{BC} = 6.6v$, gives A0 = 675 on ADC ($V_{BC} * 102.3$)


The code will sample the battery voltage on power-up to ensure it is sufficient, then at every regular intervals, calculating an average to remove noise.

Given the relatively light current drawn I have assumed a linear discharge curve ranging from 8.2v (100%) to 6.6v (0%) capacity. The rate of discharge is monitored and used to actively predict the life of the battery in use.

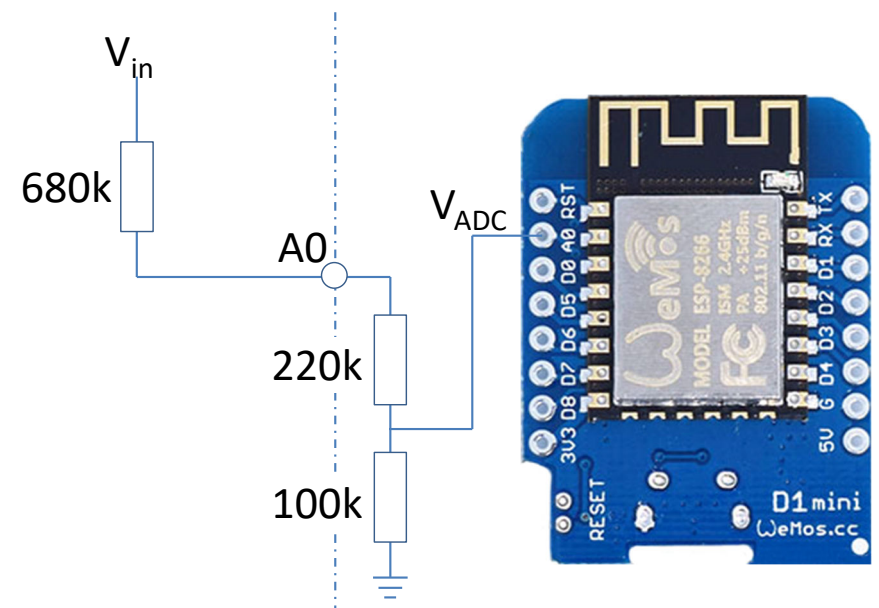Note: If connected to USB port with internal battery switched OFF the ADC will read a value much less than 5 volts. So if the micro starts with such a low reading it assumes that it is on USB power.



18650 Lithium Battery Discharge Profile

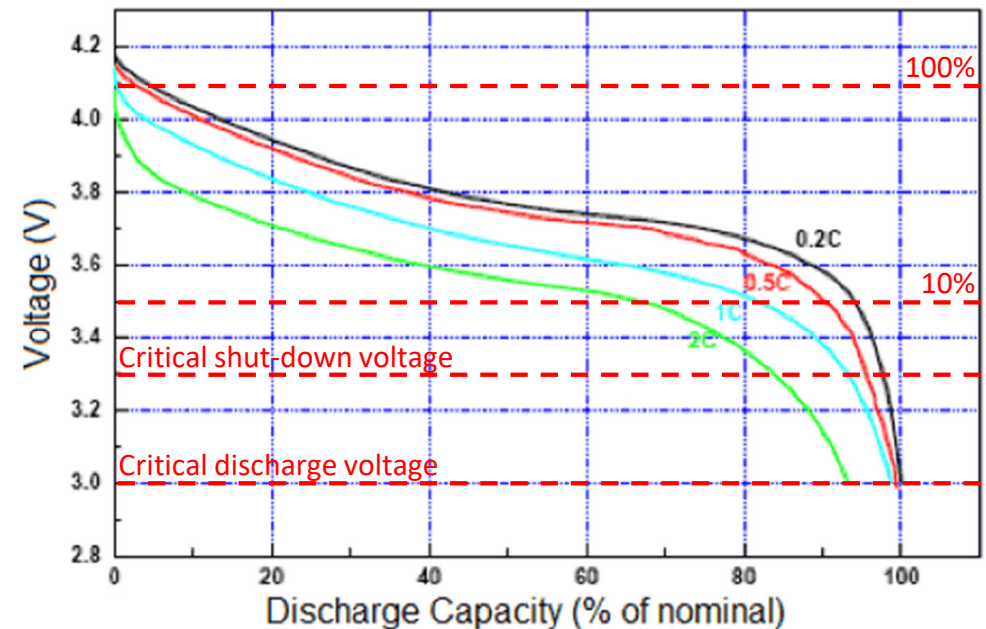

Discharge: 3.0V cutoff at room temperature.