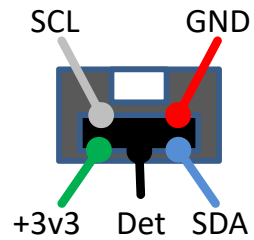


Wii Nunchuk Transceiver


Wiring Diagrams




Wii Nunchuk Controller Wiring



To Nunchuk
Controller

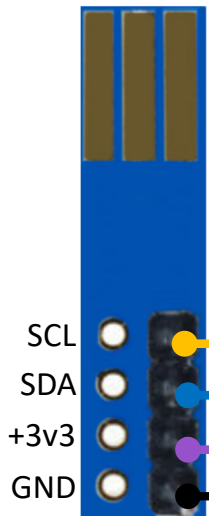


Top View

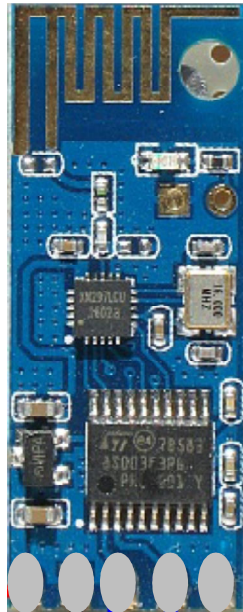


Bottom View




Bottom View

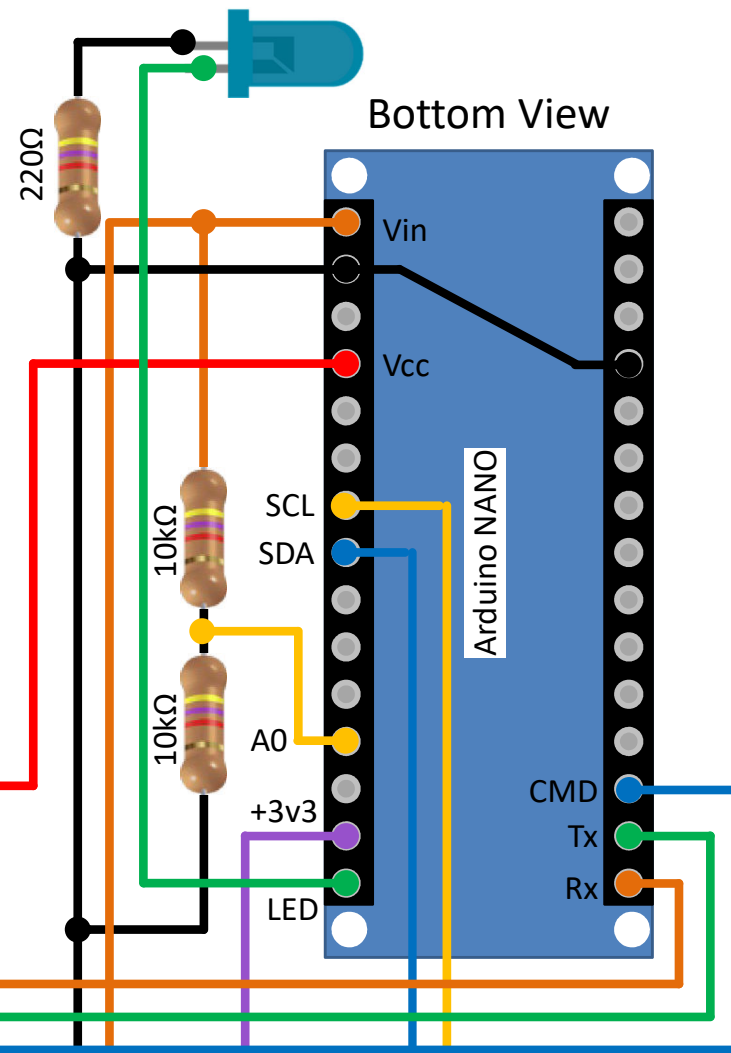

Top View

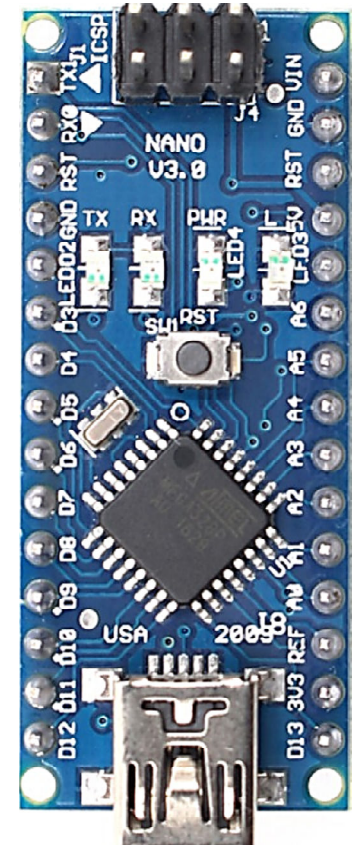


1N4006

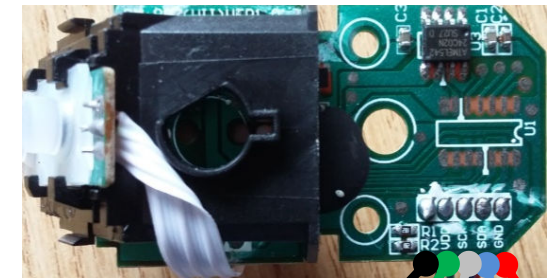


Nunchuk
Controller



Wii Nunchuk Controller Physical Wiring

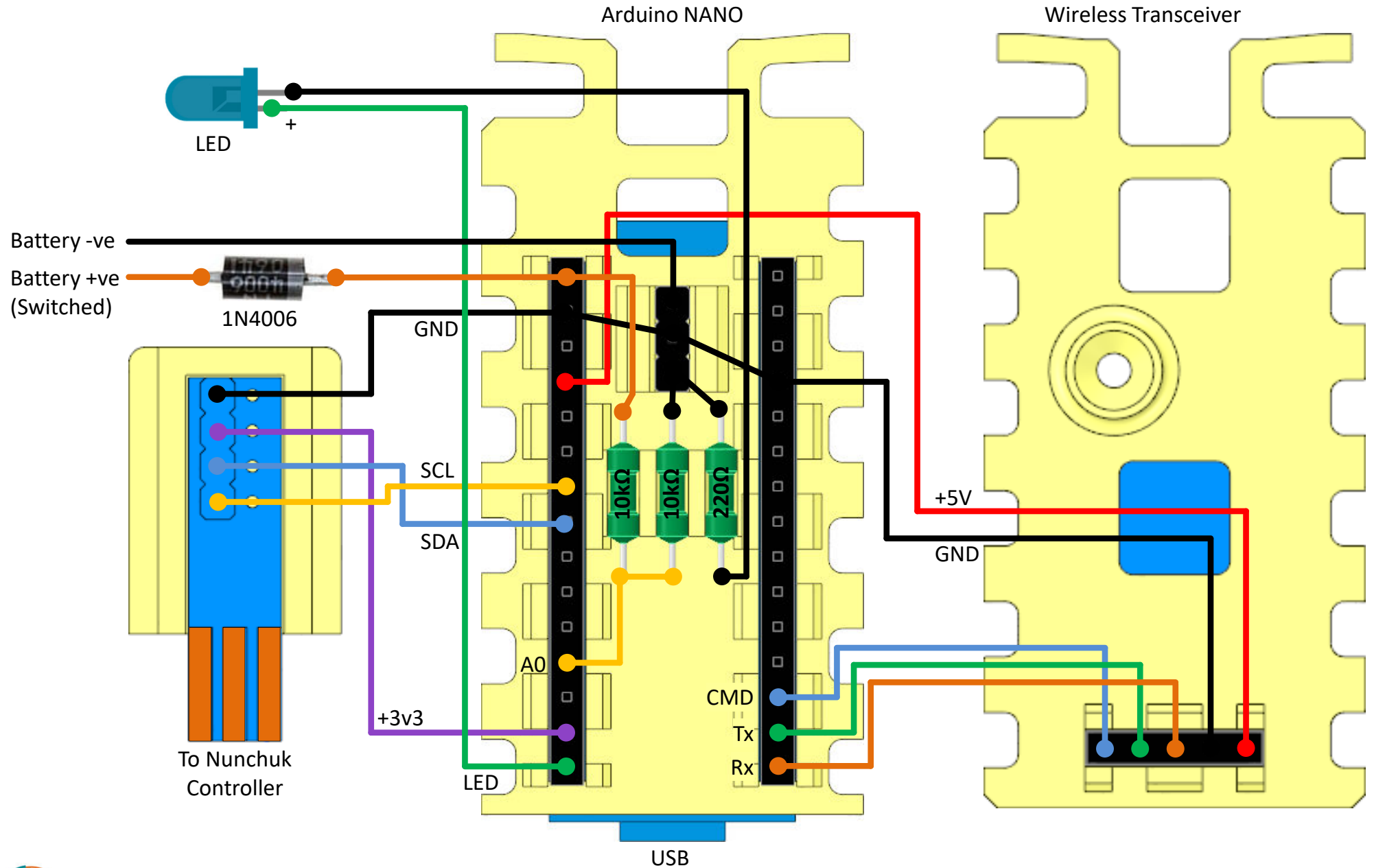

Hand Tools & Consumables

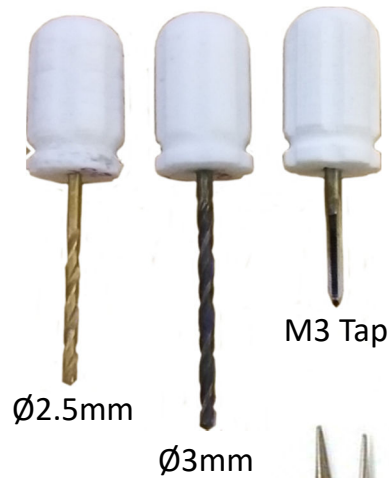

All colours not shown




I extrude thin glue rods, which I later use with an iron set to 250°, to apply the glue in a more precise manner fusing it into the PLA plastic.



Wire wrapping is used as it allows you to quickly build your circuits, test them and easily modify them as needed. You can later solder the wrapped connections for extra security, once the circuit is proven.

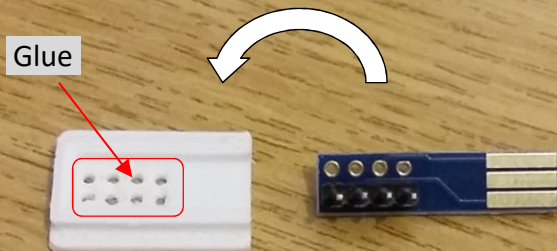
Glue the Wii Nunchuk adapter into the slide



Use two part quick setting epoxy resin glue


Ensure the adapter lies flat in the slide

Check this before gluing

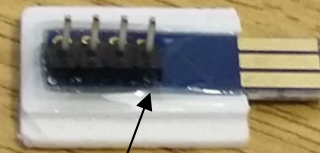


Apply extra glue to the upper edges

Ensure the 3D plastic plates are tidy

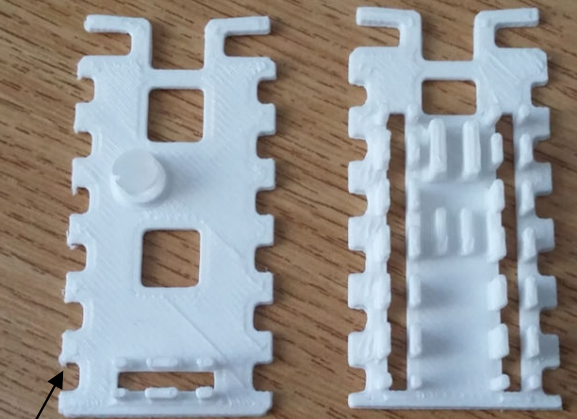

Dress to remove any brim artefacts

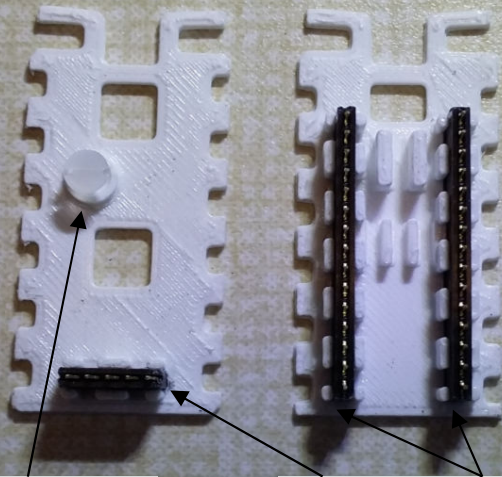Cut socket strips to length to fit both plates



Tap M3 thread


1 x 5 pins + 2 x 15 pins

Wrap wire around the 3-pin strip ends




Solder all three pins to create the GND point

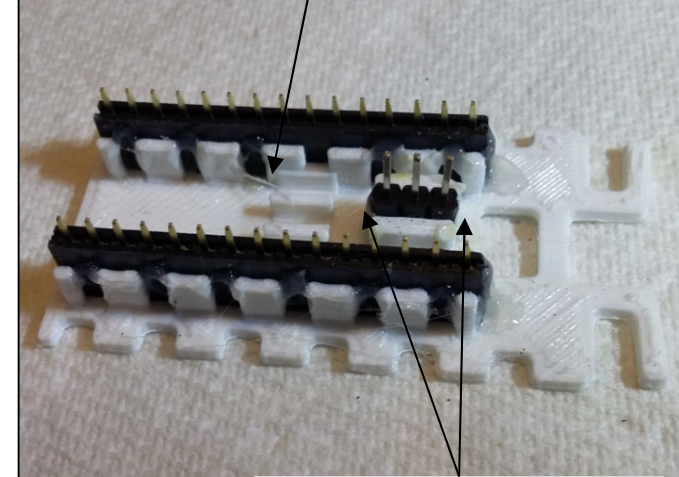Use hot-melt glue to fix the strips in place




Glue both ends of the pin strip

Cut down the NANO SPI pins to 1 mm

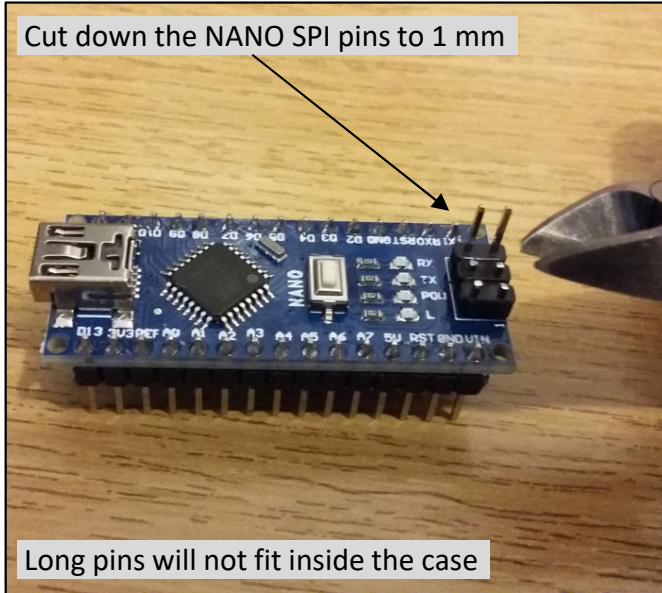


Long pins will not fit inside the case

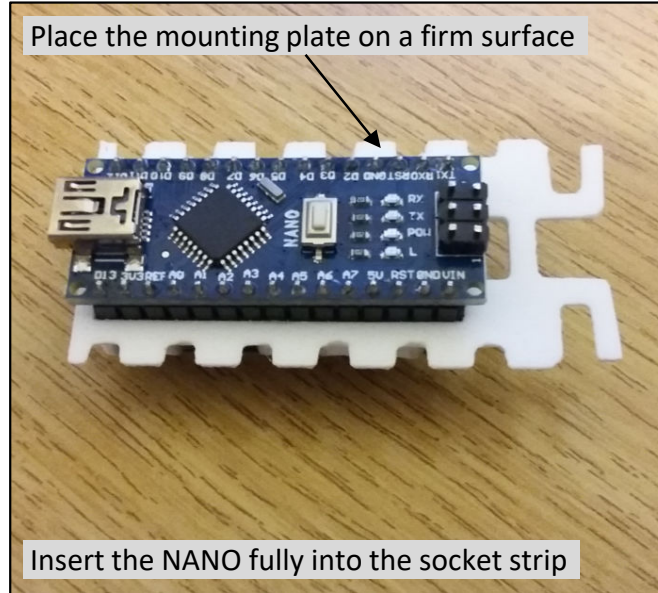Place the mounting plate on a firm surface




Insert the NANO fully into the socket strip

Do the same with the transceiver pcb

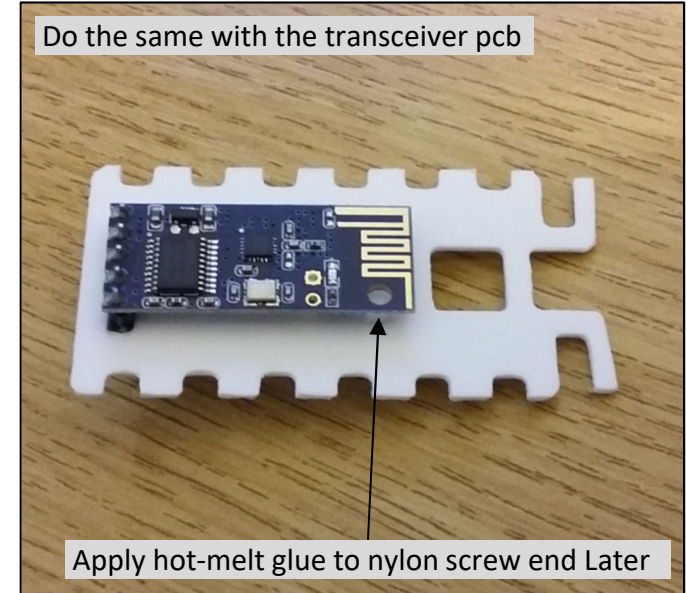


Apply hot-melt glue to nylon screw end Later

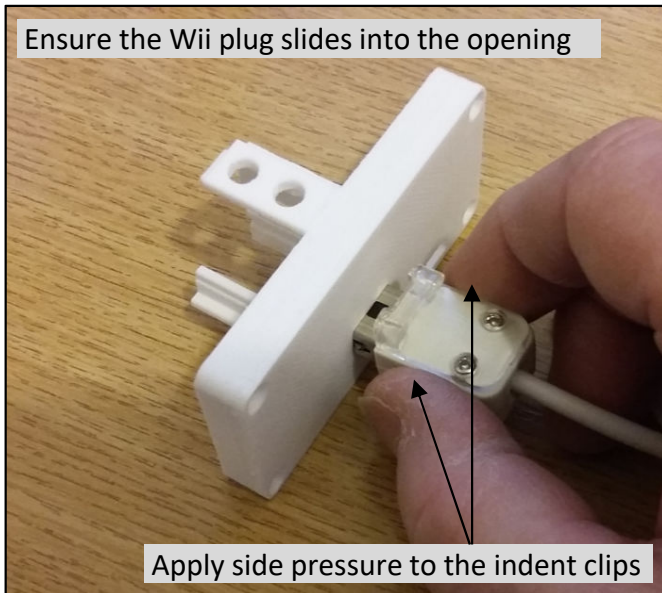Ensure the Wii plug slides into the opening




Apply side pressure to the indent clips

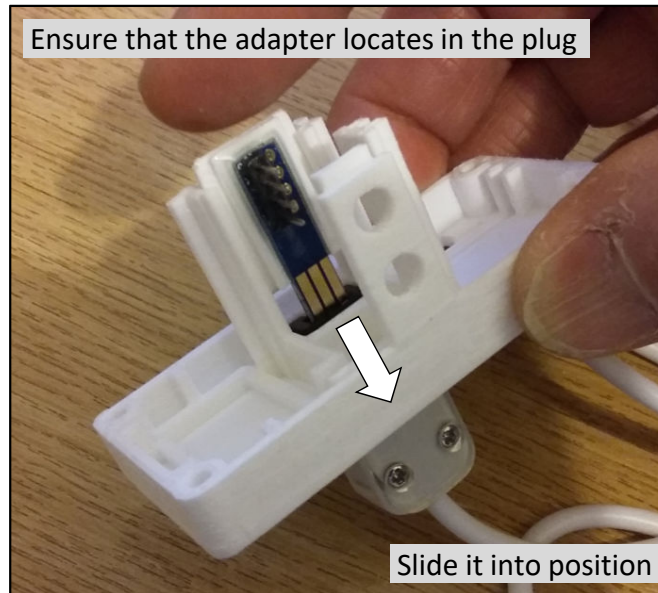Ensure that the adapter locates in the plug




Slide it into position

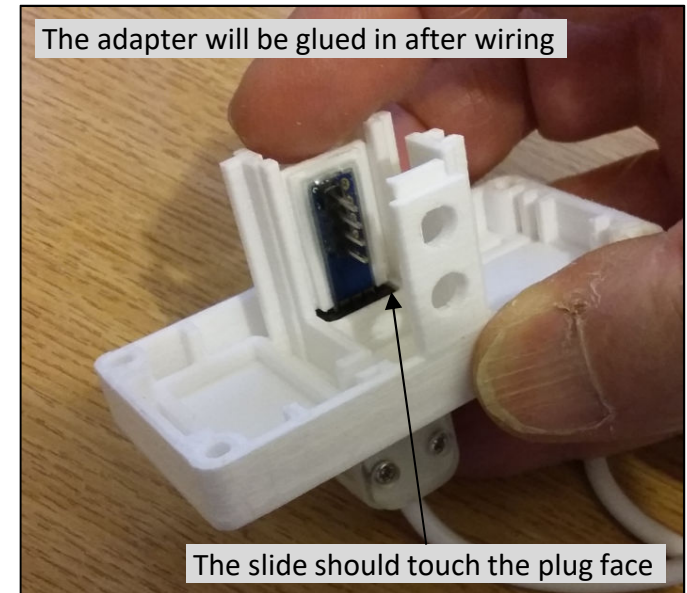The adapter will be glued in after wiring




The slide should touch the plug face

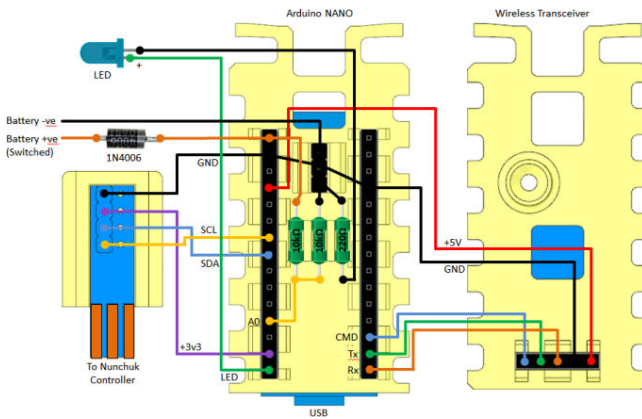Refer to the wiring diagram in the next steps




Position the 3 plates next to each other as shown

Attach wire wrap wire to the Wii adapter

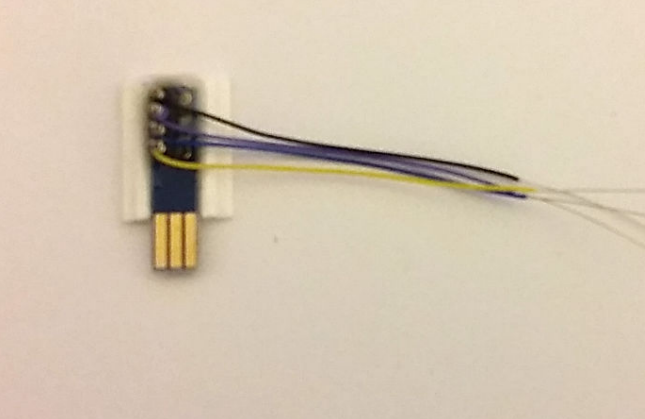

Ensure sufficient length to reach the NANO

Proceed to wire up the 3 boards

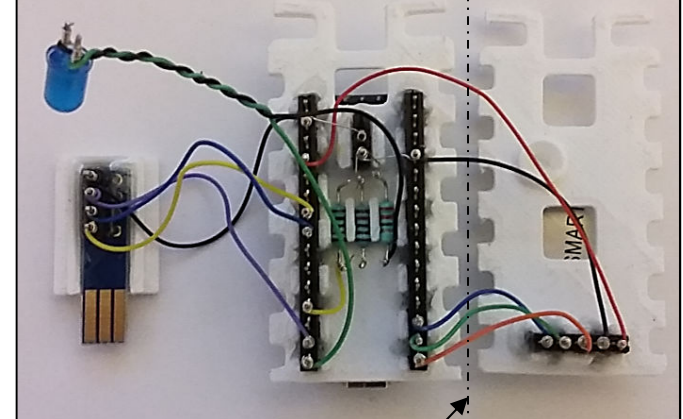


Note that wires will be folded along this line

The V_{in} wire was stripped like this

To 10k Ω resistor


This part is wrapped around V_{in} pin by hand

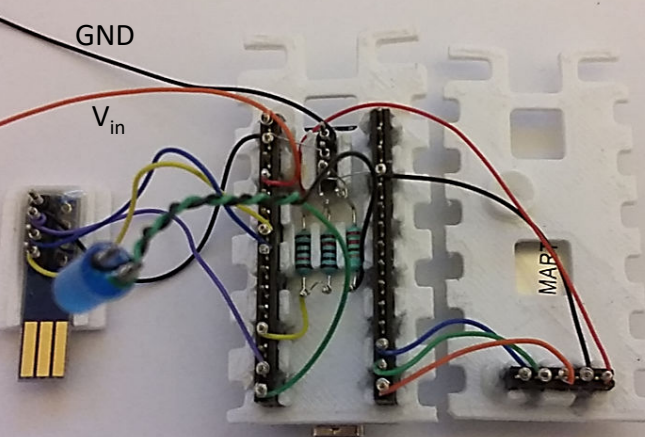The power connections will look like this








Put code in the NANO and test with Nunchuk

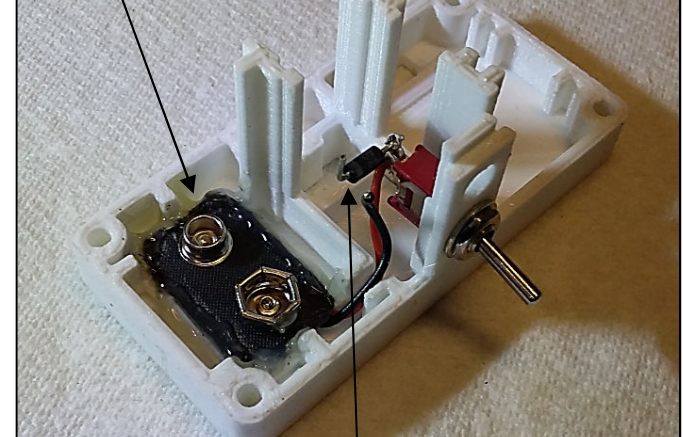Attach wires to the battery connector and glue in



Connect the 1N4006 diode to the switch

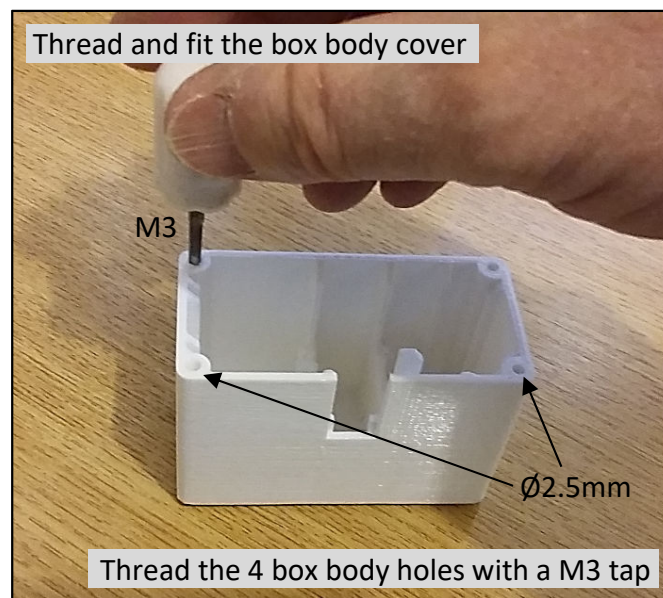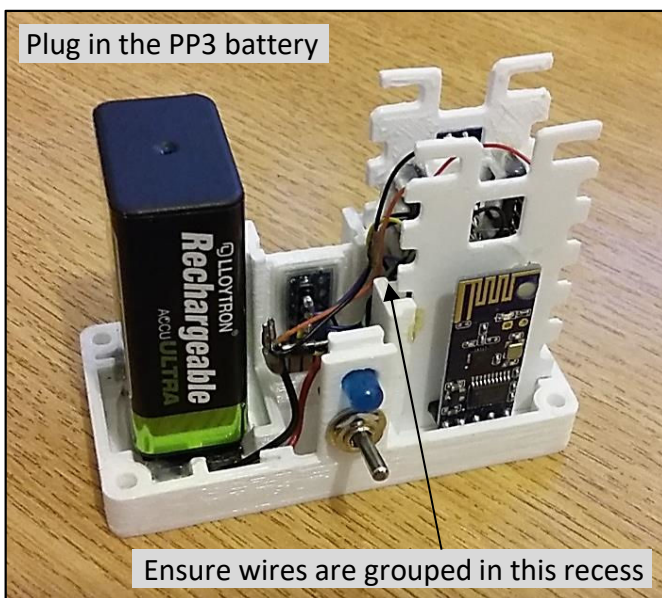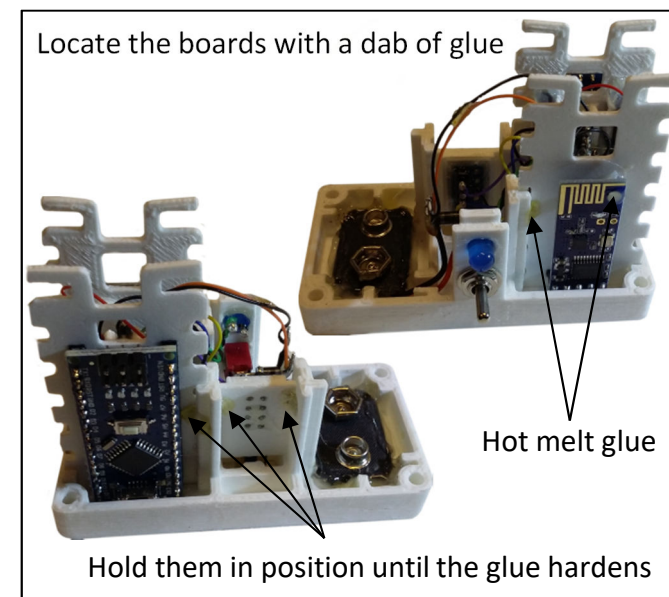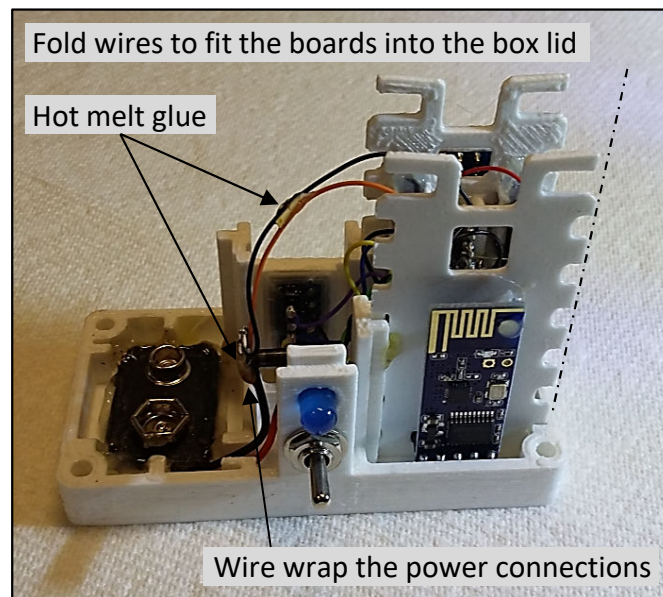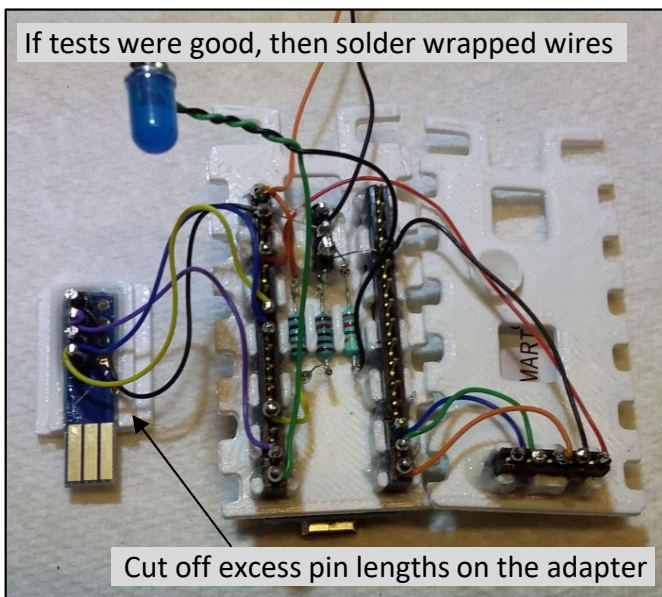

PP3 Battery Voltage Health Monitoring

See PP3 discharge curve obtained from the internet.

Assume new battery max PP3 voltage is $V_{BM} = 10\text{v}$

I measured my rechargeable PP3 at 8.65v when connected and ON.

Voltage drop across 1N4006 protection diode is $V_D = 0.77\text{v}$

Assume $V_{in} \text{ max} = V_{BM} - V_D = 9.23\text{v}$

Set battery warning point at $V_B = 7.17\text{v}$ ($V_{in} = 6.4\text{v}$)

Set battery critical point at $V_{BC} = 6.97\text{v}$ ($V_{in} = 6.2\text{v}$)

Arduino voltage regulator works well down to 6.2v

At max battery voltage, A0 input must be $\leq 5\text{v}$. Hence resistor divider network values will be set as equal.

So $V_{in} \text{ max}$ at 10v , $A0 == 4.615\text{v}$, which is 944 on 10-bit ADC


WARNING: $V_{in} = 6.4\text{v}$, gives $A0 = 3.2\text{v}$, which is 655 on ADC

CRITICAL: $V_{in} = 6.2\text{v}$, gives $A0 = 3.1\text{v}$, which is 634 on ADC

The Arduino code will sample the battery voltage on power-up to ensure it is sufficient, then at every 100ms interval, calculating a one second average ($/10$) to remove noise.

Resistor values are equal and suggested to be in the range $10\text{k} - 50\text{k}\Omega$, to reduce wasted power consumption. I used $10\text{k}\Omega$.

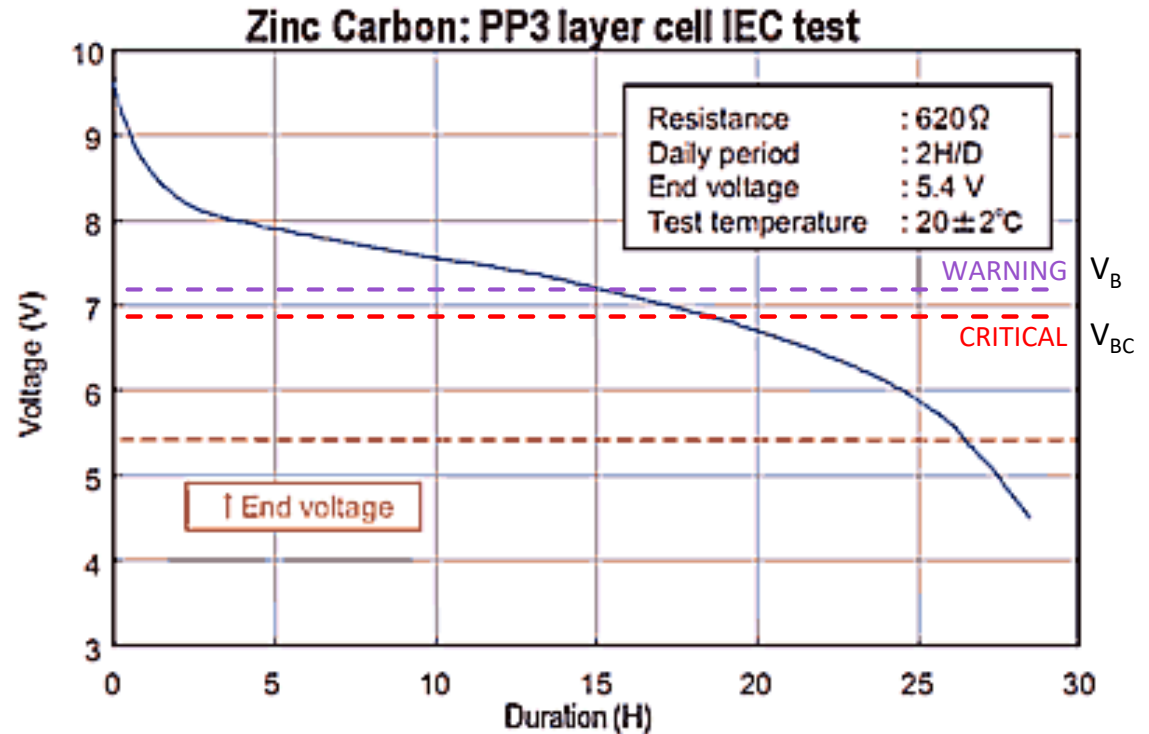Note: If connected to USB port with internal battery not switched on the ADC will read a value approximately half that of the USB voltage, specified as $5\text{v} + 0.25/-0.60 ==$



Wi-Fi Receiver Wiring

This diagram represents the Wi-Fi receiving elements only of a project, which is likely to have much more circuitry; like servo motors, sensors and display for example.

As the transceiver is connected to the NANO Tx/Rx pins you don't need to use the serial library or waste additional pins. But don't try to program your NANO whilst the transceiver is receiving data, it will fail.

The CMD wire can be used at any time to switch the transceiver into AT Command mode, at 9600 baud.

This circuit assumes that you may wish to monitor the local battery voltage and send that data back over the wireless link. This data is also present on the UB port, when connected to a PC.

